

# Digital Electronics

## Tutorial Sheet 12

---

- 1.\* Show that a binary down-counter can be implemented using a binary up-counter. To do this, draw the transition table for a 4-bit up-counter and for a 4-bit down counter and then consider the relationship between corresponding bits in the two tables.
- 2.\*\* A 3-bit synchronous counter with a synchronous  $\overline{\text{CLEAR}}$  input is connected as shown below in Figure 1. Draw a state diagram for the circuit. Draw also the modified state diagram if the  $\overline{\text{CLEAR}}$  input were asynchronous? Finally, draw the modified logic symbol.
- 3.\*\* The circuit below in Figure 2 uses a 4-bit synchronous binary counter with a synchronous  $\overline{\text{LOAD}}$  input. The signal TC is high whenever the contents of the counter equal 15. The frequency of CLOCK is 16 kHz.
  - a) If  $N_{3:0} = 5$ , draw a state diagram for the counter.
  - b) If  $N_{3:0} = 5$ , what is the frequency of the signal OUT?
  - c) Derive a general formula giving the frequency of OUT in terms of the value N.
  - d) What is the frequency of the signal OUT if  $N=15$ ?

 


Figure 1

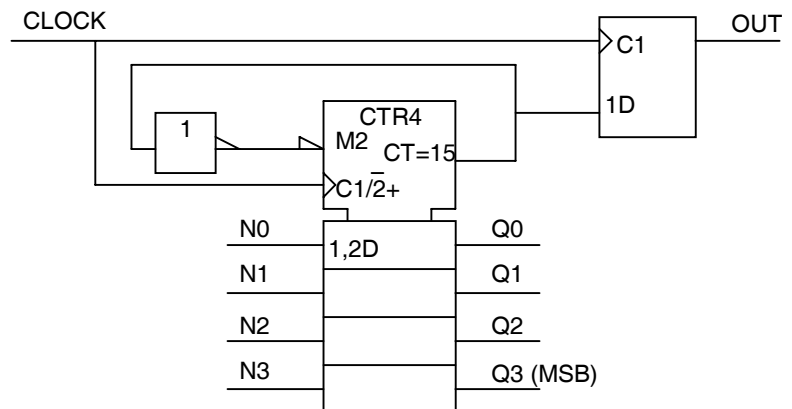


Figure 2