

Digital Electronics

Tutorial Sheet 8

- 1.* What is meant by "efficient" implementation of logic?
- 2.** Implement the following logic using (a) gates and (b) ROM. Comment on the efficiency of both implementations.

$$f = \overline{A}BCD + \overline{A}\overline{B}\overline{C}D + \overline{A}\overline{B}C\overline{D} + \overline{A}B\overline{C}D + \overline{A}B\overline{C}\overline{D} + \overline{A}BC\overline{D} + \overline{A}BCD$$

For the case of ROM implementation, consider a 64 x 1 bit device and construct a memory map as follows:

	Col 0 Cells 0-7	Col 1 Cells 8-15	Col 2 Cells 16-23	Col 3 Cells 24-31	Col 4 Cells 32-39	Col 5 Cells 40-47	Col 6 Cells 48-55	Col 7 Cells 56-63
Row 0								
Row 1								
Row 2								
Row 3								
Row 4								
Row 5								
Row 6								
Row 7								

- 3.** Design a circuit free of static hazards to implement the function

$$f = \overline{B}\overline{C}\overline{D} + \overline{A}BC + B\overline{C}\overline{D}$$