

2019 Paper E2.1: Digital Electronics II

Answer ALL questions.

There are THREE questions on the paper.

Question ONE counts for 50% of the marks, other questions 25% each

Time allowed: 2 hours

<h1>SOLUTIONS</h1>

(For Examiners Only)

1. (a) This question tests student's ability to specify simple combinational circuit in Verilog, and their understanding of memory map and address decoding circuits.

(i)

```

module decoder (a, en_ram1, en_ram2, en_rom, en_io);
    input [17:0] a;
    output en_ram1, en_ram2, en_rom, en_io;

    assign en_ram1 = ~a[17] & ~a[16] & ~a[15];
    assign en_ram2 = ~a[17] & ~a[16] & a[15] & ~a[14];
    assign en_rom = ~a[17] & a[16];
    assign en_io = a[17] & a[16] & a[15] & a[14] & a[13] & a[12] & a[11] & a[9] & a[8] & a[7] & a[6] & a[5];
endmodule

```

[2]

(ii) The address ranges for the four spaces are:

RAM_1: 18'h00000 to 18'h07FFF


RAM_2: 18'h08000 to 18'h0BFFF

ROM_1: 18'h10000 to 18'h1FFFF

I/O: 18'h3FFE0 to 18'h3FFFF

[4]


(iii)

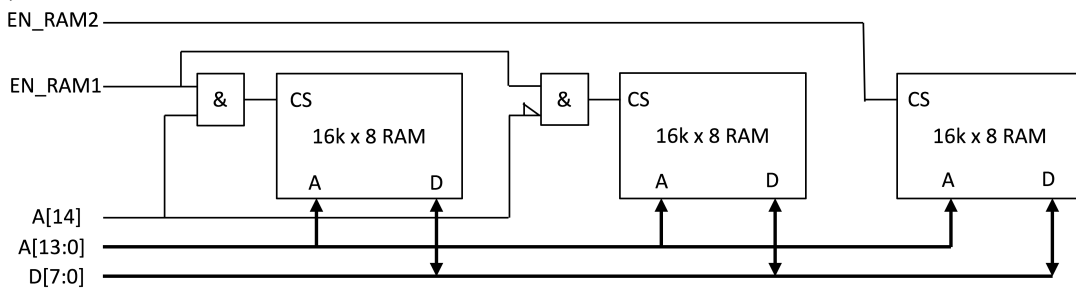

[4]

(b) This question tests students understanding of the use of ROM to implement FSM, and how to specify a FSM in terms of state diagram and Verilog HDL.

(i)

 

[5]

(ii)

```

module fsm (clk, in, out);
  input in, clk;
  output out;

  reg out;
  reg [1:0] state;
  parameter S0 = 2'b00, S1 = 2'b01, S2 = 2'b10, S3 = 2'b11;

  initial state = 2'b00;

  always @ (posedge clk)
  case (state)
    S0: if (in == 1'b1) state <= S1;
    S1: if (in == 1'b0) state <= S0;
        else state <= S2;
    S2: if (in == 1'b0) state <= S0;
        else state <= S3;
    S3: if (in == 1'b0) state <= S1;
        else state <= S2;
    default: state <= S0;
  endcase


  always @ (*)
  case (state)
    S0: out = 0;
    S1: out = 1;
    S2: out = 0;
    S3: out = 1;
    default: out = 0;
  endcase
endmodule

```

[5]

(c) This question tests student's ability to read Verilog code and their understanding of using LFSR to implement a pseudo-random binary sequence generator circuit.

(i)

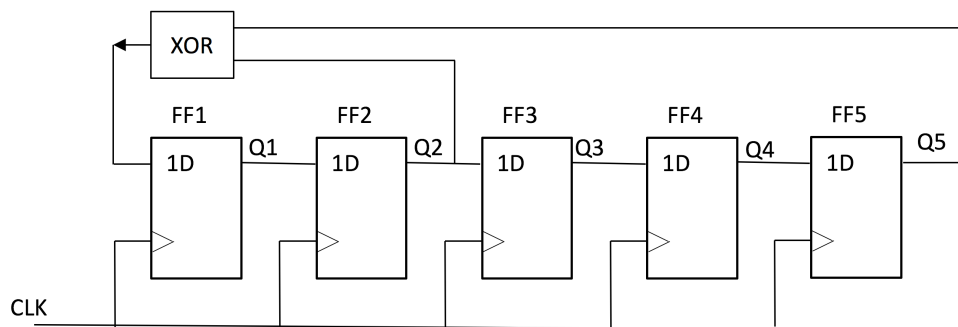

[4]

(ii)

Q5:Q1	Q5^Q2
0 0 0 0 1	0
0 0 0 1 0	1
0 0 1 0 1	0
0 1 0 1 0	1
1 0 1 0 1	1
0 1 0 1 1	1
1 0 1 1 1	0


[4]

(iii) The primitive polynomial implemented is:

$$1 + x^2 + x^5$$

[2]

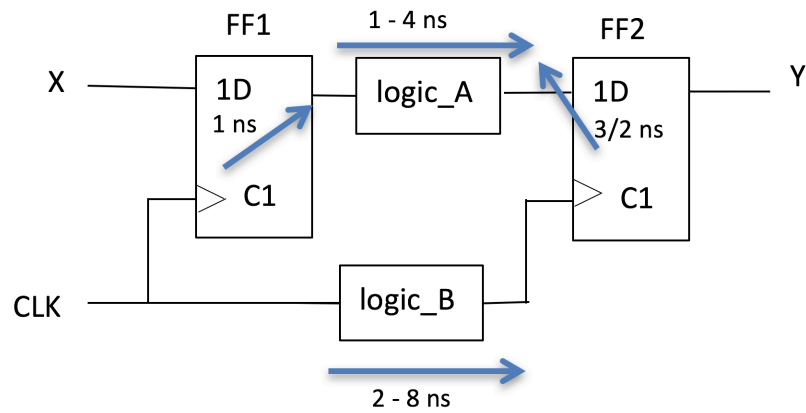- (d) This tests student's understanding of timing constraints in digital circuits.
 (i)



Setup time constraint:

$$tc-q(\max) + \text{logic_A}(\max) + t_{\text{setup}} < T + \text{logic_B}(\min)$$

[4]

(ii)

Given the various timing specification, we get:

$$1 + 4 + 3 \leq T + 2, \text{ therefore } T \geq 6\text{ns and } F_{\max}(\text{setup}) \leq 166.7 \text{ MHz}$$

[2]

(iii)

Hold time constraint:

$$T + tc-q(\min) + \text{logic_A}(\min) \geq \text{logic_B}(\max) + t_{\text{hold}}$$


$6 + 1 + 1 \geq 8 + 2$, which does not hold! Therefore there can be hold time violation

[4]

(e) This tests student's understanding of PWM DAC principles and implementation.

 - (i) Bookwork. This question tests student's understanding of PWM DAC which has been covered in the lectures.

Generate a triangular signal (in the form of a 12-bit counter) and compare the input value `data_in` to that of the counter value. Set `pwm_out` to be high if the counter value is lower than `data_in`, otherwise set it to low. The DAC output is the lowpass filtered version of the PWM signal.



[5]

- (ii)

```
module pwm_dac (clk, data_in, pwm_out);  
  
    input        clk;           // system clock  
    input [11:0] data_in;      // input data for conversion  
    output       pwm_out;      // PWM output  
  
    reg [11:0]   count;        // internal 12-bit counter  
    reg         pwm_out;  
  
    initial count = 12'b0;  
  
    always @ (posedge clk) begin  
        count <= count + 1'b1;  
        if (count > data_in)  
            pwm_out <= 1'b0;  
        else  
            pwm_out <= 1'b1;  
        end  
    end  
  
endmodule
```

[5]

2. This question tests student's ability to apply what they have learned in the Lab to a practical problem in sine and cosine generation.

(a) Dual-port ROM consists of two independent ports, with separate address and data buses. In this way, the contents of the ROM can be accessed by two sources at two addresses simultaneously. Since the ROM contains 1024 samples of a complete sinewave, we can produce a sinewave by sequentially reading the contents of the ROM, increasing the address value using a 10-bit counter at each counter clock cycle. The quadrature signal (i.e. the sinewave that is 90 degrees apart) can be produced by offsetting the address value by $\frac{1}{4}$ of a cycle or 256 location.

[10]

(b) The frequency of the sine and cosine signals is given by:

$$f_{sig} = f_{samp}/1024 = (50\text{MHz}/K) / 1024.$$

For f_{sig} to be as close to 10kHz as possible, we need f_{samp} to be 10.24MHz. Therefore the closest we can get to is to divide the 50MHz clock by 5.

Hence $K = 5$ and $N = 256$.

[5]

(c)

```

module quadrature_gen (CLK50, sine_sig, cosine_sig);
    input          CLK50;          // 50 MHz clock
    output [8:0]   sine_sig;       // sinewave signal
    output [8:0]   cosine_sig;    // cosinewave signal

    // ---- clock divider
    reg [2:0]      clk_ctr;        // count clock cycles
    reg           time_out;        // goes high for 1 cycle every 4 clk cycles
    initial       clk_ctr = 6'b0;
    parameter     tc = 4;         // count from 0 to 4
    always @ (posedge CLK50)
    begin
        if (clk_ctr==0) begin
            time_out <= 1'b1;
            clk_ctr <= tc;
        end
        else begin
            time_out <= 1'b0;
            clk_ctr <= clk_ctr + 1'b1;
        end
    end
    // ---- end of clock divider

    // ---- address counter ----

    reg [9:0]     address_a;       // address counter for sine_sig
    reg [9:0]     address_b;       // address counter for cosine_sig
    initial       address_a = 10'b0;

    always @ (posedge CLK50)
    begin
        if (time_out == 1'b1) begin
            address_a <= address_a + 1'b1;
            address_b <= address_a + 10'd256;
        end
    end


    ROM2port sine_rom (address_a, address_b, CLK50, sine_sig, cosines_sig);
endmodule

```

[10]

3. This question tests student's ability to design and code in Verilog HDL a reasonably complex FSM with a practical application.

(a)

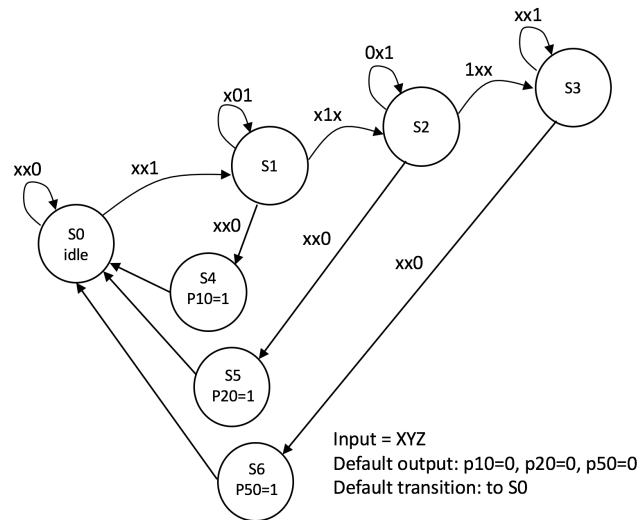

[15]

(b)

```

module fsm (clk, x,y,x, p10, p20, p50);
  input x,y,z, clk;
  output p10, p20, p50;

  reg p10, p20, p50;
  reg [6:0] state;
  parameter S0 = 7'd1, S1 = 7'd2, S2 = 7'd4, S3 = 7'd8;
  parameter S4 = 7'd16, S5 = 7'd32, S6 = 7'd64;

  initial state = S0;

  always @ (posedge clk)
  case (state)
  S0: if (z == 1'b1) state <= S1;
      else state <= S0;
  S1: if (y == 1'b1) state <= S2;
      else if (z == 1'b0) state <= S4;
      else if ((z==1'b1) && (y==1'b0)) state <= S1;
  S2: if (x == 1'b1) state <= S3;
      else if (z == 1'b0) state <= S5;
      else if ((z==1'b1) && (x==1'b0)) state <= S2;
  S3: if (z == 1'b1) state <= S3;
      else if (z == 1'b0) state <= S6;
  S4: state <= S0;
  S5: state <= S0;
  S6: state <= S0;
  default: state <= S0;
  endcase

  always @ (*)
  case (state)
  S4: p10 = 1;
  S5: p20 = 1;
  S6: p50 = 1;
  default: begin p10 = 0; p20 = 0; p50 = 0;end
  endcase
endmodule
  
```

[10]