

# Lecture 13

## Memory Interface

Peter Cheung  
Department of Electrical & Electronic Engineering  
Imperial College London



URL: [www.ee.imperial.ac.uk/pcheung/teaching/ee2\\_digital/](http://www.ee.imperial.ac.uk/pcheung/teaching/ee2_digital/)  
E-mail: [p.cheung@imperial.ac.uk](mailto:p.cheung@imperial.ac.uk)

## Lecture Objectives

---


- ◆ Explain how memory is connected to a microprocessor
- ◆ Describe the sequence of events in reading from and writing to a static RAM
- ◆ Different ways to use memory inside FPGAs
  - Register File
  - ROM and waveform generation
  - First-in-First-Out memory
- ◆ Memory resources inside Cyclone V FPGAs
- ◆ M9K memory block
- ◆ Library components in Quartus (IP Catalog)

Memory interfacing is an essential topic for digital system design. In fact the amount of silicon area devoted to memory in a typical digital embedded system or a computer system is substantial. For example, in a mobile phone, the number of transistors devoted to memory is many times more than those used for computation. For the second year course, I will only focus on interfacing to static memory, known as RAM (Random Access Memory) or ROM (Read-Only Memory). There are other types of memory such as dynamic memory (DRAM), Synchronous DRAM (SDRAM) and flash memory (Flash RAM) which will not be covered on this course.

In this lecture, we will consider the various types of storage (memory) that FPGAs allow us to implement. The major advantage of FPGAs is that it contains lots of small blocks of memory modules, which can either be used independently, or combined to form larger memory blocks. They also provide various configurations such as multi-port or registered input/output for data and address.

There are various useful references you can look up if you are interested to learn more about this. For the purpose of examination, the contents in this lecture and in the VERI experiment are sufficient.

## Simplified RAM Organization

 

- A typical memory has:
- ◆ N-bit address bus
    - This defines  $2^N$  memory locations
  - ◆ M-bit data bus
    - This defines the size of data word
  - ◆ Control signals to define read/write cycles,
    - Asynchronous memory – no clock in control
    - Synchronous memory – every action synchronised to a clock

A typical 8-bit microprocessor typically has

- ◆ A 16-bit address bus, A15:0
  - Can have up to  $2^{16}=65536$  memory locations
- ◆ An 8-bit data bus, D7:0 - Each data word in memory has  $2^8 = 256$  possible values
- ◆ In the RAM shown above uses 12-bit address and 16-bit data, i.e. 4096 locations of 16-bits each
- ◆ These are arranged as 256 x 256 rows of memory cells.  $4096 = 256 \text{ rows} \times 16 \text{ columns}$  as shown
- ◆ The address bus is therefore split into two components: 8-bit to specify which row, and 4-bit to select the correct column.

This slide shows a typical organisation inside a RAM chip. Memory cells are usually organised in the form of a 2-D array of RAM cells. These are accessed first in a row, then in a column. The address bus is divided into two components, the row address (8-bit in the example here) and the column address (4-bit in this example). There is a decode to translate the 8-bit row address into one-hot outputs in order to specify which row is being accessed. Only ONE ROW will be enable at any one time (hence one-hot).


The second part of the address (normally the less significant bits) is used as select signal into the output mux. This is because when memory is accessed, they are normally read or written in a sequence. Using LSB for column decoding means that one stays on the same row of memory as much as possible. Staying in the same row uses significantly lower energy than switching between rows in memory accesses.

In the example here, the 4-bit column address is used to select from a 16-to-1 mux to provide the correct location in memory to access. There are 16 identical blocks, each providing one-bit of the data output.

The output enable signal OE allows the selected data value be driven on the data bus.

## RAM: Read/Write Memory

### 8k × 8 Static RAM

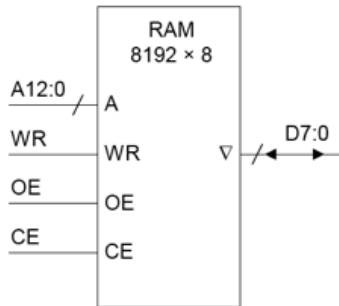

CE	OE	WR	D0:7	Action
0	?	?	Hi Z	Disabled
1	0	0	Hi Z	Idle
1	1	0	Out	Read
1	?	1	In	Write

Hi Z = High impedance

Static RAM: Data stored in bistable latches

Dynamic RAM: Data stored in charged capacitors: retained for only 2ms. Less circuitry ⇒ denser ⇒ cheaper.

∇ Tri-state output: Low, High or Off (High Impedance). Allows outputs from several chips to be connected; Designer must ensure only one is enabled at a time.

CE Chip Enable: disabling chip cuts power by 80%.

OE Output Enable: Turns the tri-state outputs on/off.

A12:0 Address: selects one of the  $2^{13}$  8-bit locations.

WR Write: stores new data in selected location



D7:0 Data in for write cycles or out for read cycles.

Here is a 8K x 8 static RAM chip and its associated digital signals. The 13-bit address bus A12:0, the 8-bit data bus D7:0 are mandatory. There are three more control signals: Output Enable OE which we have seen before, Chip Enable CE which is used to address or select this particular memory chip (hence the name), and finally the WRITE ENABLE signal WE, which, when set high, indicates that you are writing to the RAM chip, and is normally low (i.e. reading).


Note that the data bus has an inverted triangle sign, indicating that this is a **tri-state bus**. This means that the pin could be an input pin, output pin, or an open-circuit pin (i.e. not connected to anything – we call the signal *floating*). The truth table shown here specifies the behaviour of the data bus in one of the three possible states.
  
## 8k x 8 Static RAM

- The 64k memory cells are arranged in a square array:



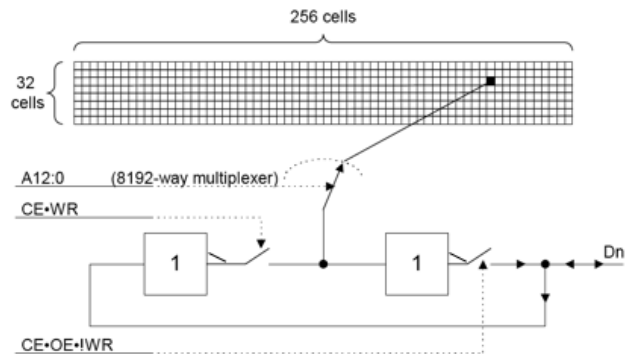- For each output bit, an 8192-way multiplexer selects one of the cells. The control signals, **OE**, **CE** and **WR** determine how it connects to the output pin via buffers:



- Occasionally DIN and DOUT are separate but  $\Rightarrow$  more pins

For a 8k x 8 RAM, there are 8 data bits, and therefore 8 separate 1-bit arrays. Let us assume that each data bit array is organised as a 256 rows x 32 column (=8192) of memory cells. Eight such array are placed next to each other to form the 8 data bits required. This makes the memory chip roughly square (which is generally desirable).


You can think of the row decoder and the column selector driven by the 13-bit address as a 8192 way multiplexer, selecting one of 8192 cells organised as 256 x 32, to be accessed.

The simplified circuit of each memory cell shown here consists of two inverters and two switches is a schematic of the read-write circuit. When reading from the cell, A12:0 select one of 8192 cells to route its signal via the right inverter to Dn. Now Dn is an output pin. This only happens if  $CE \cdot OE \cdot \overline{WR} = 1$  (i.e. asserting CE and OE, but not asserting WR).

When writing to the memory cell, the right switch is open, Dn is an input pin driving the left hand inverter and the output switch from that inverter is closed because both CE and WR are asserted.

Some memory chips have separate Din and Dout pins, but that's expensive on pins and is not particularly common nowadays.


## Microprocessor ↔ Memory Interface

 

- ◆ During each memory cycle:
- ◆ A15:0 selects one of  $2^{16}$  possible memory locations
- ◆ D7:0 transfer one word (8 bits) of information either to the memory (write) or to the microprocessor (read).
- ◆ D7:0 connections to the microprocessor are tri-state ( $\nabla$ ): they can be:
  - “logic 0”, “logic 1” or “high impedance” (inputs)
- ◆ The control signals tell the memory what to do and when to do it.

Here is a slide showing a generic interfacing between a microprocessor and a memory sub-system. We assume that we use a 16-bit address bus and an 8-bit data bus. The control signals go between the two to control the transfer of information, and is in general governed by the microprocessor which acts as the “**master**”.

## Microprocessor Memory Map

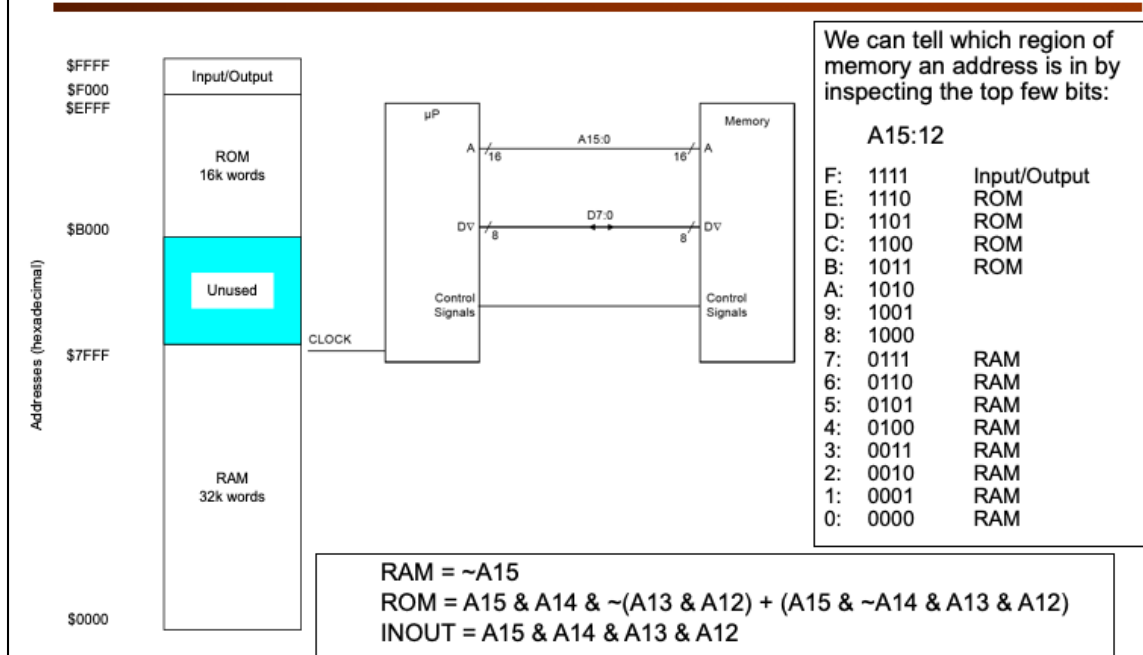


While we show memory as a block, in a real system, the memory address space is divided into many different partitions. Here we use '\$' (instead of 16'hxxxx) to indicate that the addresses are hexadecimal numbers. The left hand diagram shows the memory being partitioned into 32k of RAM, 16k of ROM and 4k space for input/output devices.

A design needs to take **the upper bits of the address bus** and decode these bits into **enable signals** for the three different partitions. In this case, we can see that we only need to decode A15:12 according to the Boolean equations shown here. What about A11:0? These are the address bits used inside the RAM, ROM and input/output modules to select particular locations.

## Memory Chip Selection

- ◆ Each memory circuit has a “chip enable” input (CE)
- ◆ The “Decoder” uses the top few address bits to decide which memory circuit should be enabled. Each one is enabled only for the correct address range:
  - RAM =  $\sim A_{15}$
  - ROM =  $A_{15} \& A_{14} \& \sim(A_{13} \& A_{12}) + (A_{15} \& \sim A_{14} \& A_{13} \& A_{12})$
  - INOUTx =  $A_{15} \& A_{14} \& A_{13} \& A_{12} \& \sim A_{11} \& A_{10} \& \sim A_9 \& A_8 \& \sim A_7 \& A_6 \& A_5 \& A_4 \& \sim A_3 \& A_2$
- ◆ INOUTx responds to addresses: \$F574 to \$F577  
other I/O circuits will have different addresses
- ◆ Low  $n$  address bits select one of  $2^n$  locations within each memory circuit (value of  $n$  depends on memory size)

Addr Range	Usage
\$F578 - \$FFFF	Not used
<b>\$F574 - \$F577</b>	<b>INOUTx</b>
\$F000 - \$F573	Not used
\$B000 - \$EFFF	16k ROM
\$8000 - \$AFFF	Not used
\$0000 - \$7FFF	32k RAM

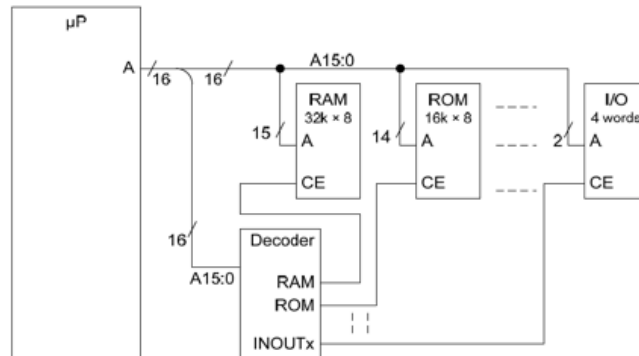

Selecting which memory sub-system and therefore which memory chip to enable is the job of the address decoder circuit. This circuit takes the upper bits of the address bus, and produce enable signals for RAM, ROM and INOUTx for a particular I/O device.

In the previous slide, we showed that the input/output occupies 4k of memory space. This is uncommon. Typically an I/O device may take up, say, 4 memory locations.


In this example, INOUTx occupies only the address space \$F574 - \$F577, i.e. 4 locations. Therefore we need to decode lots of address signals: A15:2.

Can you work out the Boolean equations for the address decoder shown here?

The ROM CE signal is another challenge. The ROM is enable if the address A15:A12 falls between the range 4'b1011 and 4'b1110. You should prove for yourself that the Boolean equation to decode the address for the ROM is as shown here.



## Memory Interface Control Signals

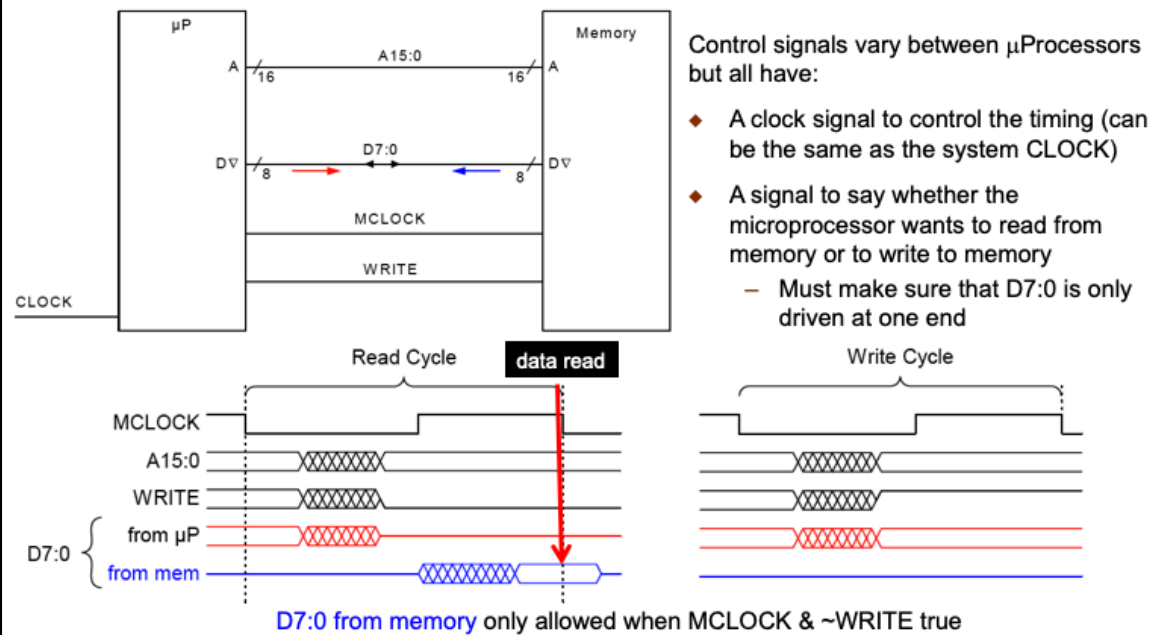

Control signals vary between  $\mu$ Processors but all have:

- ◆ A clock signal to control the timing (can be the same as the system CLOCK)
- ◆ A signal to say whether the microprocessor wants to read from memory or to write to memory
  - Must make sure that D7:0 is only driven at one end


In addition to the address decoder circuit, we need to provide the control signals from the microprocessor to the memory chips. Here we assume there exists at least two control signals from the microprocessor: MCLOCK which is memory clock signal (which may be different from the system clock signal CLOCK), and a WRITE signal, which is high when writing to memory, but low otherwise.

The interaction between the microprocessor and memory can be separated into two types of transactions: a **Read Cycle** and a **Write Cycle**.

During Read Cycle, the microprocessor asserts the address A15:0 and the control signals MCLOCK and WRITE. Shortly after the beginning of the Read Cycle, the microprocessor must STOP driving the data bus D7:0, and on the second half of the cycle, we assume that memory will then provide the data for the microprocessor to read. Reading is actually performed at the end of the Read Cycle, on the falling edge of MCLOCK. Note that I use red colour to indicate the action of the microprocessor on the data bus, and blue colour for the action by the memory chip on the data bus.

During a Write Cycle, the microprocessor drives everything. Writing also occurs on the falling edge of MCLOCK in our case. (Note that other system may have a different protocol than the one shown here.)

## Memory Circuit Control Signals

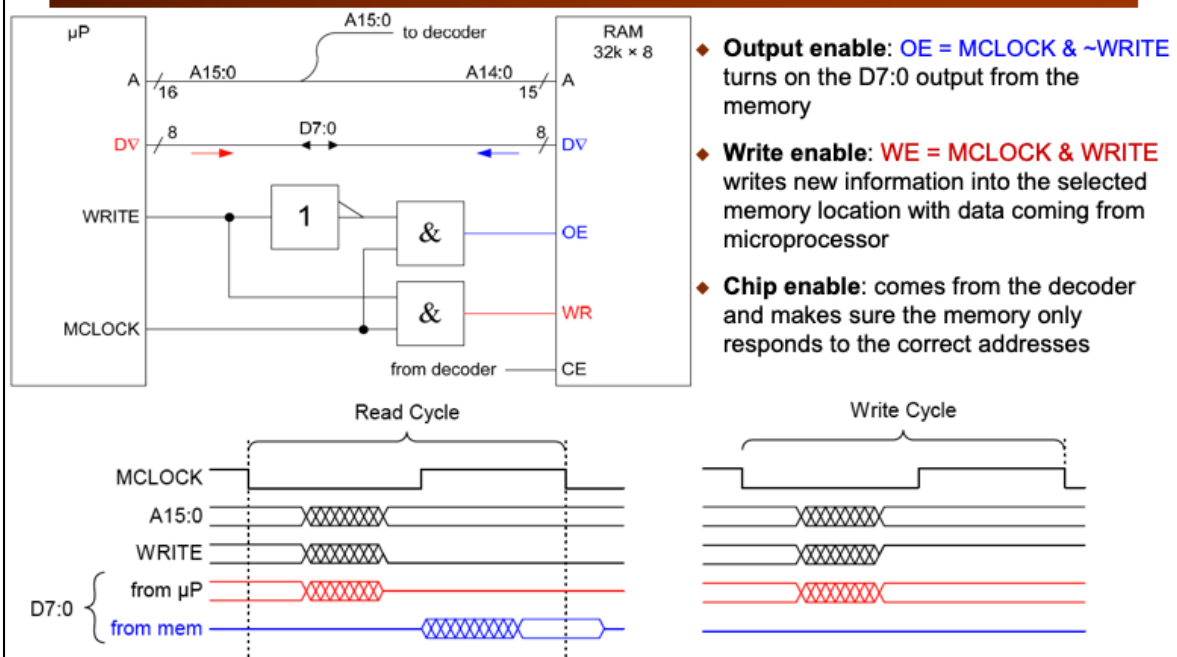

PYKC 25 Nov 2019


E2.1 Digital Electronics

Lecture 13 Slide 10

This slide shows the control circuit used to interface the microprocessor to the 32k x 8 RAM chip.

Chip Enable (CE) is driven by the output from the address decoder, which we have considered in an earlier slide. Remember the colour code I am using: RED driven by the microprocessor, BLUE driven by memory.

## Memory Read Cycle

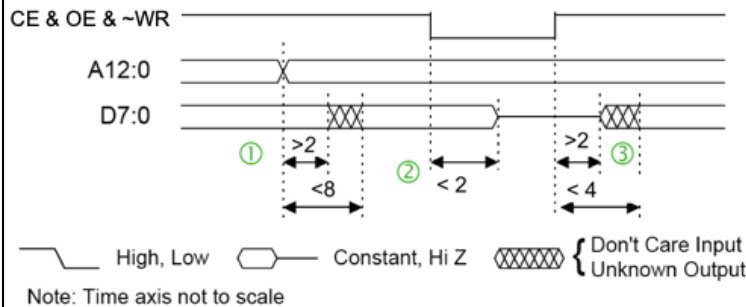

A read cycle happens when CE&OE&~WR is true.

① If A12:0 changes, D7:0 remains for at least 2 ns and goes to new value within 8 ns. Rubbish in between even if new and old locations contain the same value.

② If a read cycle ends due to OE going low, the outputs go Hi-Z within 2 ns

③ If a read cycle starts due to OE going high, D7:0 stays Hi-Z for at least another 2 ns and the selected word appears within 4ns

- ◆ This diagram shows the timing constraints on memory during a read cycle.
- ◆ All timing shown here are only indicative. Another memory device would have totally different timing specifications.

- ◆ You can use CE instead of OE but it is slower: 10 ns to turn off and 15 ns to turn on (in parentheses on timing diagram).
- ◆ When reading data, the propagation delay to the D7:0 outputs is called the RAM's **access time**: 8 ns from A12:0 and 4 ns from OE.

PYKC 25 Nov 2019

E2.1 Digital Electronics

Lecture 13 Slide 11


Let us now consider the timing constraints imposed by memory during a Read Cycle. First thing that happens would be a valid address A12:0 being presented at (1). As a typical example for memory timing, it is assumed that data D7:0 holds for at least 2ns before changing, but it is guaranteed to provide the correct D7:0 at the new address in 8ns or earlier. This is address to data ACCESS TIME for this RAM. Note that even if new and old location have the same data value, there will be a period when D7:0 contains rubbish – beware. Also note that memory is providing data to be read by the microprocessor, CE, OE and ~WR must all be asserted (i.e. '1').

At (2), memory is deselected or output not enabled, or we are no longer reading from memory. D7:0 again is guaranteed to go high-impedance after 2ns.

Some time later, if memory is selected again at (3), it takes 2ns before memory starts to drive D7:0, but guaranteed to provide correct data after 4ns.

The most important delay here is that from address or OE to data. They are called address access time and output enable access time. Usually address access timing is longer (here it is 8ns) than OE access time (4ns) because output enable simply enables the output multiplex stage, which is close to the data output pin. Address access involves decoding the address values to produce the one-hot row select signal (known as the WORD line), and then the row of memory cells needs to present its data to the column multiplexer. Selecting which row to access is generally a much slower process than the column multiplexer.

## Memory Write Cycle

 

- ◆ Timing specifications that end on an output are guarantees from the chip manufacturer (shown in **black**).
- ◆ Timing specifications that end on an input are requirements that the designer must meet (shown in **blue**).

A write cycle happens whenever CE&WR is true.


- ① CE&WR must go high for at least 10 ns.
- ② To avoid writing to the wrong locations, the address, A12:0 must remain constant for at least 2 ns at both ends of the write pulse.
- ③ Input data D0:7 only matters at the *end* of the write pulse. Setup & hold times of 4 ns & 1 ns define a window within which data must not change.
- ④ When CE&OE&~WR goes high, the memory reverts to read mode. The input data must be removed from D7:0 before this happens.

Here is the timing for the **Write Cycle**. Remember that Write Cycle timing is particularly important – any timing error here could result in corrupting the contents store in RAM.

- (1)The write pulse is signified by CE and WR both being asserted (i.e. TRUE). There is usually a minimum period specified – here 10ns. Also as soon as the WR is asserted, WR = 1 and D7:0 must go high-impedance within 2ns (i.e. memory no longer driving the data bus).
- (2)The address A12:0 must be stable at least 2ns before the write pulse, and it must hold for another 2ns after the write pulse.
- (3)The data is written to memory on the falling edge of the write pulse. The setup and hold time is 4ns and 1ns respectively.
- (4)This is when the Write Cycle finishes, and we go back to Read Cycle. Expect D7:0 stays high impedance for at least 2ns.

## Register File

### ◆ Register file from microprocessor

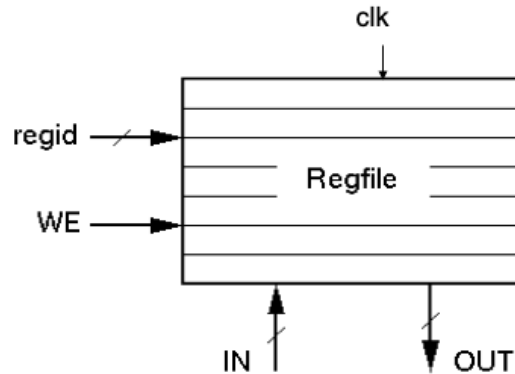

regid = register identifier (address of word in memory)

$\text{sizeof}(\text{regid}) = \log_2(\# \text{ of reg})$

WE = write enable

The simplest form of storage is a register file. All microprocessors have register files, which are known as “registers” in the architectural context.


Register files are fast, large and flexible. They are generally used to store temporary data for easy access by the ALU or floating point unit of a microprocessor, or for computational engine of an application specific digital system.

On the FPGA, register files are often implemented with the D-FF's in the Adaptive Logic Modules (ALMs). Each ALM has two D-FFs. Therefore a 32-bit register will take up 16 ALMs. Alternatively one could also use the static memory blocks for this purpose.


## Register File Internals

- ◆ For read operations, functionally the regfile is equivalent to a 2-D array of flipflops with tristate outputs on each

- MUX, but distributed
- Unary control

 


- ◆ Cell with added write logic:

 

The circuit of a register file is simple – it consists of arrays of D-FFs, which can be disabled (and output becomes high impedance). The register select signals sel\_reg0, sel\_reg1 etc. enable the correct register to put the data on the data line (called bit line here). The read/write control signal WE is used to determine if you are reading or writing to the register.


## Regid (address) Decoding

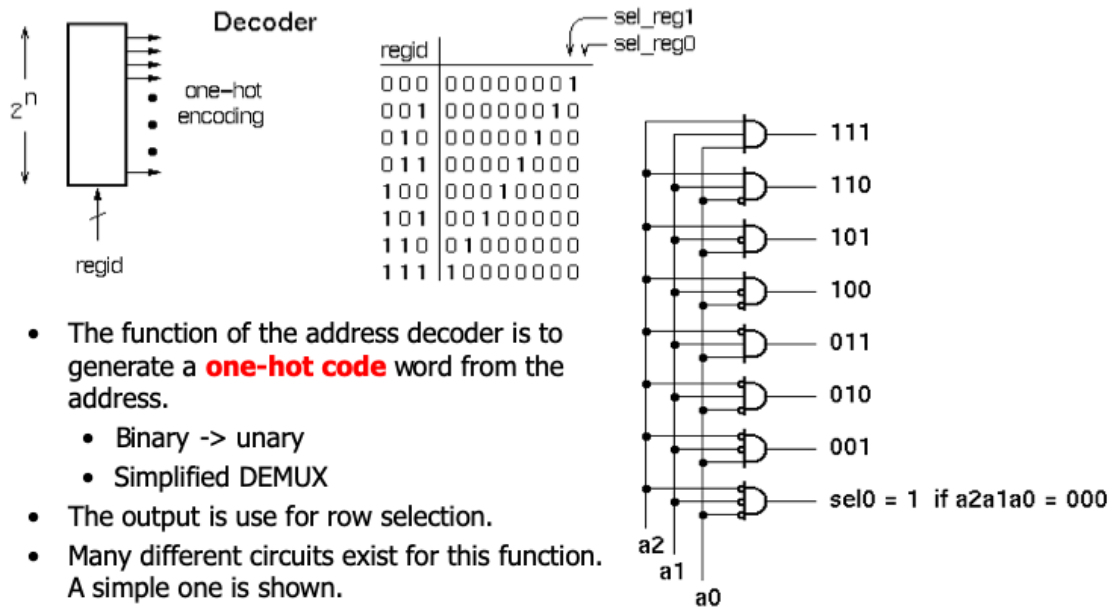

The register identification (regid) determines which register you are trying to access. This is achieved through a standard decoder, which generate a one-hot code word to select the appropriate register to access.
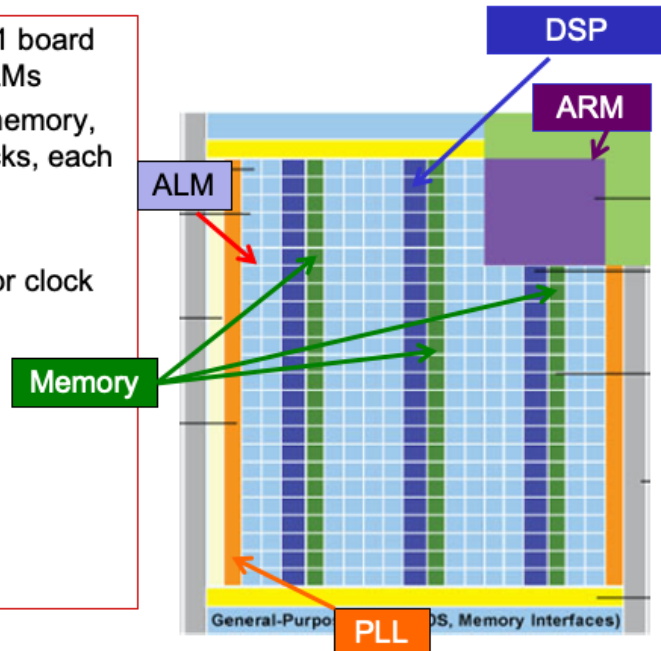
## Cyclone V FPGA resources

- ◆ The Cyclone V used in the DE1 board (**5CSEMA5F31C6**) has 31k ALMs
- ◆ It also contains 4.45 Mbits of memory, organised as 397 memory blocks, each with 10 kbits of storage
- ◆ It has 87 DSP Blocks (later)
- ◆ It has 16 phase-locked loops for clock generation (later)



PYKC 25 Nov 2019

E2.1 Digital Electronics

Lecture 13 Slide 16

Now let us turn to the Cyclone V FPGA. The FPGA has many different type of resources in addition to Adaptive Logic Modules (ALMs). These are: memory blocks, Digital Signal Processing (DSP) units, phase-locked loops and input/output pads. In addition, there is a dual-core ARM processor and its associated bus interface circuit (shown in light green).

Here we focus on memory. In the C5-SE-A5 series, which is the one we use in the DE1 board, there are near 400 separate memory blocks, each with 10k bits of storage. Together with the ALMs, there is 4.45 Mbits of flexible memory storage available to the designer.



## Cyclone V Embedded Memory

- ◆ Each 10kbit memory block (M10K) can be configured with different data width from 1 bit to 40 bit wide
- ◆ It also has multiple operating modes (which is user configurable), of which we will focus on the following only: single-port, shift-register, ROM, FIFO

- Single-port
- Simple dual-port
- True dual-port
- Shift-register
- ROM
- FIFO

Memory Block	Depth (bits)	Programmable Width
MLAB	32	x16, x18, or x20
M10K	256	x40 or x32
	512	x20 or x16
	1K	x10 or x8
	2K	x5 or x4
	4K	x2
	8K	x1

PYKC 25 Nov 2019

E2.1 Digital Electronics

Lecture 13 Slide 17


Each of these blocks (known as M10K) can be configured with different depth and data width as shown in the table above.

Even more importantly, they can also be configured to act as conventional single-port memory, or simple dual-port with one port for read and one port for write.

Further, they can be made to be true dual-port, both ports being read/write ports, or as a shift register, a ROM or a first-in-first-out buffer (FIFO).
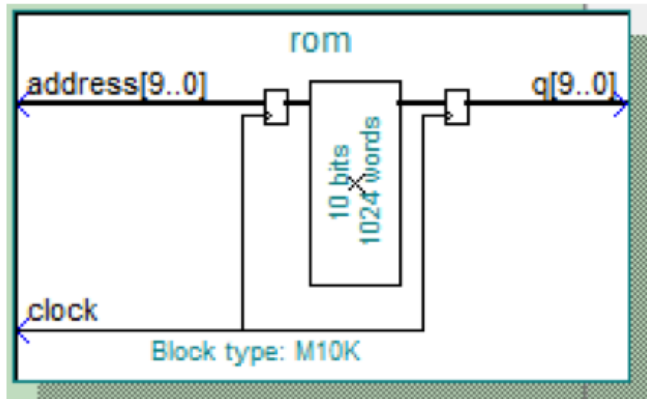
## Intialization of ROM Contents (1k x 8)

- ◆ Create ROM and initialize its content in a .mif file:



```
-- ROM Initialization file
WIDTH = 10;
DEPTH = 1024;
ADDRESS_RADIX = HEX;
DATA_RADIX = HEX;
CONTENT
BEGIN
    0 : 200;
    1 : 203;
    2 : 206;
    3 : 209;
    4 : 20C;
    5 : 20F;
    6 : 212;
    7 : 215;
    8 : 219;
    9 : 21C;
    A : 21F;
```

As you have seen in the VERI experiment, if the memory block is a ROM (or even as a RAM), its content can be configured via a memory initialization file .mif. The format of the file is shown here. Typing the contents of a 1024 ROM module by hand is silly and impractical. I wrote two versions of a simple programme to generate this .mif file, one in Matlab and one in Python. Below is the code for the Matlab version.

The ROM is produced using the IP Catalog tool. Here is a 1024 x 10 bit ROM generated with all input and output registered and synchronised with the clock signal

```
% Purpose:  MATLAB script to produce contents of a ROM that stores
%           one cycle of sinewave
% Inputs:   None
% Outputs:  rom_data.mif file
% Author:   Peter Cheung
% Version:  1.0
% Date:     20 Nov 2011

DEPTH = 1024;    % Size of ROM
WIDTH = 10;     % Size of data in bits
OUTMAX = 2^WIDTH - 1; % Amplitude of sinewave

filename = 'rom_data.mif';
fid = fopen(filename,'w');

fprintf(fid,'-- ROM Initialization file\n');
fprintf(fid,'WIDTH = %d;\n',WIDTH);
fprintf(fid,'DEPTH = %d;\n',DEPTH);
fprintf(fid,'ADDRESS_RADIX = HEX;\n');
fprintf(fid,'DATA_RADIX = HEX;\n');
fprintf(fid,'CONTENT\nBEGIN\n');


for address = 0:1023
    angle = (address*2*pi)/DEPTH;
    sine_value = sin(angle);
    data = (sine_value*0.5*OUTMAX) + OUTMAX*0.5;

    fprintf(fid,'%4X : %4X;\n',address,int16(data));
end

fprintf(fid,'END\n');
fclose(fid);
disp('Finished');
```
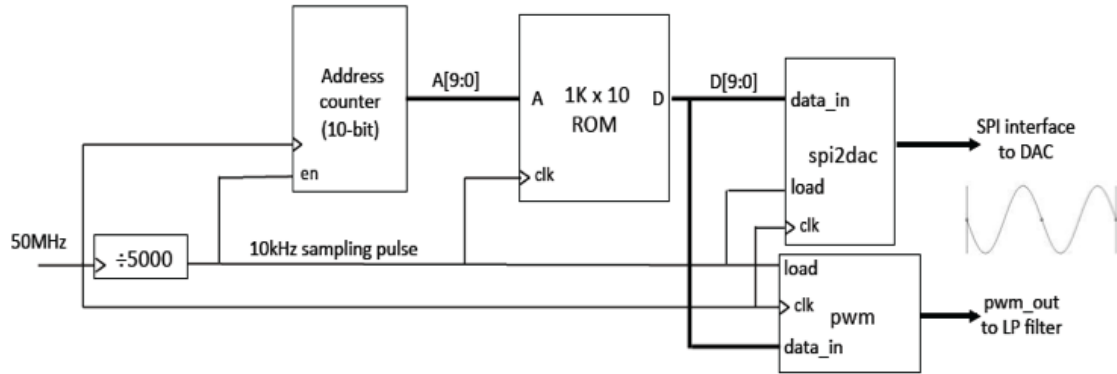
## Sinewave Generation


- ◆ Generate any waveform or function  $y = F(x)$  using table lookup
- ◆ Phase counter increment phase whenever *step* goes high
- ◆ ROM stores one cycle of sinewave to produce  $F(x)$
- ◆ Digital-to-Analogue convert and the PWM DAC generate the analogue outputs on L & R channels



In the experiment, you have already implemented a sine wave generator using the ROM to store one cycle of a sine wave. The counter is used to advance the phase of the sine wave, which is specified as the address  $X$  of the ROM. The content of the ROM,  $y = F(x)$  is the content of the ROM and is the generated wave form. Instead of storing a sine wave, you can easily store any other signal (such as a voice or music segment).

In order to implement a variable frequency sinewave, you could modify the address counter so that it goes up not only by 1 count for each clock cycle, but by  $N$ . For example if  $N$  is 2, then the address counter will skip every other sample in the ROM and therefore the generated sinewave will be at twice the signal frequency.

## Single-port Memory (M10K as RAM)

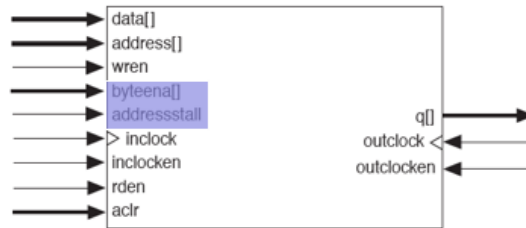


Signal name	meaning
data[ ]	Write data port
address[ ]	Read/write address port
q[ ]	Read data port
wren	Write enable
rden	Read enable
aclr	Asynchronous clear
inclock	Clock signal to control writing
outclock	Clock signal to control reading

Here is a generated single-port memory with ALL possible signals included. The meaning of all the signals are self explanatory.
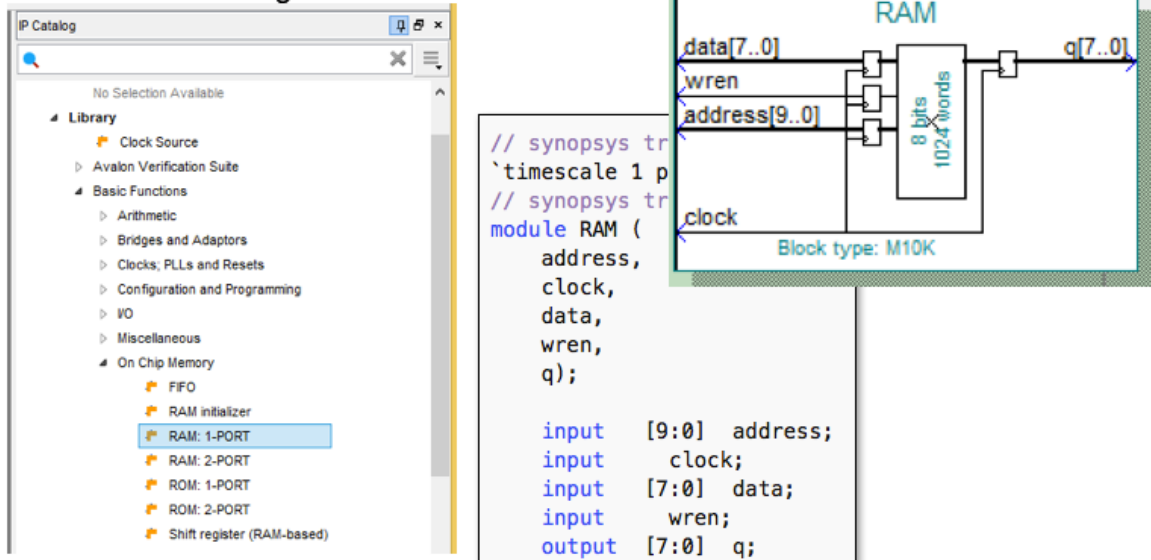
## How to use M10K memory block? (1k x 8)

- ◆ Use IP Catalog manager tool in Quartus to produce memory of the correct configuration:



The image shows the IP Catalog tool interface. On the left, the 'Library' pane is expanded to 'On Chip Memory', where 'RAM: 1-PORT' is selected. On the right, a circuit diagram shows a RAM block with inputs for data[7..0], wren, and address[9..0], and an output q[7..0]. The block is labeled 'Block type: M10K'. Below the diagram, a Verilog code block defines the RAM module:

```
// synopsys tr
`timescale 1 p
// synopsys tr
module RAM (
    address,
    clock,
    data,
    wren,
    q);

    input    [9:0] address;
    input    clock;
    input    [7:0] data;
    input    wren;
    output   [7:0] q;
```


PYKC 25 Nov 2019

E2.1 Digital Electronics


Lecture 13 Slide 21

Here is an example of using the MegaWizard manager tool in Quartus. We are producing a 1-port RAM with 1024 x 8, all signals are clocked. The generator produces a sample header file (a template) which defines the interface signal to the generated block. Remember you must tick the Verilog HDL radio button.
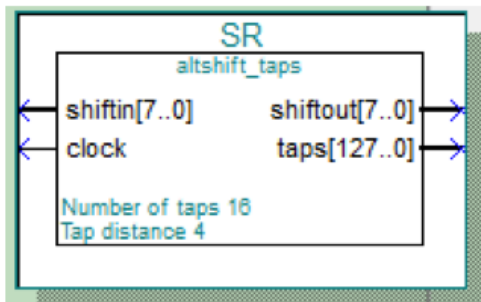
## M10K Memory as Shift Register (8-bit 16 stages)



 
```
module SR (  
    clock,  
    shiftin,  
    shiftout,  
    taps);  
  
    input    clock;  
    input   [7:0] shiftin;  
    output  [7:0] shiftout;  
    output  [127:0] taps;
```



You can also configure the M9K memory block as a shift register. Here is an 8-bit 16 stage SR. In addition, it provides “tap” outputs for every stage, i.e.  $16 \times 8 = 128$  output signals. This is very useful to implement FIR filter or perform time domain convolution.
 
## First-in-first-out (FIFO) Memory


- ◆ Used to implement *queues*.
- ◆ These find common use in computers and communication circuits.
- ◆ Generally, used for rate matching data producer and consumer:
- ◆ Producer can perform many writes without consumer performing any reads (or vice versa). However, because of finite buffer size, on average, need equal number of reads and writes.
- ◆ Typical uses:



- interfacing I/O devices. Example network interface. Data bursts from network, then processor bursts to memory buffer (or reads one word at a time from interface). Operations not synchronized.
- Example: Audio output. Processor produces output samples in bursts (during process swap-in time). Audio DAC clocks it out at constant sample rate.


In the Part IV of the VERI experiment, you will be using a FIFO to implement an echo synthesizer. The action of a FIFO is shown in the diagram above.

## FIFO Interfaces

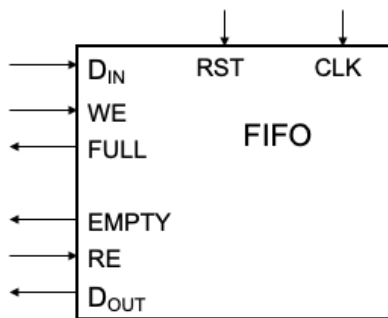


- ◆ After write or read operation, FULL and EMPTY indicate status of buffer.
- ◆ Used by external logic to control own reading from or writing to the buffer.
- ◆ FIFO resets to EMPTY state.

 
- ◆ Address pointers are used internally to keep next write position and next read position into a dual-port memory.



 - ◆ If pointers equal after write  $\Rightarrow$  FULL:



 
- ◆ If pointers equal after read  $\Rightarrow$  EMPTY:



Here is a generic block diagram of a FIFO with its typical interface signals. FIFO is a form of queue. Internally there typically two counters, one keeping track of the read address (or read pointer) and another counter keeping track of the write address (write pointer). There needs to be status signals such as FULL, which is asserted if the FIFO is completely filled and writing any more words to it will destroy stored data, or EMPTY, which signifies that there are no data left to read.



## M10K Memory as FIFO (8-bit x 32 word)

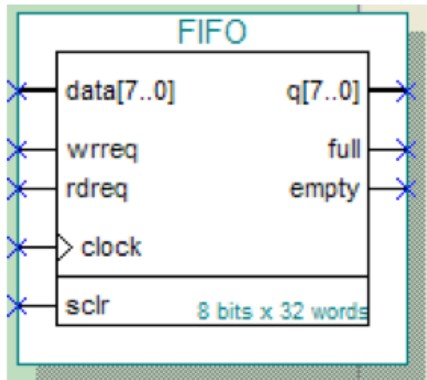

```
module FIFO (  
    clock,  
    data,  
    rdreq,  
    sclr,  
    wrreq,  
    empty,  
    full,  
    q);  
  
    input    clock;  
    input   [7:0] data;  
    input   rdreq;  
    input   sclr;  
    input   wrreq;  
    output  empty;  
    output  full;  
    output  [7:0] q;  
  
endmodule
```

FIFO can be generated using the IP Catalog manager tool. Here is an example of a 32 word x 8 bit FIFO.