

## Problem Class 5

### Timing Constraints (Problem Sheet 4)


Peter Cheung  
Department of Electrical & Electronic Engineering  
Imperial College London

URL: [www.ee.imperial.ac.uk/pcheung/teaching/ee2\\_digital/](http://www.ee.imperial.ac.uk/pcheung/teaching/ee2_digital/)  
E-mail: [p.cheung@imperial.ac.uk](mailto:p.cheung@imperial.ac.uk)
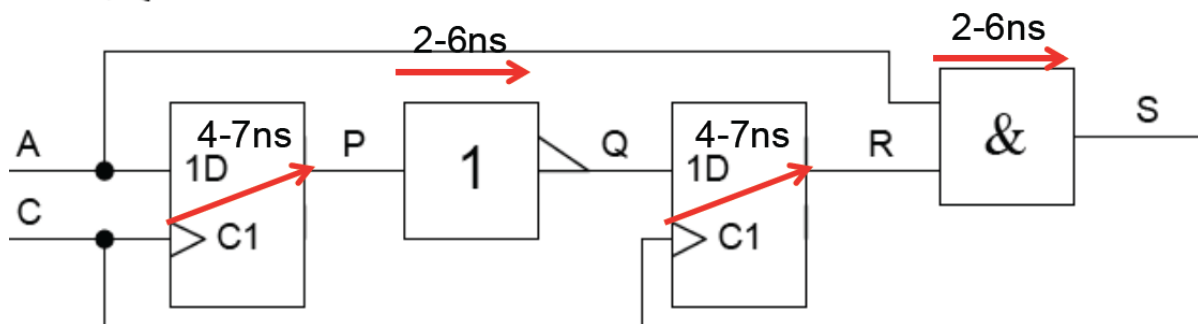
### Problem 1: Test yourself (not in tutorial sheet)


In the circuit below the propagation delay of the flipflops may vary between 4 and 7 ns while the propagation delay of the gates may vary between 2 and 6 ns.

Calculate the minimum and the maximum propagation delays from each of A and C to each of P, Q and R and S.


 
## Solution 1: Test yourself

Calculate the minimum and the maximum propagation delays from each of A and C to each of P, Q and R and S.




This is a trick question: there is no propagation delay between A and any of P, Q or R since a transition in A does not directly cause any of these other signals to change. The min and max delays from A to S are 2 and 6 ns. Of course if R happens to be low, there is no propagation delay between A and S either.

The min and max delays from C to P, Q, R and S are 4 and 7, 6 and 13, 4 and 7, and 6 and 13 ns respectively. The important point to realise is that since a transition at Q does not directly cause R to change, it follows that there is no delay path through both flipflops. The expression for a propagation delay **never** involves more than one flipflop delay.

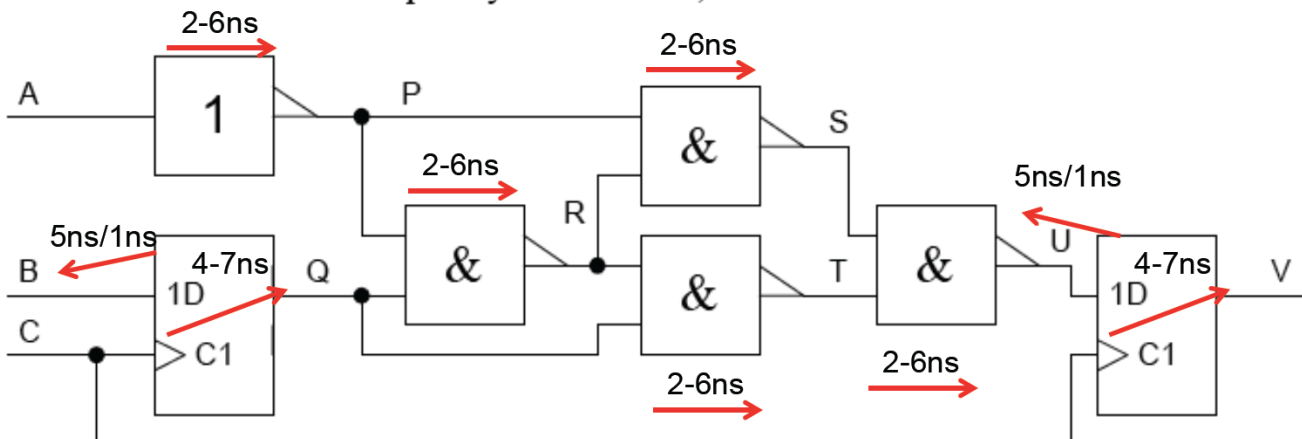
## Problem 2: Explain it (Not in tutorial sheet)

In the circuit below the setup and hold times of the flipflops are 5 ns and 1 ns respectively. The propagation delay of the flipflops may vary between 4 and 7 ns while the propagation delay of the gates may vary between 2 and 6 ns.

Calculate the minimum and the maximum propagation delays between C and U. Hence calculate the maximum frequency of the clock, C.



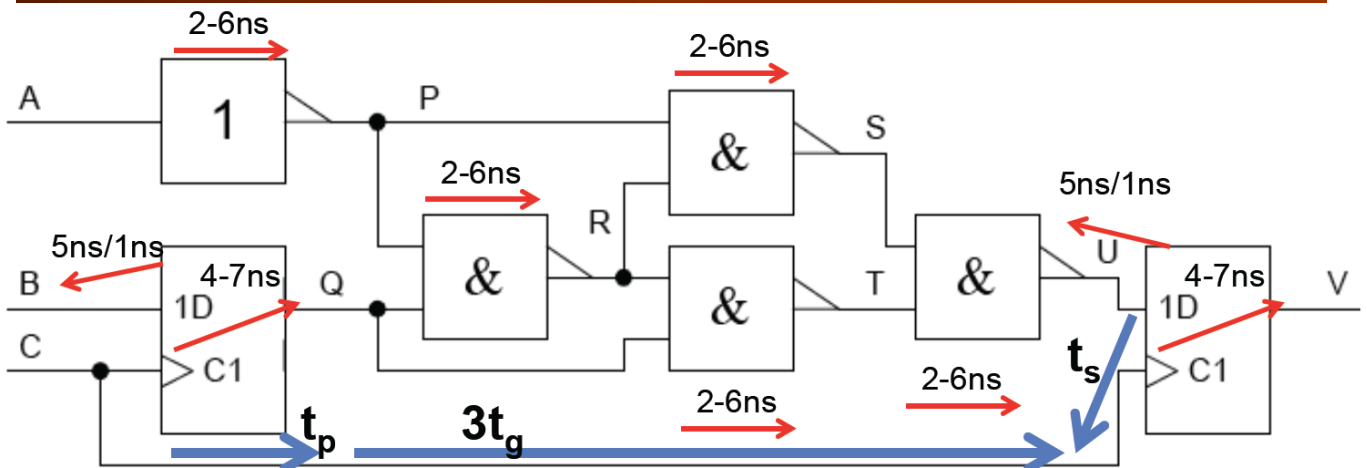
## Solution 2: Explain it – Setup requirement



The longest path from C to U passes through the flipflop and then through three gates: this gives a maximum propagation delay of 25 ns. This happens when  $A=0 \Rightarrow P=1 \Rightarrow R=!Q \Rightarrow T=1 \Rightarrow U=!S=R=!Q$ . We therefore use  $3t_g$  in the setup inequality below.

$$\text{Setup: } t_p + 3t_g + t_s < T \Rightarrow T > 7 + 3 \times 6 + 5 = 30 \text{ ns} \Rightarrow f < 33 \text{ MHz}$$
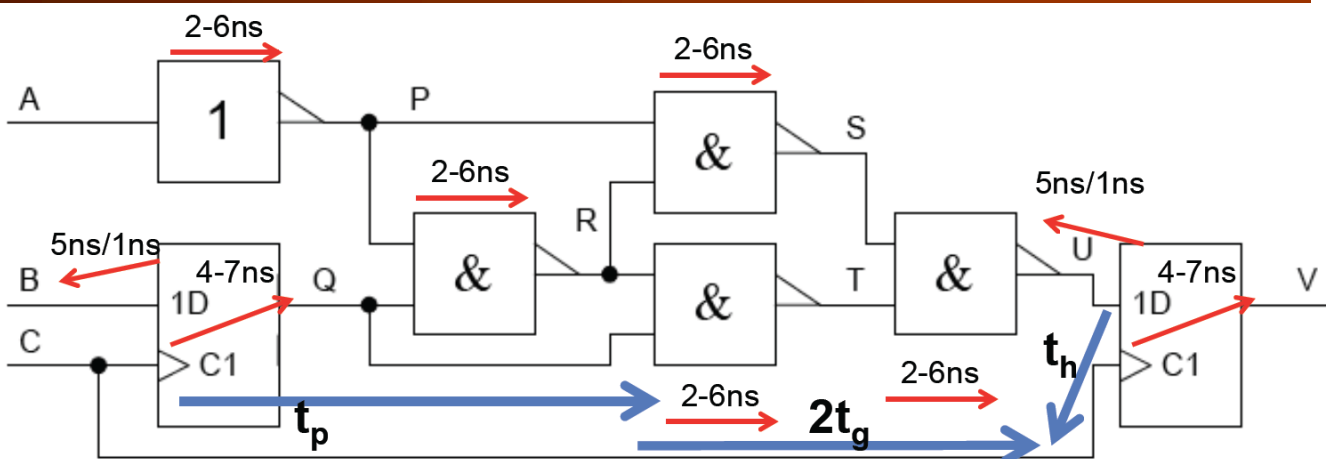
## Solution 2: Explain it – hold requirement




The shortest path from C to U passes through the flipflop and then through two gates: this gives a minimum propagation delay of 8 ns. This happens when  $A=1 \Rightarrow P=0 \Rightarrow R=S=1 \Rightarrow U=!T=Q$ . We therefore use  $2t_g$  in the hold inequality below.

$$\text{Hold: } t_h < t_p + 2t_g \Rightarrow 1 < 4 + 2 \times 2 = 8 \quad \checkmark$$
 
## Problem 3: Test yourself (Sheet 4 Q1)


A toggle flipflop (T-flipflop) changes state whenever its T input is high on the CLOCK  $\uparrow$  edge as shown in the timing diagram.

Show how a T-flipflop can be made by combining an XOR gate with a D-flipflop.



 
## Solution 3: Test yourself (Sheet 4 Q1)

Show how a T-flipflop can be made by combining an XOR gate with a D-flipflop.




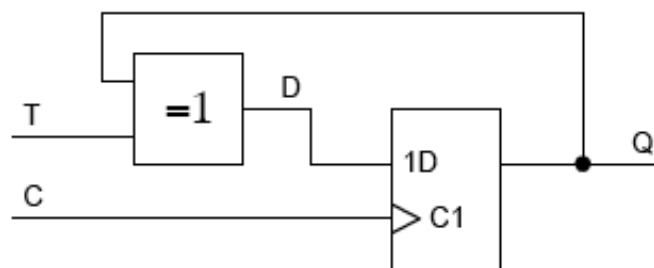An XOR gate can be used to invert a signal or pass it through unchanged according to whether a control input is high or low.



 
## Problem 4: Explain it (Sheet 4 Q2)

A multi-processor system contains two microprocessors which are mounted on separate printed circuit cards. The clock and data signals pass through a line driver when they leave one card and a line receiver when they pass onto the next. The combined delay of the driver+receiver may vary between 13 ns and 22 ns. New data values appear at DA on the falling edge of CA with a propagation delay of 5 to 50 ns. Data is clocked into  $\mu\text{P B}$  on the rising edge of CB with a setup time of 12 ns and a hold time of 27 ns. If the clock, CA, is a symmetrical squarewave, calculate its maximum frequency.



## Solution 4: Explain it (Sheet 4 Q2)

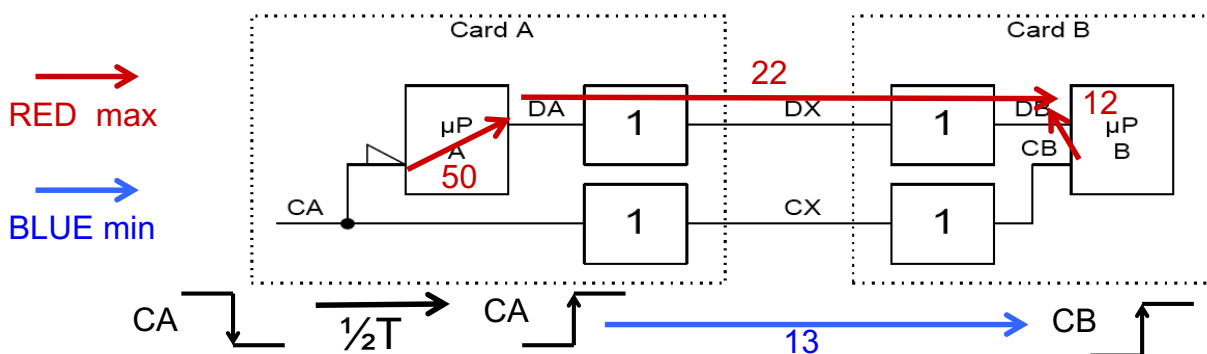

We define  $t=0$  as the falling edge of CA.

Setup requirement:


$$\max(\text{DB} \uparrow \downarrow) + 12 < \min(\text{CB} \uparrow)$$

$$50 + 22 + 12 < (13 + \frac{1}{2}T)$$

$$\frac{1}{2}T > 71 \Rightarrow f < 7 \text{ MHz}$$

**Setup time** requirement is governed by the **slowest data signal path** relative to **fastest clock path**

## Solution 4: Explain it (Sheet 4 Q2)

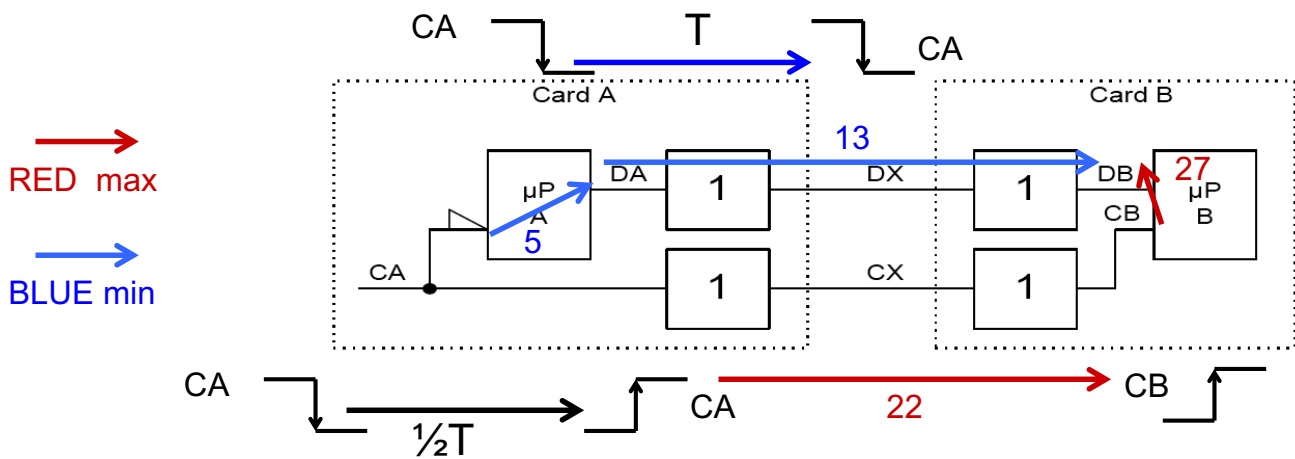

Hold requirement:

$$\max(\text{CB}\uparrow) + 27 > \min(\text{T} + \text{DB}\uparrow\downarrow)$$

$$\frac{1}{2}\text{T} + 22 + 27 > \text{T} + 5 + 13$$

$$\frac{1}{2}\text{T} > 31 \text{ (less severe restriction than above)}$$

**Hold time** requirement is governed by the **fastest data signal path on successive cycles relative to slowest clock path**