

**Problem Class**

**Tutorial Problem Sheet 1**


**Synchronous Circuits**

Peter Cheung  
Department of Electrical & Electronic Engineering  
Imperial College London



URL: [www.ee.imperial.ac.uk/pcheung/](http://www.ee.imperial.ac.uk/pcheung/)  
E-mail: [p.cheung@imperial.ac.uk](mailto:p.cheung@imperial.ac.uk)
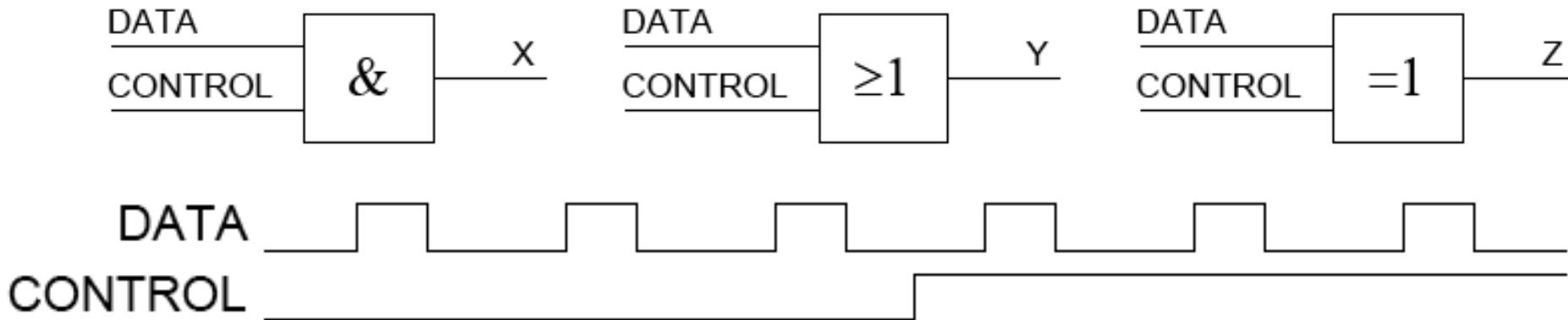
# Problem 1 - Test yourself (Sheet 1 Q1)

The diagram shows three gates in which one input (CONTROL) is being used to modify a signal at the other input (DATA). Complete the timing diagram by drawing the waveforms of X, Y and Z. Describe in words the effect each of the gates has on DATA when CONTROL is low and when it is high.





# Solution 1: Test yourself

  

 
 
## Problem 2 - Test yourself (Sheet 1 Q2)

The circuits below are a D-latch and a D-flipflop. Complete the timing diagram by drawing the waveforms of X and Y assuming that they are both low initially.




# Solution 2: Test yourself

---

  

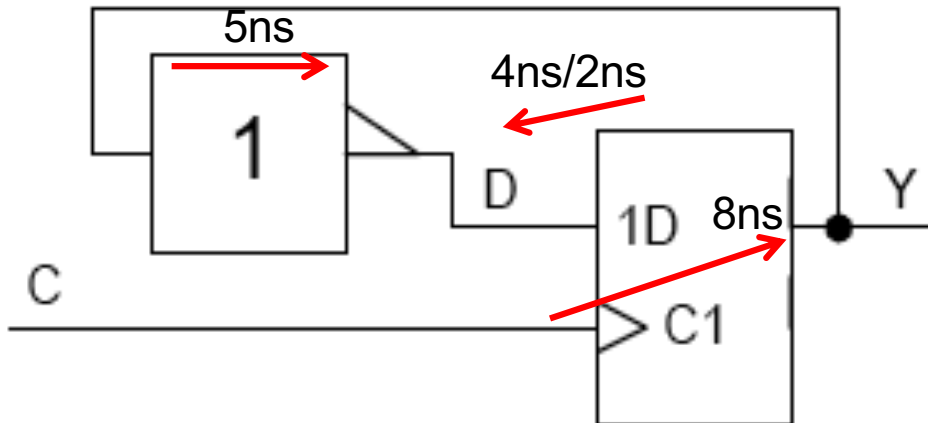
## Problem 3: Explain it (Sheet 1 Q3)

The circuit below forms a  $\div 2$  counter. If the inverter has a propagation delay of 5 ns and the propagation delay, setup time and hold time of the flipflop are 8 ns, 4 ns and 2 ns respectively, calculate the highest clock frequency for reliable operation.


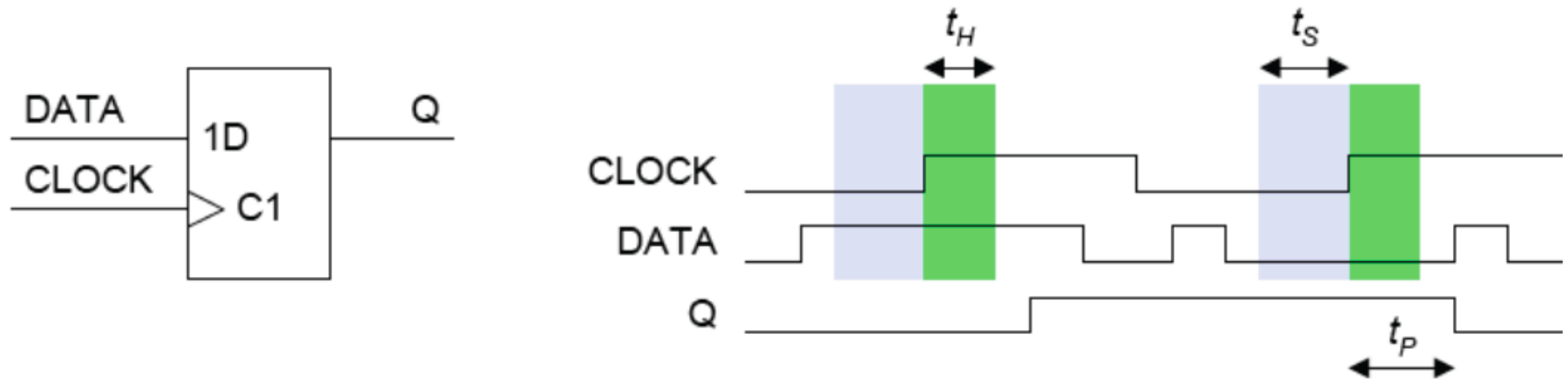
## Solution 3: Explain it (setup and hold times)

The DATA input to a flipflop or register must not change at the same time as the CLOCK.




**Setup Time:** DATA must reach its new value at least  $t_S$  before the CLOCK $\uparrow$  edge.


**Hold Time:** DATA must be held constant for at least  $t_H$  after the CLOCK $\uparrow$  edge.
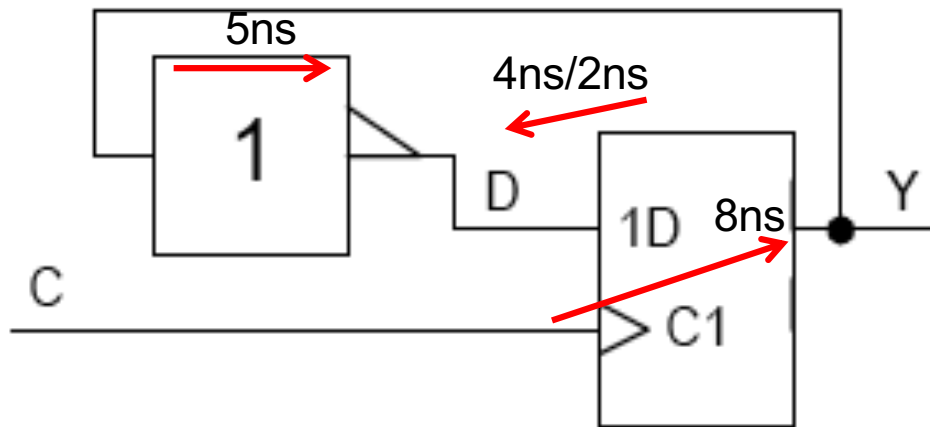
## Solution 3: Explain it

The circuit below forms a ÷2 counter. If the inverter has a propagation delay of 5 ns and the propagation delay, setup time and hold time of the flipflop are 8 ns, 4 ns and 2 ns respectively, calculate the highest clock frequency for reliable operation.



 
$$T - (5 + 8) > 4 \Rightarrow T > 17 \text{ ns}$$
$$\Rightarrow f < 58.8 \text{ MHz}$$





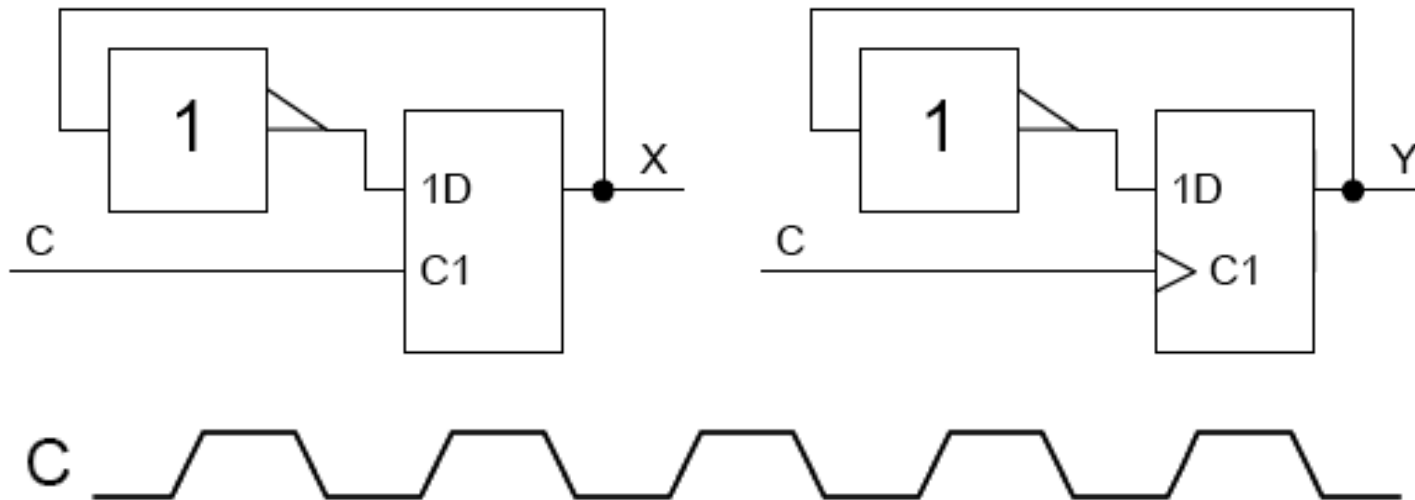
## Problem 4: Test yourself (Sheet 1 Q4)

The circuits below are a D-latch and a D-flipflop with their outputs connected to their inputs via an inverter. Draw the waveforms of X and Y assuming that they are both low initially and that C is a uniform square wave. (One of these circuits is a disaster and should never be used)




# Solution 4: Test yourself

 

## Problem 5: Test yourself (Sheet 1 Q5)

The 3-input Look-up Table (LUT) circuit could be made up from eight 2-to-1 multiplexers as shown here. Determine the configuration bits that must be stored in the eight registers driving this 3-LUT in order to implement the Boolean function:

$$Y = A*/C + /B*C + /A*B$$

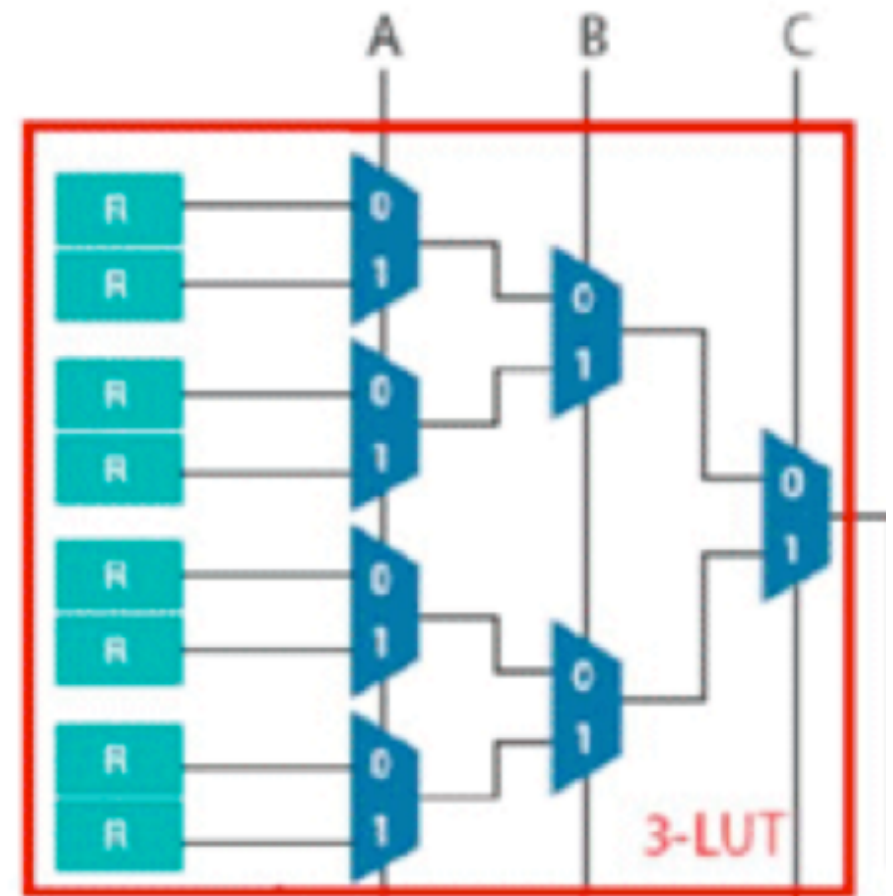


# Solution 5: Test yourself

$$Y = A*/C + /B*C + /A*B$$


Truth table:

C	B	A	Y output
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	1
1	0	1	1
1	1	0	1
1	1	1	0

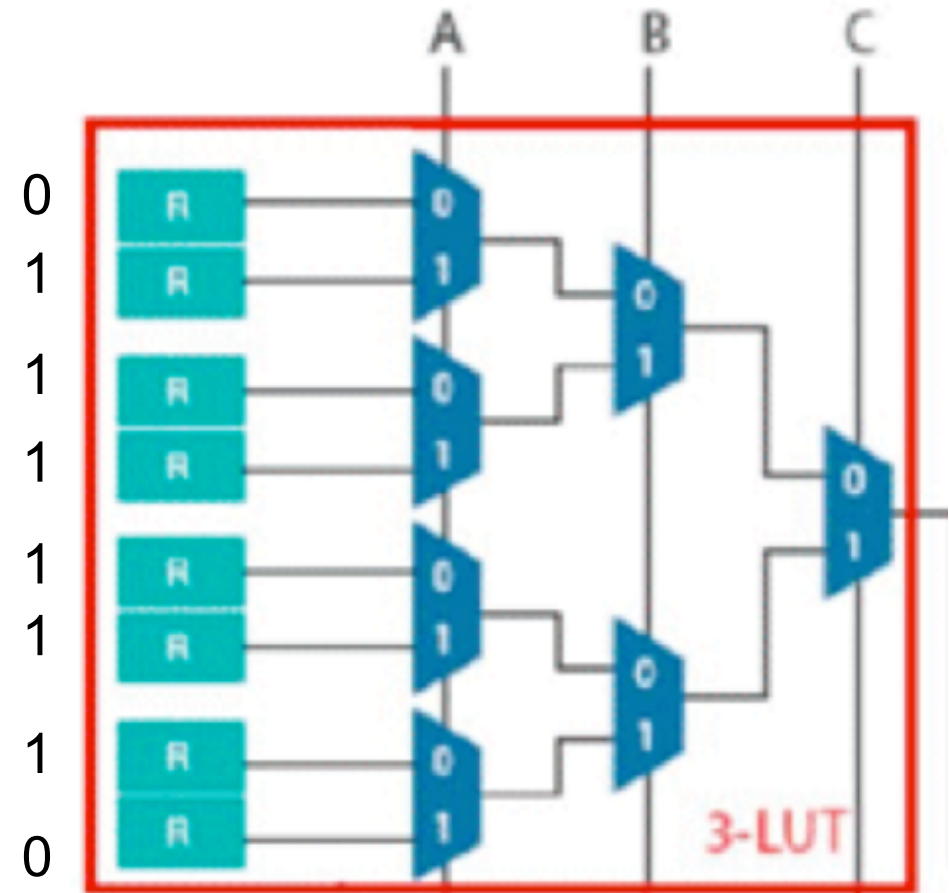
 
## Problem 6: Explain it (Sheet 1 Q6)

Design in Verilog HDL the hardware module LE\_3LUT that implements the 3-LUT circuit shown above.




## Solution 6: Explain it (Sheet 1 Q6)

```
// Implementation of a 3_LUT circuit
module lut_3 (out, in, A, B, C);

    output      out;
    input [7:0]  in;    // input value to LUT
    input       A, B, C; // control for LUT

    assign out = C ?
        (B ? (A ? in[7] : in[6]) : (A ? in[5] : in[4]))
        :(B ? (A ? in[3] : in[2]) : (A ? in[1] : in[0]));

endmodule
```

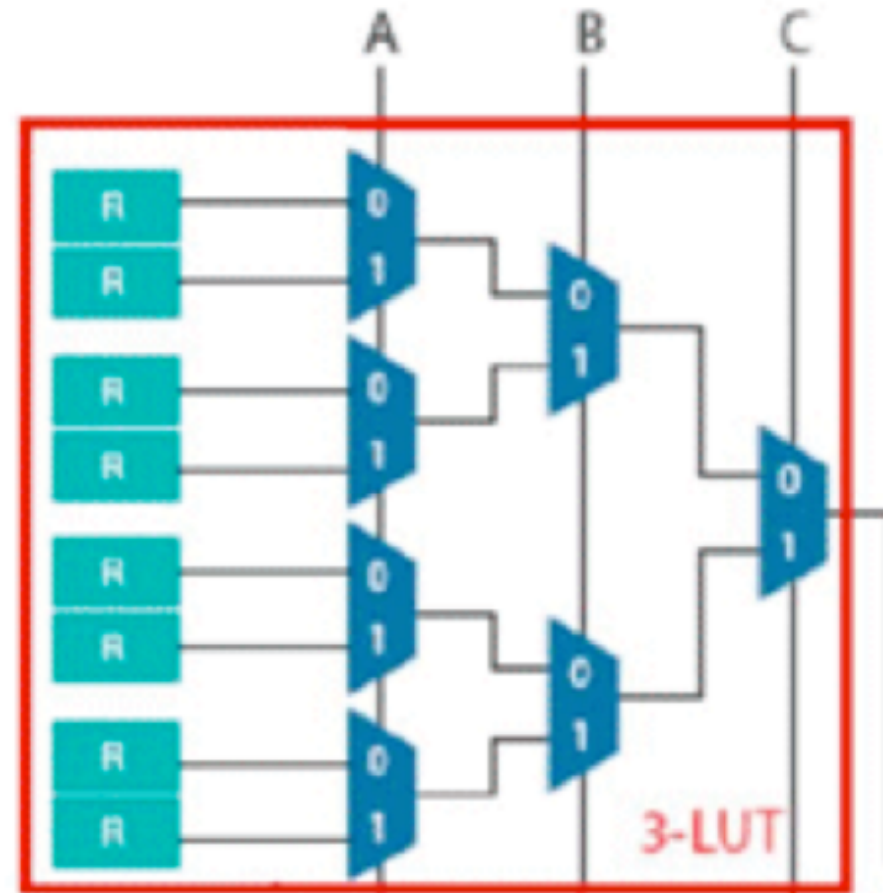

```
// ... instantiate the LUT
....
lut_3 q6_logic (out, 8'b01111110, A, B,C);
```