

## About this Topic

- ◆ Comparison of adder architectures on FPGAs
- ◆ Multiple operands addition
- ◆ Basic multipliers
- ◆ Booth recoding multipliers
- ◆ Fixed point vs Floating Point
- ◆ Floating point Unit architectures
- ◆ Example: FIR and IIR filter implementations
- ◆ References
  - “Computer Arithmetic”, B. Parhami, OUP
  - “Computer Arithmetic Algorithms”, I. Koren, AK Peters

## Topic 4

### Arithmetic Circuits


Peter Cheung  
Department of Electrical & Electronic Engineering  
Imperial College London

URL: [www.ee.imperial.ac.uk/pcheung/](http://www.ee.imperial.ac.uk/pcheung/)  
E-mail: [p.cheung@imperial.ac.uk](mailto:p.cheung@imperial.ac.uk)


## Different adder architectures

- ◆ Revision on last year's digital electronics II course ([http://www.ee.ic.ac.uk/hp/staff/dmb/courses/dig2/5\\_Adder.pdf](http://www.ee.ic.ac.uk/hp/staff/dmb/courses/dig2/5_Adder.pdf))
- ◆ Common adder architectures are:
  - Ripple carry adder
  - Carry lookahead adder
  - Carry skip (or carry select) adder
  - Carry save adder
  - Parallel prefix adder (Brent & Kung's)

## Basic Ripple Carry Adder

 


(a) Bit-serial adder.

 

Source: Parhami
 
## Critical Path Through a Ripple-Carry Adder


$$T_{\text{ripple-add}} = T_{\text{FA}}(x, y \rightarrow c_{\text{out}}) + (k - 2) \times T_{\text{FA}}(c_{\text{in}} \rightarrow c_{\text{out}}) + T_{\text{FA}}(c_{\text{in}} \rightarrow s)$$



Critical path in a  $k$ -bit ripple-carry adder.

Source: Parhami

## Adder Conditions and Exceptions

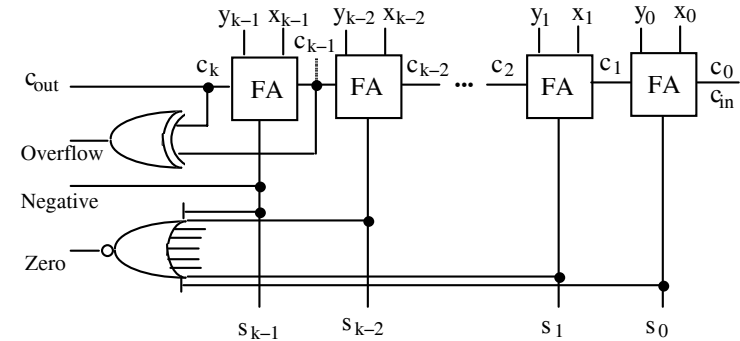

Two's-complement adder with provisions for detecting conditions and exceptions.

$$\text{overflow}_{2\text{'s-compl}} = x_{k-1} y_{k-1} s_{k-1}' \vee x_{k-1}' y_{k-1}' s_{k-1}$$

$$\text{overflow}_{2\text{'s-compl}} = c_k \oplus c_{k-1} = c_k c_{k-1}' \vee c_k' c_{k-1}$$

Source: Parhami

## Saturating Adders

### Saturating (saturation) arithmetic:

When a result's magnitude is too large, do not wrap around; rather, provide the most positive or the most negative value that is representable in the number format


**Example** – In 8-bit 2's-complement format, we have:  
 $120 + 26 \rightarrow 18$  (wraparound);  $120 +_{\text{sat}} 26 \rightarrow 127$  (saturating)

Saturating arithmetic is desirable in many DSP applications

### Designing saturating adders


Unsigned (quite easy)

Signed (only slightly harder)

 

Source: Parhami

## Full Carry Lookahead

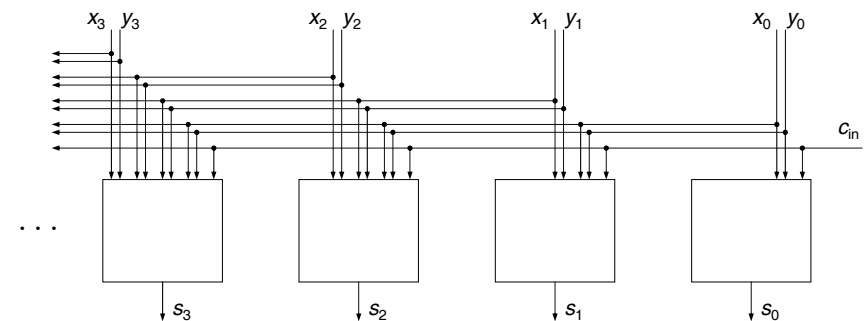

Theoretically, it is possible to derive each sum digit directly from the inputs that affect it

Carry-lookahead adder design is simply a way of reducing the complexity of this ideal, but impractical, arrangement by hardware sharing among the various lookahead circuits

Source: Parhami

## Unrolling the Carry Recurrence

Recall the *generate g*, *propagate p* signals:

Signal	Radix $r$	Binary
$g_i$	is 1 iff $x_i + y_i \geq r$	$x_i y_i$
$p_i$	is 1 iff $x_i + y_i = r - 1$	$x_i \oplus y_i$
$s_i$	$(x_i + y_i + c_i) \bmod r$	$x_i \oplus y_i \oplus c_i$

The carry recurrence can be unrolled to obtain each carry signal directly from inputs, rather than through propagation


$$\begin{aligned}
 c_i &= g_{i-1} + c_{i-1} p_{i-1} \\
 &= g_{i-1} + (g_{i-2} + c_{i-2} p_{i-2}) p_{i-1} \\
 &= g_{i-1} + g_{i-2} p_{i-1} + c_{i-2} p_{i-2} p_{i-1} \\
 &= g_{i-1} + g_{i-2} p_{i-1} + g_{i-3} p_{i-2} p_{i-1} + c_{i-3} p_{i-3} p_{i-2} p_{i-1} \\
 &= g_{i-1} + g_{i-2} p_{i-1} + g_{i-3} p_{i-2} p_{i-1} + g_{i-4} p_{i-3} p_{i-2} p_{i-1} + c_{i-4} p_{i-4} p_{i-3} p_{i-2} p_{i-1} \\
 &= \dots
 \end{aligned}$$

Source: Parhami
 
## Carry-Lookahead Adder Design

Block *generate* and *propagate* signals


$$\begin{aligned}
 g_{[i,i+3]} &= g_{i+3} + g_{i+2} p_{i+3} + g_{i+1} p_{i+2} p_{i+3} + g_i p_{i+1} p_{i+2} p_{i+3} \\
 p_{[i,i+3]} &= p_i p_{i+1} p_{i+2} p_{i+3}
 \end{aligned}$$



Schematic diagram of a 4-bit lookahead carry generator.


Source: Parhami
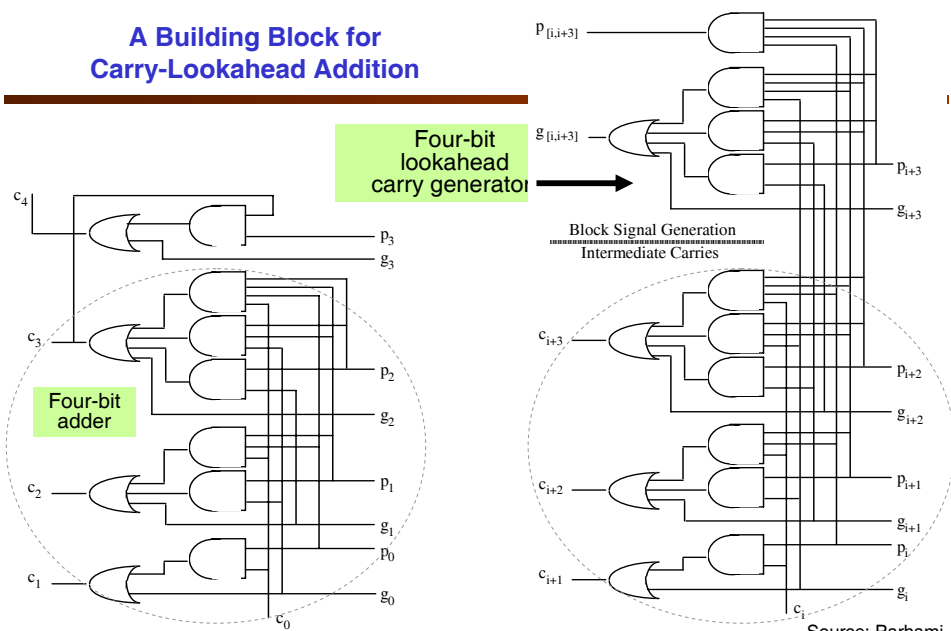
## A Building Block for Carry-Lookahead Addition



Source: Parhami

## Combining Block *g* and *p* Signals

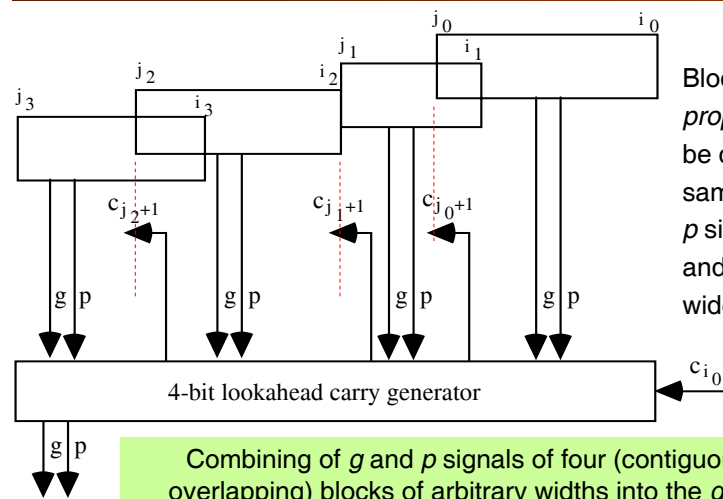


Block *generate* and *propagate* signals can be combined in the same way as bit *g* and *p* signals to form *g* and *p* signals for wider blocks

Combining of *g* and *p* signals of four (contiguous or overlapping) blocks of arbitrary widths into the *g* and *p* signals for the overall block  $[i_0, j_3]$ .

Source: Parhami

## Carry-Select Adders

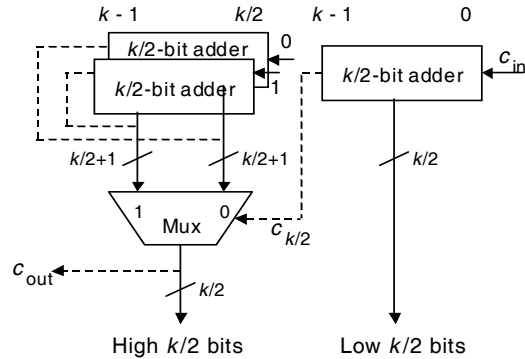


Carry-select adder for  $k$ -bit numbers built from three  $k/2$ -bit adders.

$$C_{\text{select-add}}(k) = 3C_{\text{add}}(k/2) + k/2 + 1$$

$$T_{\text{select-add}}(k) = T_{\text{add}}(k/2) + 1$$

Source: Parhami

## Multilevel Carry-Select Adders

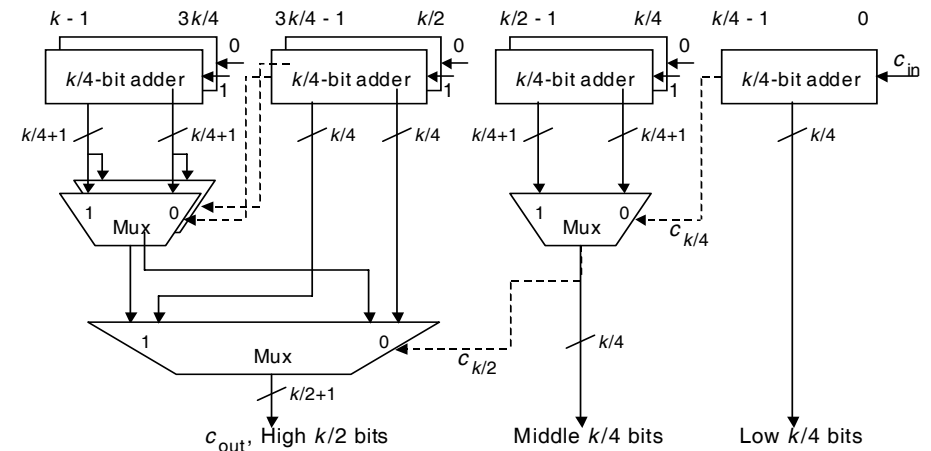


Two-level carry-select adder built of  $k/4$ -bit adders.

Source: Parhami

## Comparison between adders on modern FPGAs


- ◆ Sacristan, Rodella & Diaz, "Comparison of addition structures synthesis over commercial FPGAs", International Conf. on Design & Test, 2006 Page(s):413 - 417
- ◆ Compare ripple carry adder (RCA), carry lookahead adder (CLA), carry select adder (CSLA), Brent&Kung parallel prefix adder (PA-BK) and finally not specifying any structure and let the synthesis tool decide!
- ◆ Use Altera Stratix II and Xilinx Virtex-4 (not latest, but pretty recent).
- ◆ Result summary:
  - Mostly as expected, faster means larger
  - Surprising, synthesis tools does the best: both fast and small!!
  - Morale – at low level, difficult to beat modern synthesis tools
- ◆ Results shown in the next four slides.

## Results for Stratix II – Area

 


Source: Sacristan

## Results for Stratix II – Delay

 


Source: Sacristan

## Results for Virtex 4 – Area

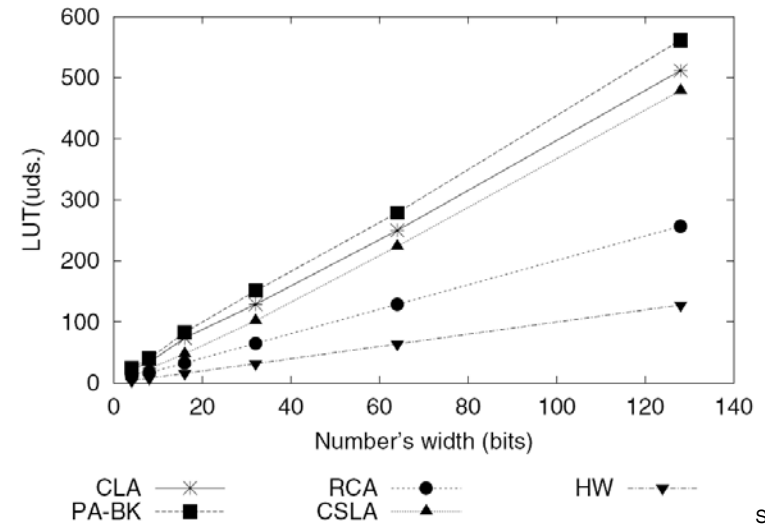

Source: Sacristan

## Results for Virtex-4 – Delay

 

Source: Sacristan

## Multipliers and DSP Blocks


- ◆ Remember that both Altera and Xilinx FPGAs have embedded multipliers with accumulators etc.
- ◆ This part of the lecture will look at some of the common multiplier hardware (i.e. what such embedded multiplier circuits might look like).
- ◆ We will also consider application of FPGA embedded multiplier for FIR Filter implementations.
- ◆ Topics to cover are:
  - Basic multipliers
  - Booth recoded multipliers
  - Array multipliers
  - FIR Filter Compiler

## Multiplication of two 4-bit unsigned numbers

Notation:


$a$     Multiplicand                     $a_{k-1}a_{k-2} \dots a_1a_0$   
 $x$     Multiplier                         $x_{k-1}x_{k-2} \dots x_1x_0$   
 $p$     Product ( $a \times x$ )                 $p_{2k-1}p_{2k-2} \dots p_3p_2p_1p_0$

Initially, we assume unsigned operands

 


Source: Parhami

## An example

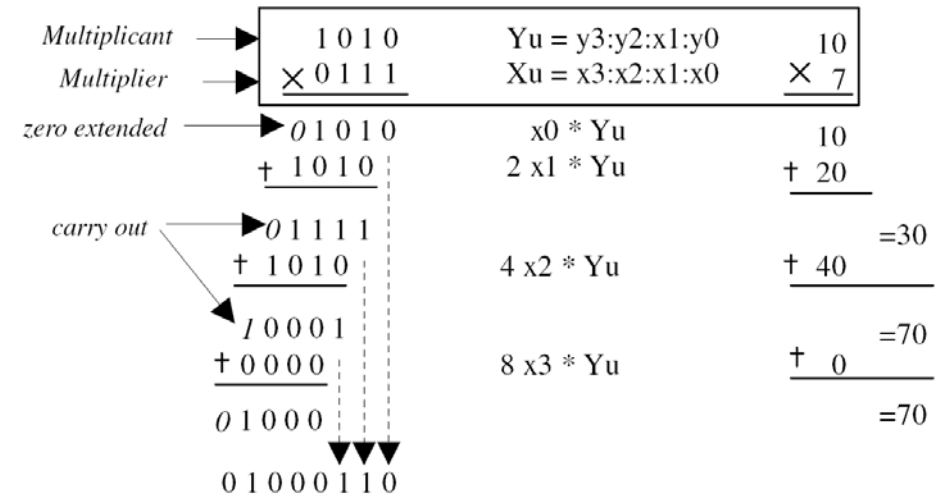


## Basic Sequential Multipliers

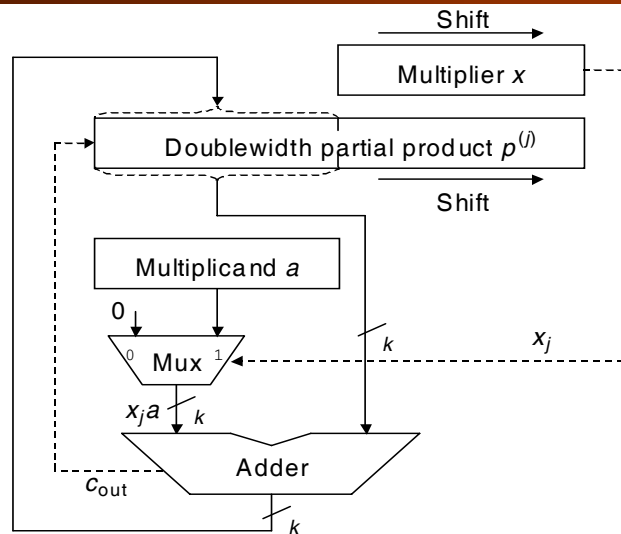

Source: Parhami

 
## Performing Add and Shift in One Clock Cycle




Combining the loading and shifting of the double-width register holding the partial product and the partially used multiplier.

Source: Parhami

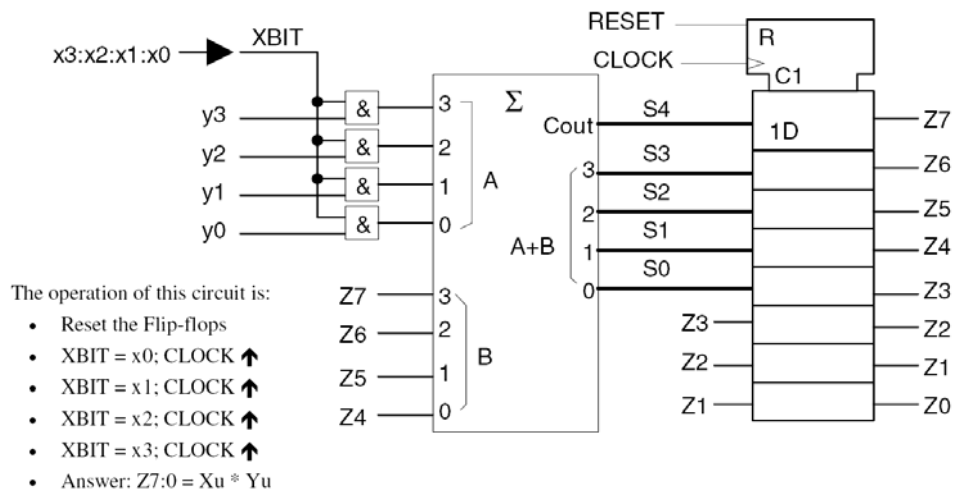
## Example of a detail 4x4 unsigned sequential multiplier



## 2's complement signed multiplication

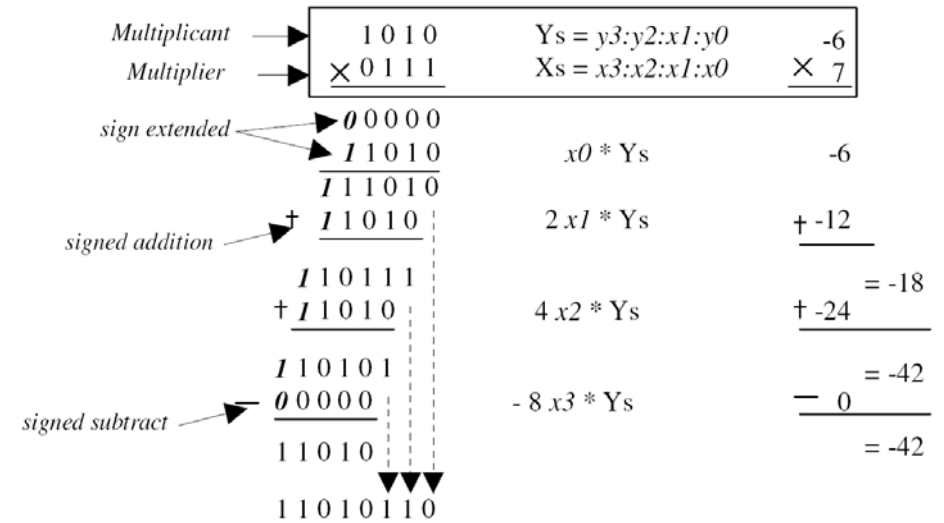
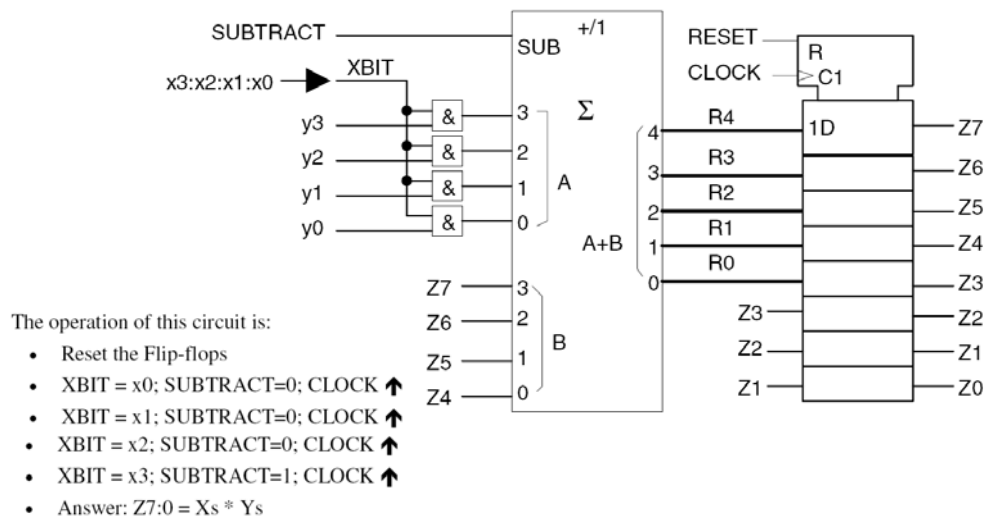
## 4x4 sequential signed multiplier circuit




## Recoded Multiplier – Booth Algorithm (1)

Instead of treating the MSB differently from all other bits, it is possible to rearrange the binary bits and code them differently. **Booth Algorithm** is one of many algorithms that group together a number of bits in the multiplier and perform a **recoding** of the binary bits before the actual addition/subtraction. The table above shows how the Booth algorithm work:

- At each stage, we add  $Y_s * 2^i * (-x_i + x_{i-1})$
- We assume that  $x_{-1} = 0$
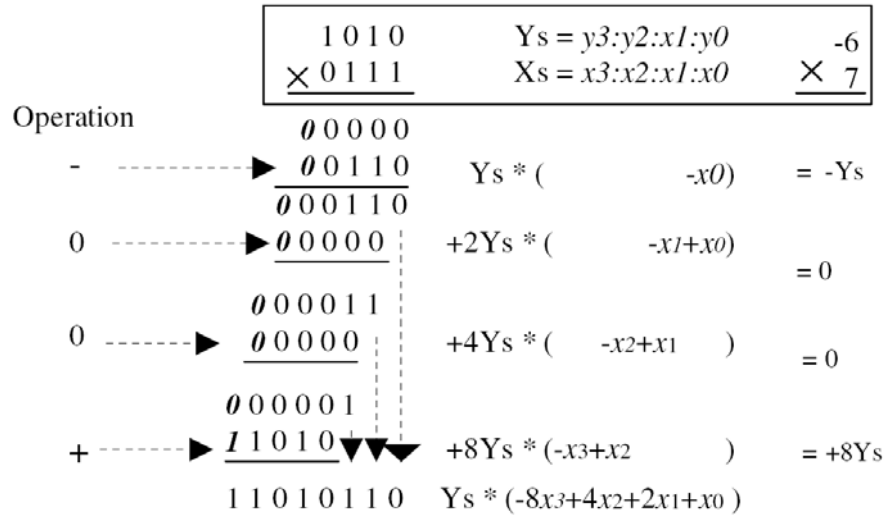
## Recoded Multiplier – Booth Algorithm (1)



## Proof of Booth Algorithm

$$\sum_{i=0}^{N-1} 2^i (-x_i + x_{i-1})$$

**Booth Algorithm does this**

$x_i$	$x_{i-1}$	$(-x_i+x_{i-1})$	Comments
0	0	0	Do nothing
0	1	+1	Add $Y_s$
1	0	-1	Subtract $Y_s$
1	1	0	Do nothing

$$= -\sum_{i=0}^{N-1} 2^i x_i + \sum_{i=0}^{N-1} 2^i x_{i-1}$$

$$= -\sum_{i=0}^{N-1} 2^i x_i + \sum_{i=-1}^{N-2} 2^{i+1} x_i$$


$$= -2^{N-1} x_{N-1} - \sum_{i=0}^{N-2} 2^i x_i + \sum_{i=0}^{N-2} 2^{i+1} x_i + 2^0 x_{-1}$$

$$= -2^{N-1} x_{N-1} + \sum_{i=0}^{N-2} (-2^i + 2^{i+1}) x_i$$

$$= -2^{N-1} x_{N-1} + \sum_{i=0}^{N-2} 2^i x_i$$


**2's complement rep of x**

## Sequential Booth Multiplier

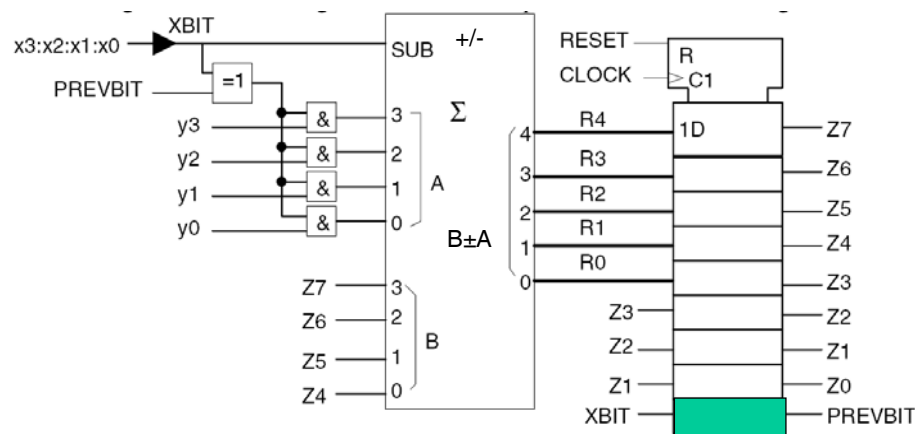
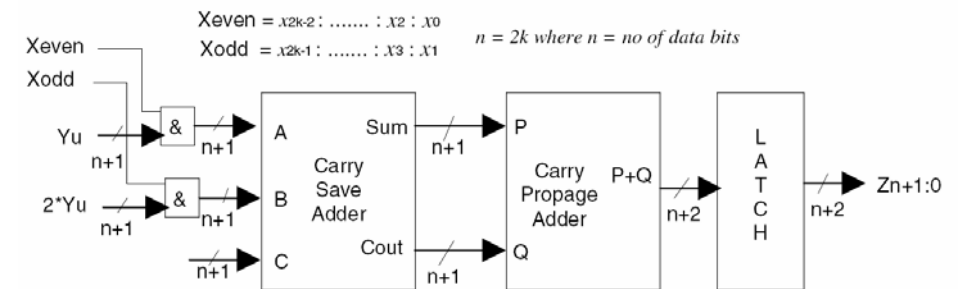
## Multi-bit sequential multiplier


All the circuits considered so far handle only one bit multiplication at each clock cycle. There are no reasons why we could not deal with two (or more) bits at a time.









## Array Multiplier

 

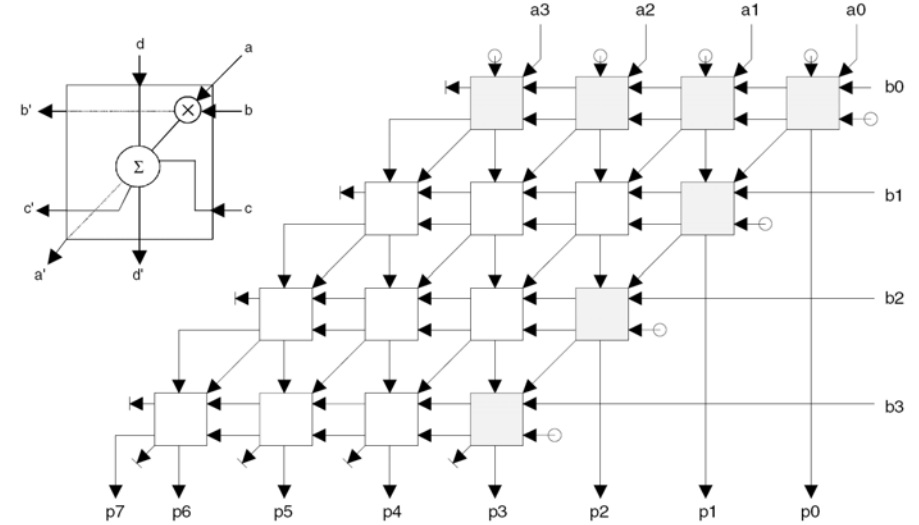
## Array Multiplier – obvious, but slow version


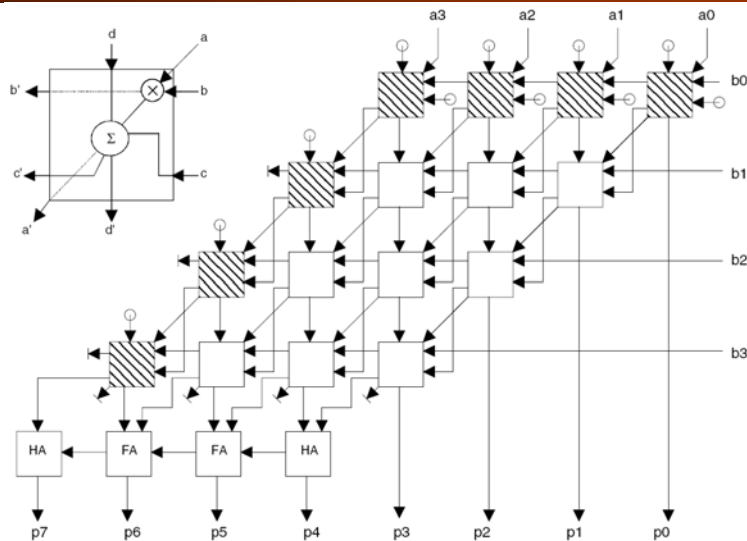
## Array Multiplier – using carry-save adders


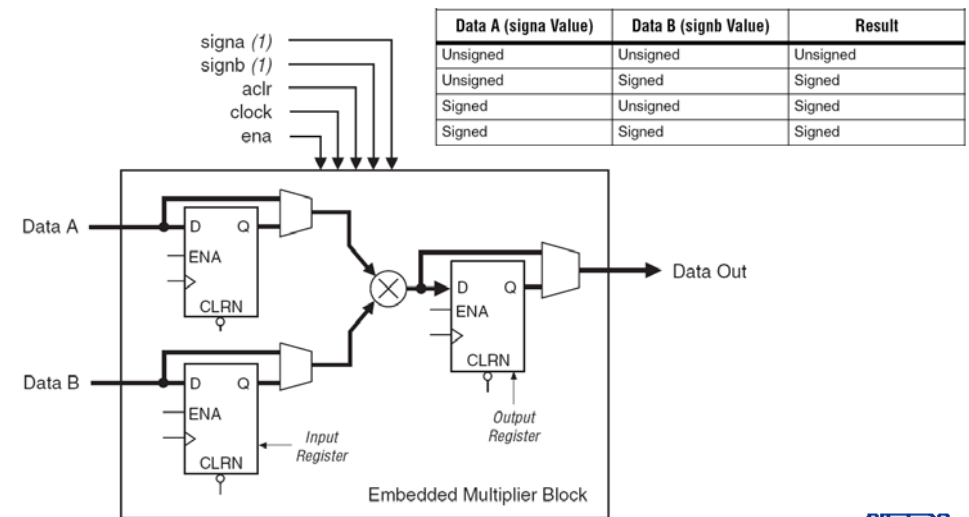
## Embedded Multipliers in Altera Cyclone II (1)




## Embedded Multipliers in Altera Cyclone II (2)

Multiplier Mode	Description
18-bit Multiplier	An embedded multiplier can be configured to support a single $18 \times 18$ multiplier for operand widths up to 18 bits. All 18-bit multiplier inputs and results can be registered independently. The multiplier operands can accept signed integers, unsigned integers, or a combination of both.
9-bit Multiplier	An embedded multiplier can be configured to support two $9 \times 9$ independent multipliers for operand widths up to 9-bits. Both 9-bit multiplier inputs and results can be registered independently. The multiplier operands can accept signed integers, unsigned integers or a combination of both. There is only one <i>signa</i> signal to control the sign representation of both data A inputs and one <i>signb</i> signal to control the sign representation of both data B inputs of the 9-bit multipliers within the same dedicated multiplier.


Source: ALTERA
 
## Embedded Multipliers in Altera Cyclone II (3)



Source: ALTERA

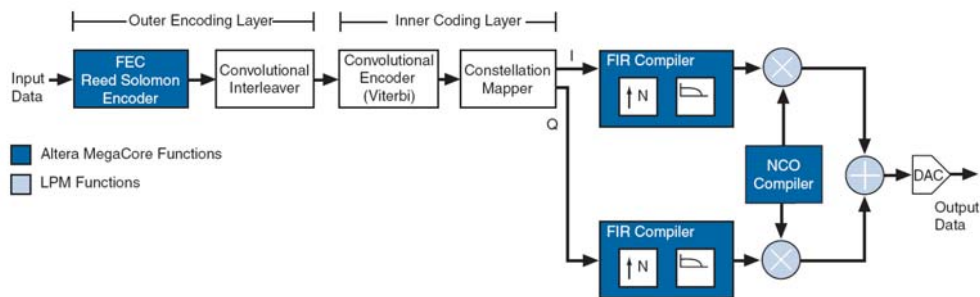
## Application of Multipliers: Typical DSP System



- ◆ Altera and Xilinx provide FIR filter compiler support.
- ◆ These examples are taken from Altera's "FIR Compiler User's Guide".
- ◆ MegaCore functions pre-designed core (large modules).
- ◆ LPM Functions are parameterised building blocks (e.g. adder, multiplier)

Source: ALTERA


## Basic FIR Filter

 

- ◆ Altera and Xilinx provide FIR filter compiler support.
- ◆ These examples are taken from Altera's "FIR Compiler User's Guide".


Source: ALTERA
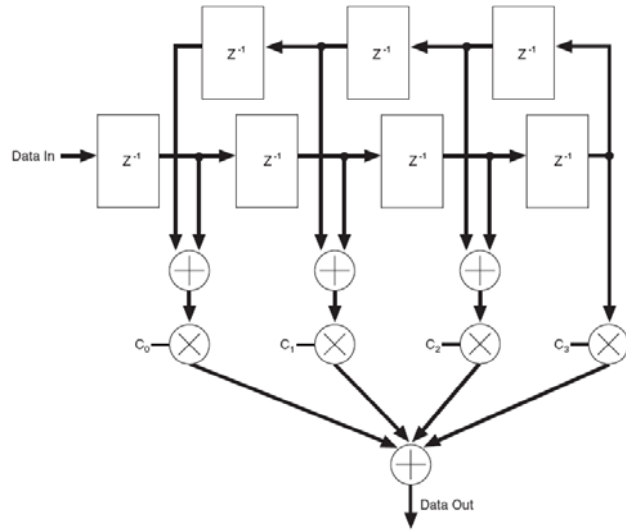
## Exploiting Symmetric Coefficients (7-tap)




Source: ALTERA

## Parallel Implementation of FIR Filter

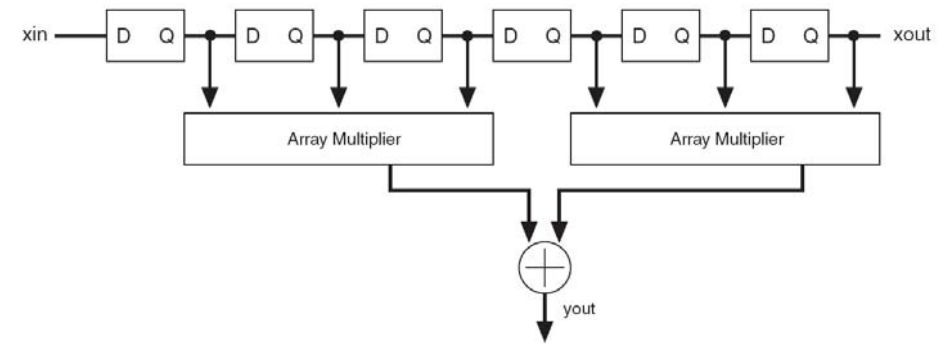


Source: ALTERA

## Serial Implementation of FIR Filter

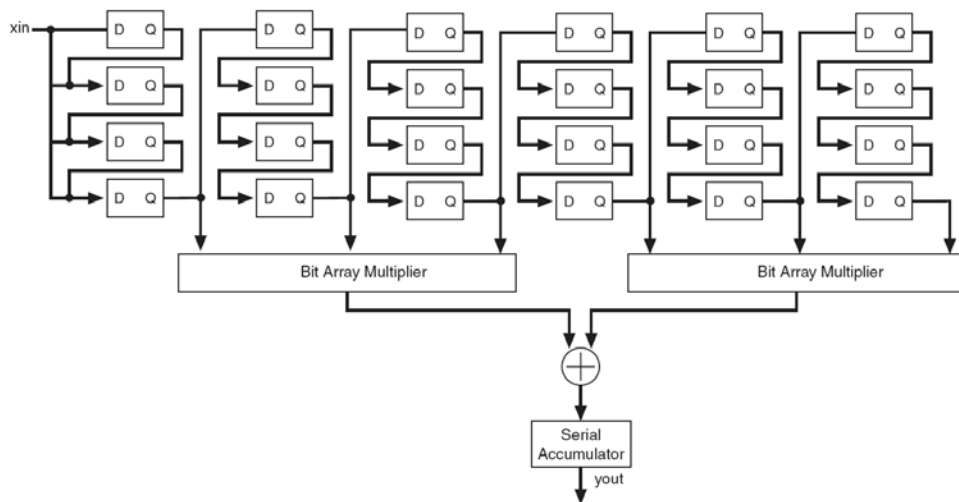


Source: ALTERA
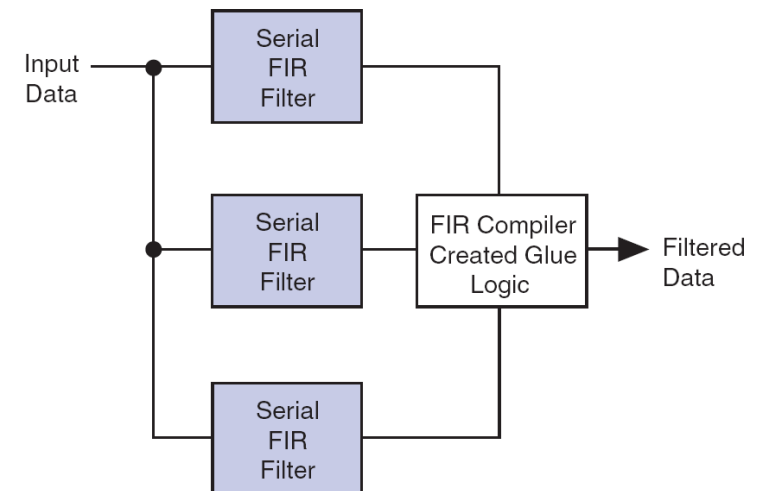
## Multibit Serial Implementation of FIR Filter



Source: ALTERA

## FIR Filter Compiler Design Space

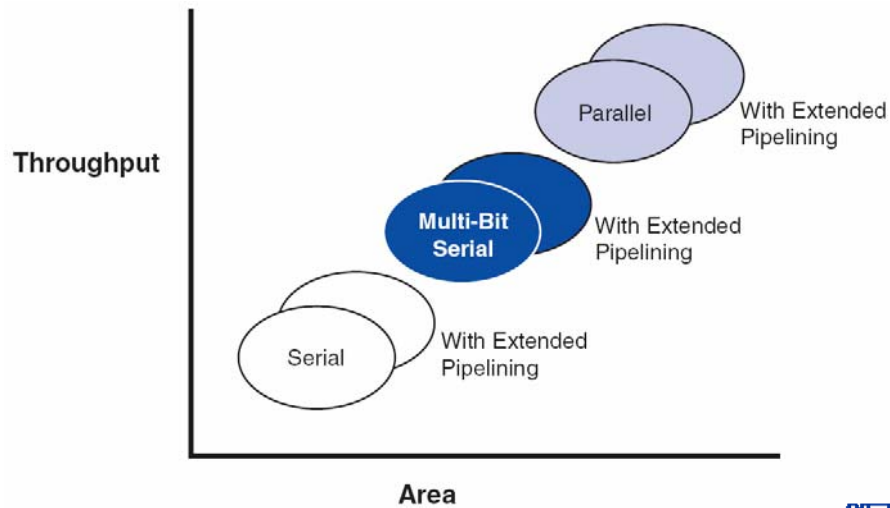

Source: ALTERA

## Floating-Point Numbers

No finite number system can represent all real numbers  
 Various systems can be used for a subset of real numbers

Fixed-point	$\pm w.f$	Low precision and/or range
Rational	$\pm p/q$	Difficult arithmetic
Floating-point	$\pm s \times b^e$	Most common scheme
Logarithmic	$\pm \log_b x$	Limiting case of floating-point

Fixed-point numbers

$$x = (0000\ 0000 . 0000\ 1001)_{\text{two}}$$

$$y = (1001\ 0000 . 0000\ 0000)_{\text{two}}$$

Small number                      Large number

Floating-point numbers

$$x = \pm s \times b^e \quad \text{or} \quad \pm \text{significand} \times \text{base}^{\text{exponent}}$$


Note that a floating-point number comes with two signs:

Number sign, usually represented by a separate bit  
 Exponent sign, usually embedded in the biased exponent


Source: Parhami

## Floating-Point Number Format and Distribution

Typical floating-point number format.

 


 Subranges and special values in floating-point number representations.



Source: Parhami
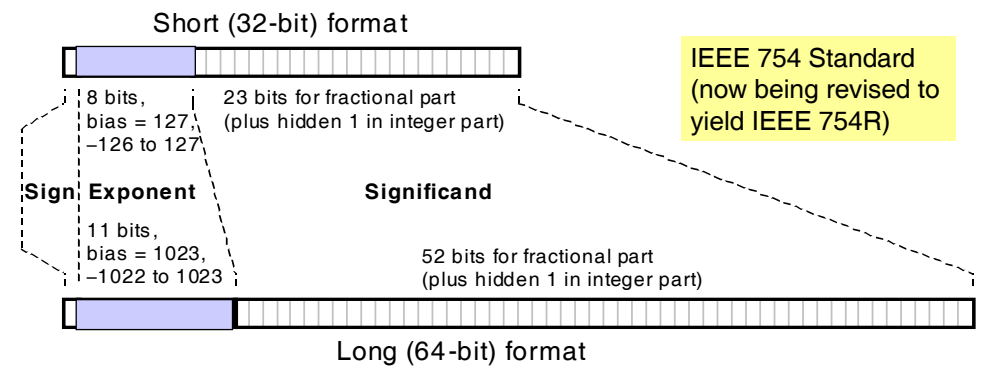
## The ANSI/IEEE Floating-Point Representation



Source: Parhami

# Overview of IEEE 754 Standard Formats


Some features of the ANSI/IEEE standard floating-point number representation formats.

Feature	Single/Short	Double/Long
Word width (bits)	32	64
Significand bits	23 + 1 hidden	52 + 1 hidden
Significand range	$[1, 2 - 2^{-23}]$	$[1, 2 - 2^{-52}]$
Exponent bits	8	11
Exponent bias	127	1023
Zero ( $\pm 0$ )	$e + bias = 0, f = 0$	$e + bias = 0, f = 0$
Denormal	$e + bias = 0, f \neq 0$ represents $\pm 0.f \times 2^{-126}$	$e + bias = 0, f \neq 0$ represents $\pm 0.f \times 2^{-1022}$
Infinity ( $\pm \infty$ )	$e + bias = 255, f = 0$	$e + bias = 2047, f = 0$
Not-a-number (NaN)	$e + bias = 255, f \neq 0$	$e + bias = 2047, f \neq 0$
Ordinary number	$e + bias \in [1, 254]$ $e \in [-126, 127]$ represents $1.f \times 2^e$	$e + bias \in [1, 2046]$ $e \in [-1022, 1023]$ represents $1.f \times 2^e$
<i>min</i>	$2^{-126} \cong 1.2 \times 10^{-38}$	$2^{-1022} \cong 2.2 \times 10^{-308}$
<i>max</i>	$\cong 2^{128} \cong 3.4 \times 10^{38}$	$\cong 2^{1024} \cong 1.8 \times 10^{308}$

Source: Parhami
 
# Exponent Encoding

Exponent encoding in 8 bits for the single/short (32-bit) ANSI/IEEE format




$f = 0$ : Representation of  $\pm 0$

$f \neq 0$ : Representation of denormals,  
 $0.f \times 2^{-126}$

$f = 0$ : Representation of  $\pm \infty$

$f \neq 0$ : Representation of NaNs

 Exponent encoding in 11 bits for the double/long (64-bit) format is similar



# Floating-Point Adders/Subtractors

Assume  $e1 \geq e2$ ; alignment shift (preshift) is needed if  $e1 > e2$

$$(\pm s1 \times b^{e1}) + (\pm s2 \times b^{e2}) = (\pm s1 \times b^{e1}) + (\pm s2 / b^{e1-e2}) \times b^{e1}$$

$$= (\pm s1 \pm s2 / b^{e1-e2}) \times b^{e1} = \pm s \times b^e$$

### Example:

Numbers to be added:

$$x = 2^5 \times 1.00101101$$

$$y = 2^1 \times 1.11101101$$

Operand with smaller exponent to be preshifted

Operands after alignment shift:

$$x = 2^5 \times 1.00101101$$

$$y = 2^5 \times 0.000111101101$$

Extra bits to be rounded off

Result of addition:

$$s = 2^5 \times 1.010010111101$$

$$s = 2^5 \times 1.01001100$$

Rounded sum

### Like signs:

Possible 1-position normalizing right shift

### Different signs:

Possible left shift by many positions

### Overflow/underflow during addition or normalization

Source: Parhami

# FP Adder/Sub


Isolate the sign, exponent, significand  
Reinstate the hidden 1  
Convert operands to internal format  
Identify special operands, exceptions

### Other key parts of the adder:


- Significand aligner (preshifter)
- Result normalizer (postshifter), including leading 0s detector/predictor
- Rounding unit
- Sign logic

Converting internal to external representation, if required, must be done at the rounding stage

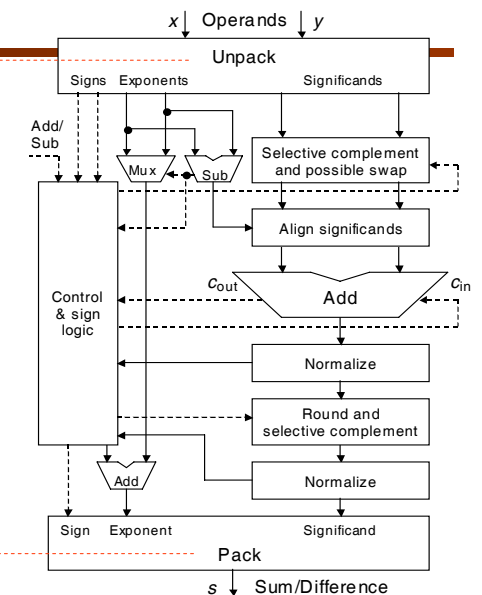Combine sign, exponent, significand  
Hide (remove) the leading 1  
Identify special outcomes, exceptions



## re- and Postshifting

 

Source: Parhami

PYKC 21-Jan-08

E3.05 Digital System Design

Topic 4 Slide 57

## Leading Zeros/Ones Detection or Prediction

Leading zeros prediction, with adder inputs  $(0x_0 \cdot x_{-1} x_{-2} \dots)_2$ 's-compl and  $(0y_0 \cdot y_{-1} y_{-2} \dots)_2$ 's-compl


Ways in which leading 0s/1s are generated:

*pp...ppgaa...aag...*  
*pp...ppgaa...aap...*  
*pp...ppagg...gga...*  
*pp...ppagg...ggp...*

Prediction might be done in two stages:

- Coarse estimate, used for coarse shift
- Fine tuning of estimate, used for fine shift

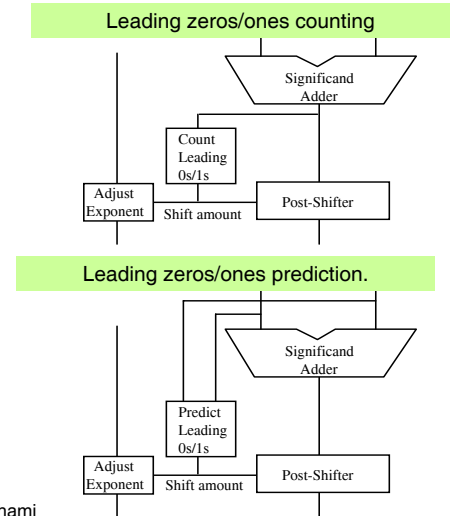In this way, prediction can be partially overlapped with shifting



Source: Parhami

PYKC 21-Jan-08

E3.05 Digital System Design

Topic 4 Slide 58


## Floating-Point Multipliers

$$(\pm s_1 \times b^{e_1}) \times (\pm s_2 \times b^{e_2}) = (\pm s_1 \times s_2) \times b^{e_1+e_2}$$

$s_1 \times s_2 \in [1, 4)$ : may need postshifting  
 Overflow or underflow can occur during multiplication or normalization

### Speed considerations

Many multipliers produce the lower half of the product (rounding info) early  
 Need for normalizing right-shift is known at or near the end  
 Hence, rounding can be integrated in the generation of the upper half, by producing two versions of these bits

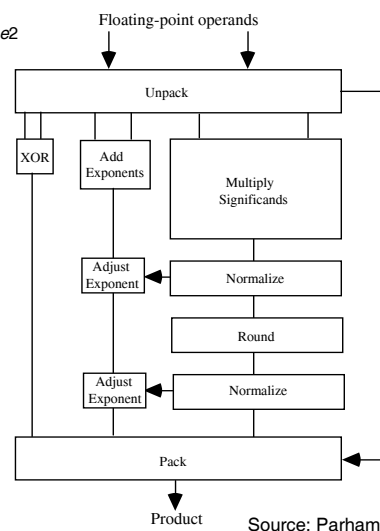

PYKC 21-Jan-08

E3.05 Digital System Design

Topic 4 Slide 59

## Further references for Floating Point on FPGAs

- ♦ **An analysis of the double-precision floating-point FFT on FPGAs**  
 Hemmert, K.S.; Underwood, K.D.; 13th Annual IEEE Symposium on Field-Programmable Custom Computing Machines, 18-20 April 2005 Page(s):171 - 180
- ♦ **Architectural Modifications to Improve Floating-Point Unit Efficiency in FPGAs**  
 Beauchamp, M.J.; Hauck, S.; Underwood, K.D.; Hemmert, K.S.; International Conference on Field Programmable Logic and Applications, 28-30 Aug. 2006 Page(s):1 - 6
- ♦ **Double precision floating-point arithmetic on FPGAs**  
 Paschalakis, S.; Lee, P.; IEEE International Conference on Field-Programmable Technology (FPT), 15-17 Dec. 2003 Page(s):352 - 358

PYKC 21-Jan-08

E3.05 Digital System Design

Topic 4 Slide 60