

Topic 3

Modern FPGA Architectures

Peter Cheung
Department of Electrical & Electronic Engineering
Imperial College London

URL: www.ee.imperial.ac.uk/pcheung/
E-mail: p.cheung@imperial.ac.uk

Key architectural improvements


1. Better programmable logic element (or CLB)
2. More flexible on-chip memories
3. Faster computation with embedded DSP blocks/Multipliers
4. Reduced routing delay and improved performance
5. Lower power

◆ We will focus on:

- Altera's latest Stratix III Family
- Xilinx's latest Virtex 5 Family

 1. Better programmable logic element (or CLB)


- ◆ For many years, all FPGAs are based around 4-LUTs (deemed to be most efficient*)
- ◆ Add block memories
- ◆ Add multipliers/DSP modules



* J. Rose, R.J. Francis, D. Lewis and P. Chow, "Architecture of Field-Programmable Gate Arrays: The Effect of Logic Functionality on Area Efficiency", IEEE Journal of Solid-State Circuits, pp. 1217-1225, 1990.


FPGA's journey: from Glue Logic to SoC

- ◆ FPGAs are now being used everywhere!

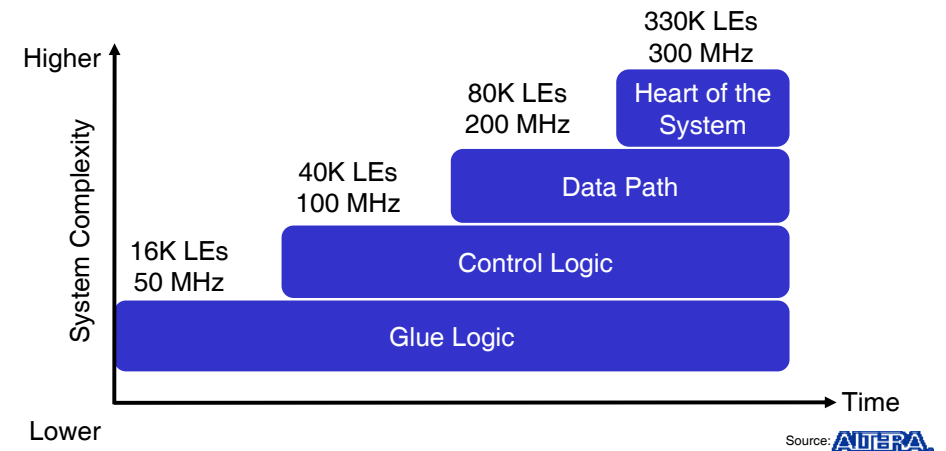


One LUT Size Does Not Fit All

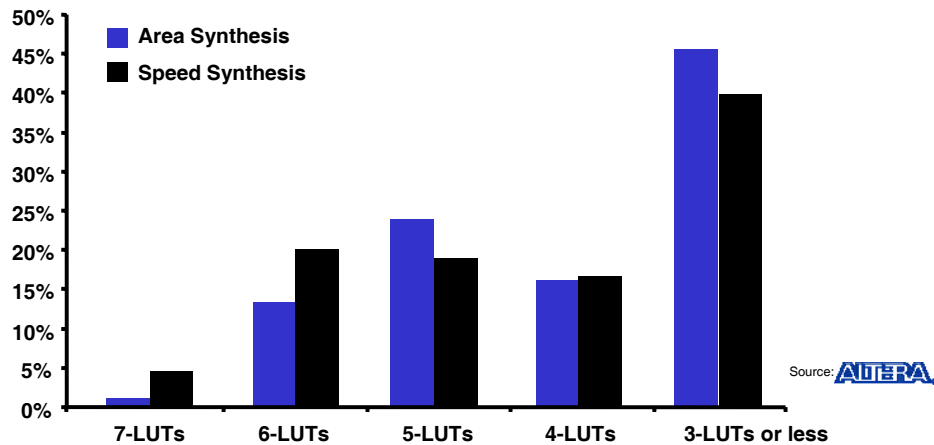- 4-LUTs are no longer the best. Here is some results of real benchmarks showing the need for other sizes of LUTs.




Altera Patented design: Adaptive Logic Module

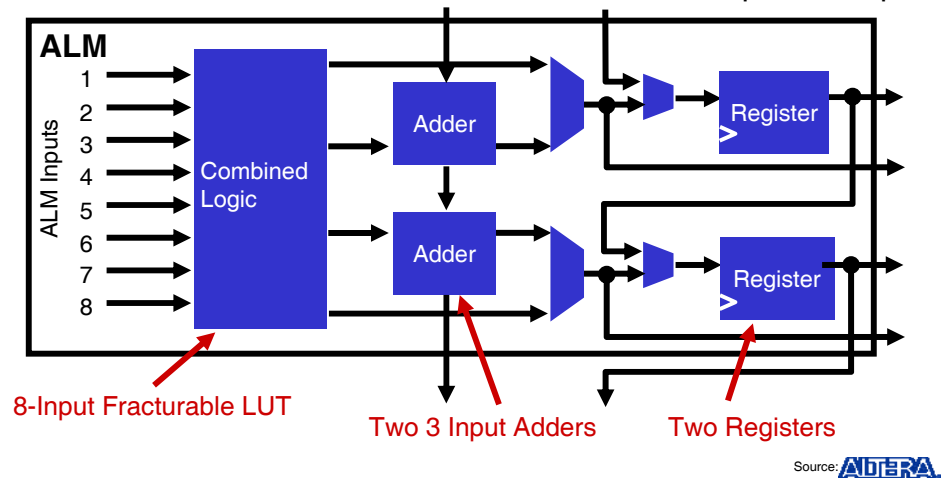- First introduced in Stratix II devices – ALM has 8 inputs 2 outputs



Altera's Stratix II/III ALM (1)

 - New and far more flexible Logic Element, now called Adaptive Logic Modules (ALMs)
- Each ALM contains a variety of (look-up table) LUT-based resources which can implement functions with up to 7 inputs and complex logic-arithmetic functions







Altera's Stratix II/III ALM (2)

Example	Description
	The logic structure in Stratix II devices can implement two independent 4-input (or smaller) LUTs (4-LUT) per ALM. This configuration is "backward-compatible" and ideal for migrating a design that is optimized for traditional 4-input LUT FPGAs to the Stratix II device family.
	Stratix II ALMs can implement a 5-input LUT (5-LUT) and a 3-input LUT (3-LUT) per ALM. The inputs to the two LUTs are independent of each other. The 3-input LUT can be used to implement any logic function that has three or fewer inputs. Therefore, a 5-input LUT and 2-input LUT are also allowed.
	The ALMs within the Stratix II architecture can be configured to implement a 5-input LUT and a 4-input LUT per ALM. One of the inputs must be shared between the two LUTs. The 5-input LUT has up to four independent inputs. The 4-input LUT has up to three independent inputs. The sharing of inputs between LUTs is very common in FPGA designs, and Quartus® II software will automatically seek logic functions that are structured in this manner.

Source: ALTERA


Altera's Stratix II/III ALM (2)

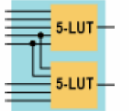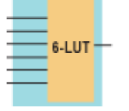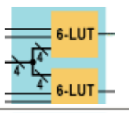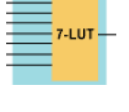	Stratix II ALMs can implement two 5-input LUTs per ALM. In this case, two of the inputs between the LUTs are common and up to three independent inputs are allowed for each 5-input LUT.
	Stratix II ALMs support any 6-input logic function per ALM. If there are two 6-input functions that have the same logic operation and four shared inputs, then these two 6-input functions can be implemented in one Stratix II ALM.
	For example, a 4x2 crossbar switch that has four data input lines and two sets of unique select signals requires 4 LEs in a Stratix device. In a Stratix II device, this same function only consumes one ALM. In another example, a single Stratix II ALM can implement two 6-input AND gates that have four common inputs. The same function in a Stratix device requires three LEs.
	In the extended mode, the Stratix II logic structure can perform certain logical functions with up to 7 inputs per ALM. Quartus II software can automatically recognize the applicable 7-input function and fit it into an ALM. For detailed information about the types of 7-input functions that can be implemented within an ALM, refer to the Stratix II Device Handbook .

Source: 

ALM in Arithmetic Mode

 
- Each ALM can also be turned into TWO 3-bit, cascadable fast adders



Source: 

Xilinx's Virtex-5 CLB

 
- Xilinx took a different approach with fixed, larger LUTs
- Each CLB has two slices
- Each slice has FOUR 6-input LUTs
- Retain fast look-ahead carry logic
- Better intra-CLB routing



Source: 

Virtex-5 Slice can be configured as memory

 
- Two types of slices
 - SLICE_L: Logic only
 - SLICE_M: Logic / RAM / ShiftReg
- Logic-to-memory ratio optimized for area and power
 - Some CLBs with two SLICE_Ls
 - Some CLBs with one SLICE_L plus one SLICE_M



Source: 

Xilinx's New 6-Input LUT with Two Outputs

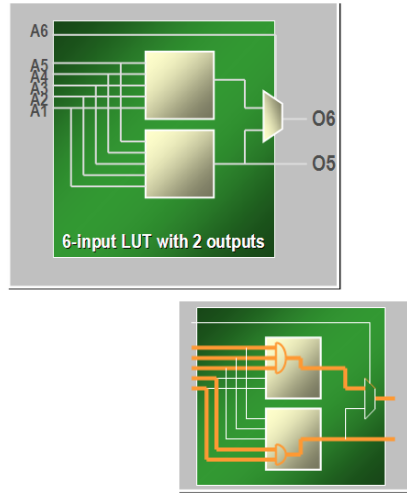
- ◆ True 6-input LUT
 - Any function of 6 variables
 - No input shared with other LUTs
- ◆ Second output adds functionality
 - Reduces average slice count by 10%
 - 2 independent functions of 5 variables
 - 1 function of 6 variables plus 1 subfunction of 5 variables
 - 1 function of 3 variables plus 1 function of 2 other variables
 - Plus other combinations of subfunctions...



Source: XILINX®

Why 6-Input LUT?

- ◆ Xilinx invented the LUT architecture
 - LUT4 has been the de-facto FPGA standard since 1988
- ◆ But:
 - Transistors got smaller
 - LUTs became a relatively smaller part of the overall logic
 - Interconnect got more significant in area and speed
- ◆ Time to re-evaluate the architecture
 - Research shows that a LUT6 is optimal for 65-nm
 - Slightly bigger LUT, compensated by significant savings through logic compaction and reduced routing

 

Source: XILINX®


Examples of LUT6 Efficiency

	Virtex-4 LUTs	Virtex-5 LUTs	% Reduction
16-input MUX	8	4	50%
MicroBlaze 32x32-bit register file, 2 read ports	384	44	89%
64x16 bit RAM	64	16	75%
Ternary adder 32bis wide	64	32	50%
Opencores triple-DES decryptor	1232	834	33%
Opencores discrete cosine transform	217	186	9%
Opencores Huffman decoder	672	463	32%
Opencores Huffman encoder	270	209	23%
Opencores_VGA_LCD	1369	993	28%
16-state FSM, 4-way branch, 6 encoded outputs	-	8	-
32x32-bit Quad-Port memory (1 write + 3 read)	-	64	-

Source: XILINX®

One LUT6 Equals 1.6 Logic Cells

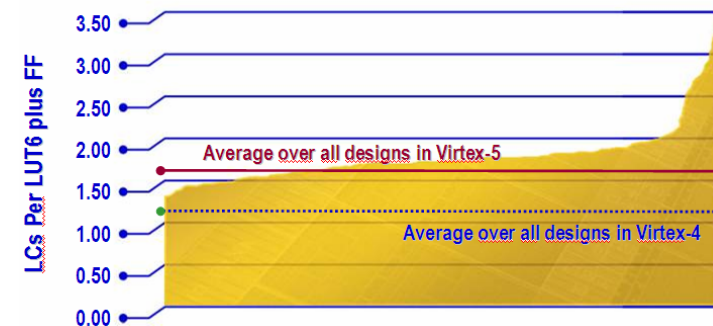
- ◆ LC has become an industry standard of measuring FPGA capacity
 - 10 years ago, a LC was defined as a LUT4 plus a flip-flop
- ◆ Extensive testing with 163 benchmark designs shows that the LUT6 plus FF is equivalent to ~1.6 LCs (old 4-LUT logic cells)



Source: XILINX®

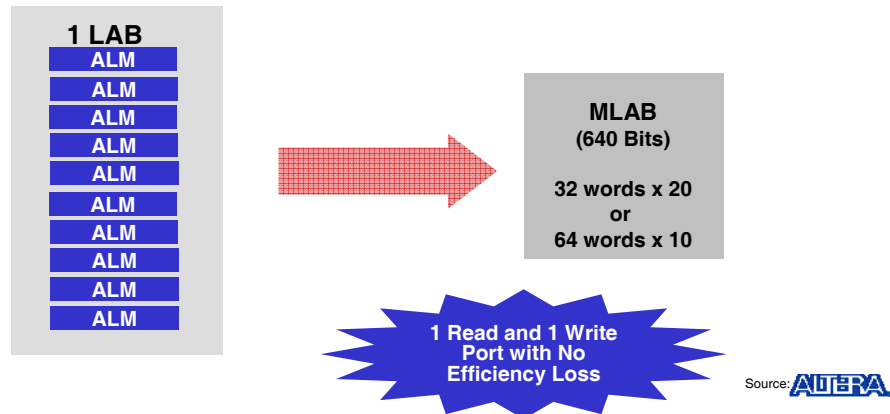2. Flexible and more on-chip memories: Altera

- ◆ For Stratix III, 10 ALM for 1 Logic Array Block (LAB).
- ◆ 50% of LABs in a Stratix III FPGA can be converted to a memory LAB (MLAB) with 640 bit of storage.
- ◆ This can be used as dual port memory (1 Read + 1 Write port).



Xilinx has even more flexibility to turn LUT to memory


- ◆ Single port
 - One LUT6 = 64x1 or 32x2 RAM
 - Cascadable up to 256x1 RAM in one CLB
- ◆ Dual port (D)
 - 1 read/write port + 1 read port
- ◆ Simple dual port (SDP)
 - 1 write-only port + 1 read-only port
 - Used in LUT FIFOs, and is also key to Microblaze register file.
- ◆ Quad-port (Q)
 - 1 read/write port + 3 read-only port

LUT RAM Primitives			
Single Port	Dual Port	Simple Dual Port	Quad Port
32x2			
32x4			
32x6			
32x8	32x2D		
64x1	32x4D	32x6SDP	32x2Q
64x2	64x1D	64x3SDP	64x1Q
64x3	64x2D		
64x4	128x1D		
128x1			
128x2			
256x1			

Source: XILINX®

Xilinx: Quad-Port Memory in One SLICE_M

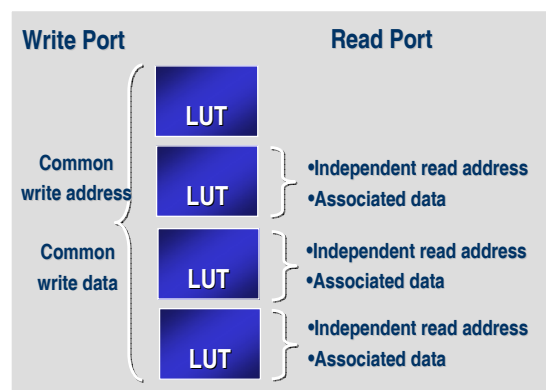- ◆ Write Port: Four LUT6s can share the write address and data
- ◆ Read Ports: Three independent read operations
- ◆ Provides 6x improvement in density over Virtex-4




New modes for distributed memory that did not exist before

Source: XILINX®


32-bit Shift Registers in 1 LUT

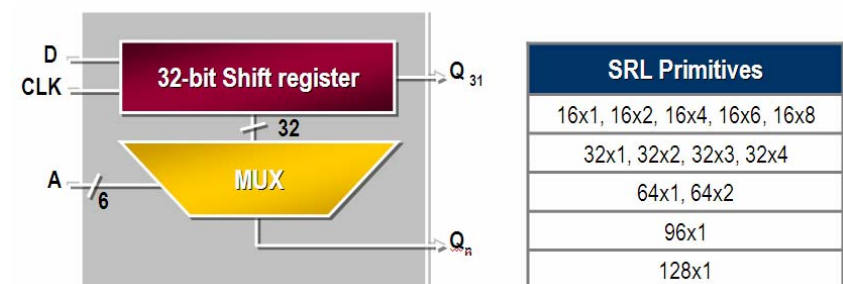- ◆ Each bit uses 2 latches as master/slave
- ◆ Length is dynamically determined by the A inputs
- ◆ Cascadable up to 128x1 shift register in one CLB




Source: XILINX®

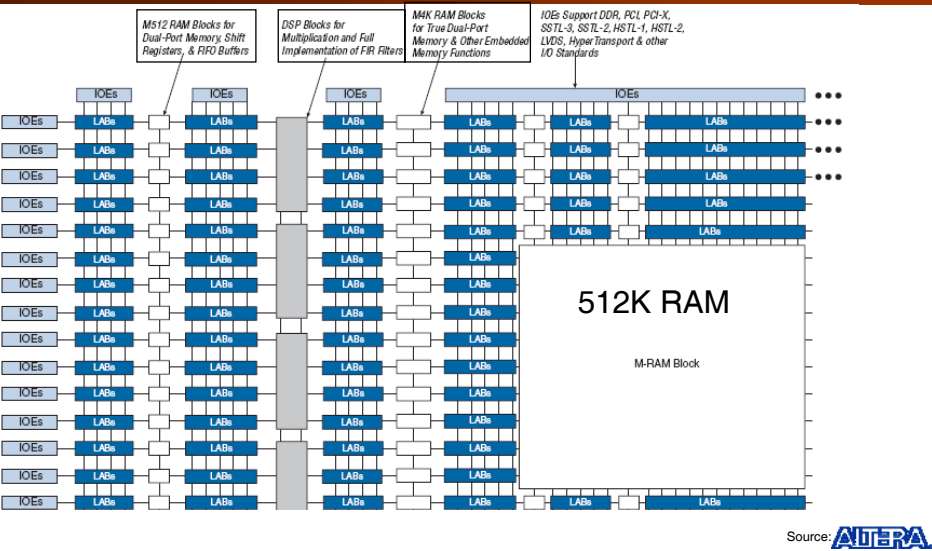
3. Faster computation with embedded DSP blocks




Stratix II DSP Blocks

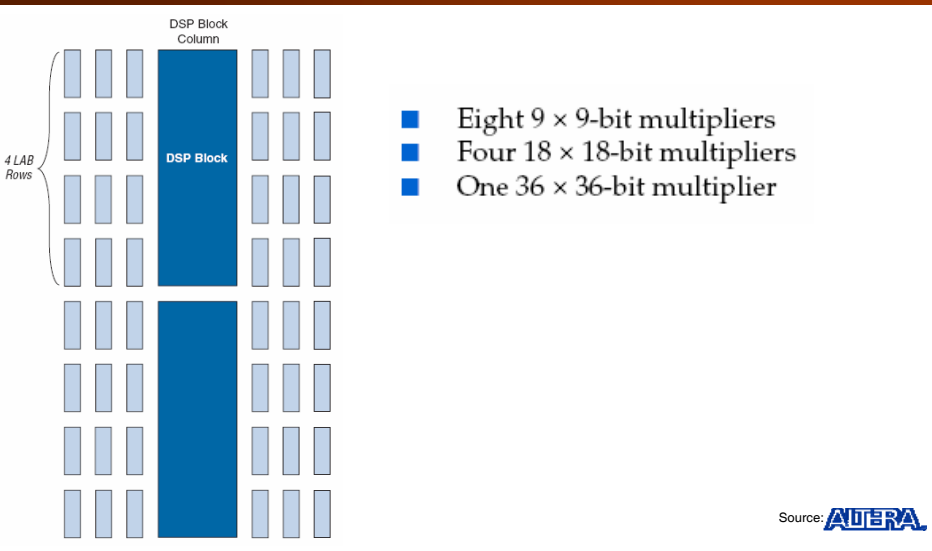

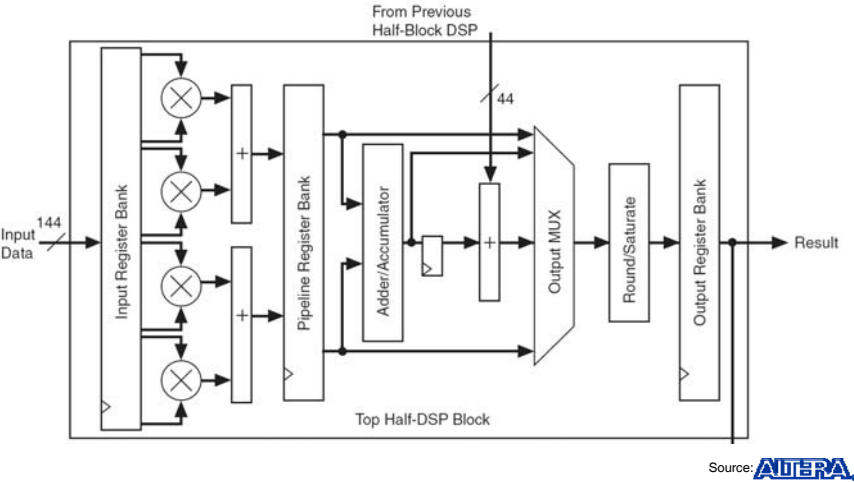Stratix III DSP Blocks are twice the size




Xilinx's Virtex 5 DSP Block

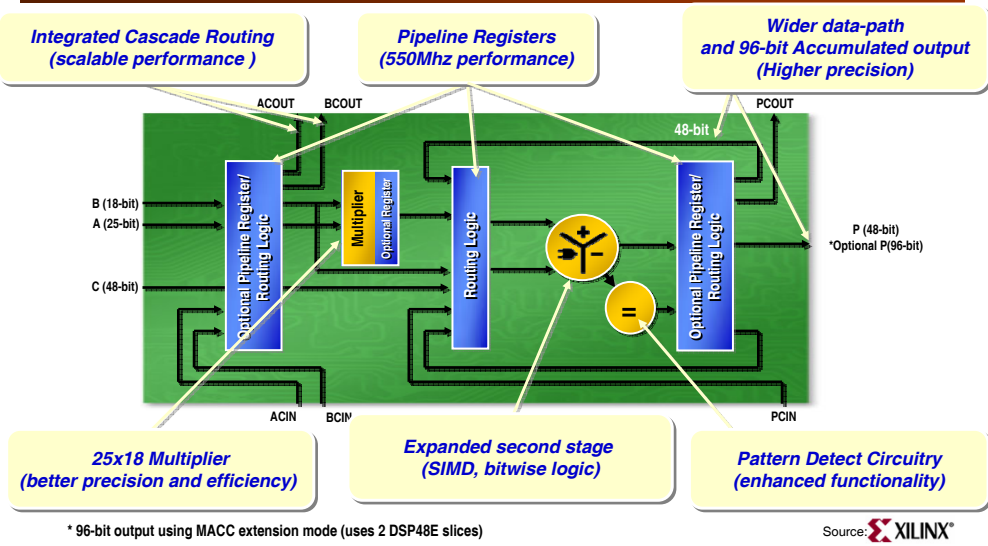

 4. Reduced routing delay and improved performance

◆ Altera's Stratix III - Minimizing number of hops critical for:

- Achieving high performance for faster timing closure
- Reducing fitting congestion




Hops	Reachable LEs
1	850
2	2,400
3	4,000
Total	7,250

Source: ALTERA

Xilinx's Virtex-4 routing

- Fast Connect
- 1 Hop
- 2 Hops
- 3 Hops

 

□ 1 CLB


Interconnects can be bottlenecks in demanding designs

Source: XILINX

Virtex-5 has More and Faster Routing Between CLBs

Symmetric routing pattern reaches more CLBs with fewer hops

- Fast Connect
- 1 Hop
- 2 Hops
- 3 Hops

 

□ 1 CLB

Dramatically increases design performance

Source: XILINX

Result: Shorter Routing Delays

Average delays from the input of the center CLB to inputs of any other CLB



	Virtex-4	Virtex-5	Improvement
1 st Ring	751 ps	665 ps	13 %
2 nd Ring	906 ps	723 ps	25 %

Source: XILINX

5. Lower Power – the 65nm Power Challenge


Cause	Effect
<div>↓ Transistor Size</div> <ul style="list-style-type: none">• Migration from 90nm to 65nm• Driven by lower cost	<div>↑ Leakage</div> <ul style="list-style-type: none">• Thinner oxide, shorter channel transistors have more leakage
<div>↑ Speed</div> <ul style="list-style-type: none">• Increased FPGA performance invites higher clock rate• Up to 50% faster than Virtex-4	<div>↑ Dynamic</div> <ul style="list-style-type: none">• Higher frequency = more power• CV^2f
<div>↑ Density</div> <ul style="list-style-type: none">• Greater logic capacity• Up to 65% more logic than Virtex-4	<div>↑ Dynamic</div> <ul style="list-style-type: none">• More logic per device = more power per device• More nodes switching

- ◆ On the positive side: operating voltage (V) and node capacitance (C) decrease with process shrink, lowering Dynamic Power (CV^2f)


Source: XILINX®

 Question: How fast should logic be?

- ◆ Only a small proportion of logic is performance critical



 
Altera's Programmable Power Technology (1)



- ◆ Could make all logic fast (and high power)
- ◆ Critical path shown in red

Source: ALTERA


Programmable Power Technology

 

- ◆ Better if only critical path logic are high speed
- ◆ The rest are low-power (and low speed)

Source: ALTERA

Programmable Power Technology

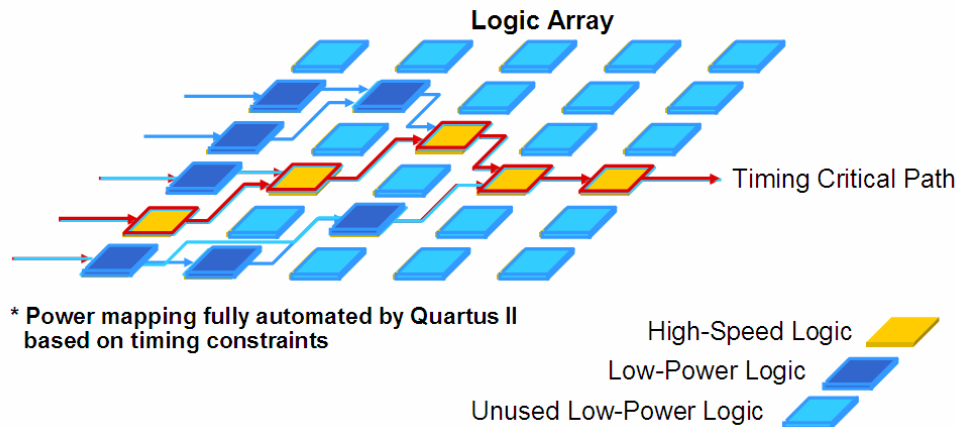

* Power mapping fully automated by Quartus II based on timing constraints

High Performance Where You Need It, Lowest Power Everywhere Else

Source: ALTERA

Stratix III has Selectable Core Voltage


- Customer selects the FPGA core voltage
 - 1.1 V for maximum performance
 - 0.9 V for minimum power
- I/O and PLL voltages unaffected
 - Still get maximum I/O interface speed

Core Voltage	Dynamic Power Reduction From Stratix II FPGAs	Static Power Reduction From Stratix II FPGAs	Performance Gain Over Stratix II FPGAs
1.1 V	33%	52%	25%
0.9 V	55%	64%	0%


Total Power Reduction reflects reduced capacitance, Programmable Power Technology, and other Stratix III architectural optimizations

Source: ALTERA

Static Power Tamed (85 degree C)

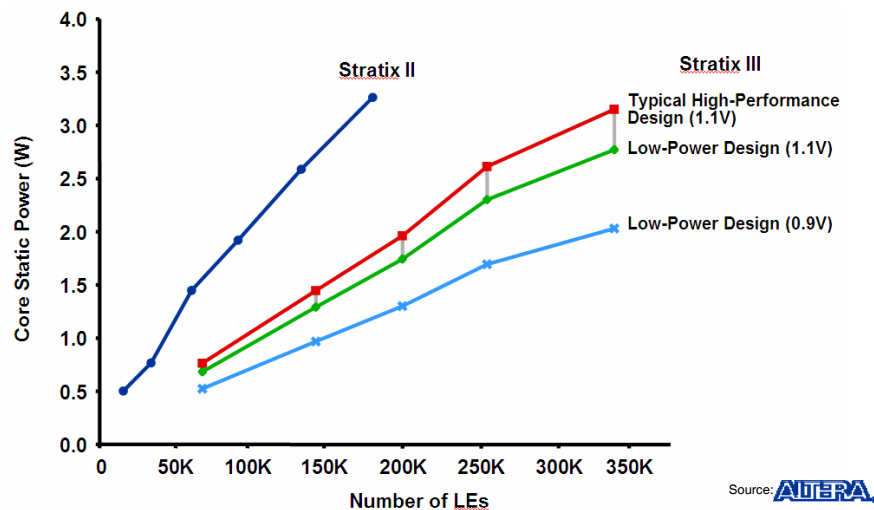


Xilinx focus on Leakage Current at 65nm

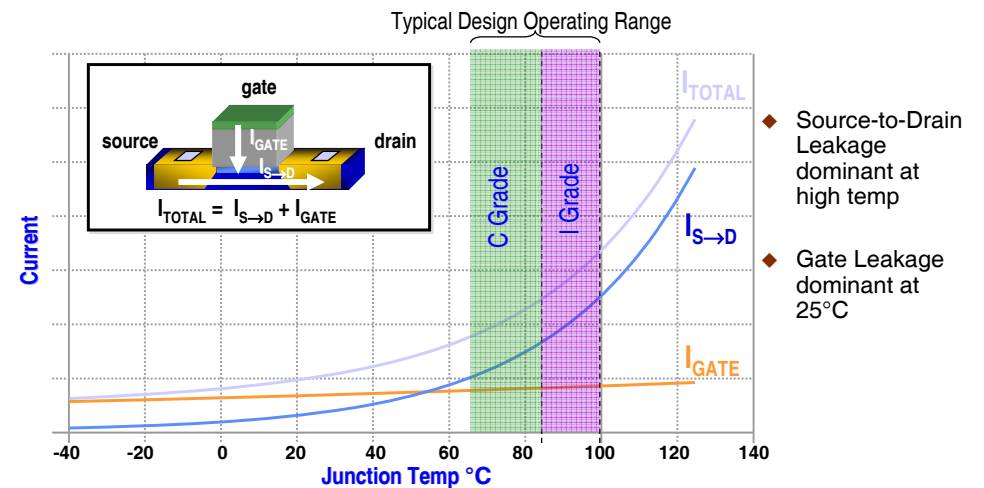

Source: XILINX

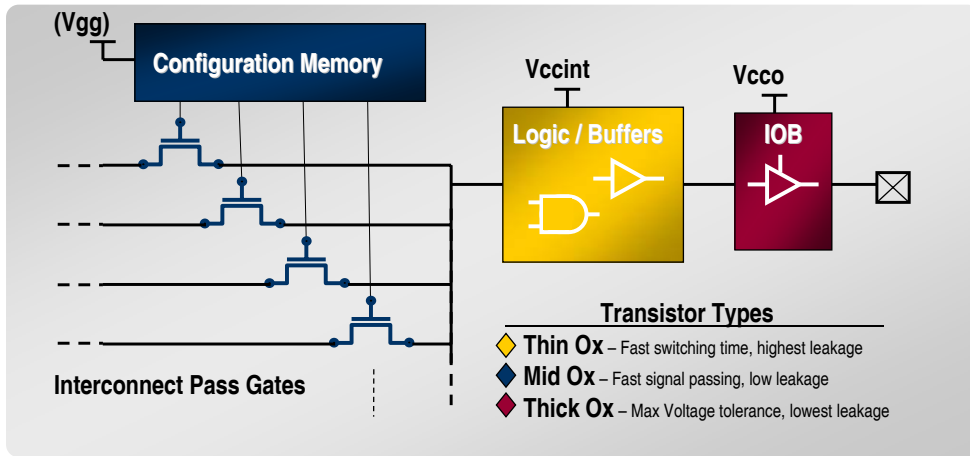Xilinx's way to Optimize Speed and Leakage



No Compromise on Performance

Source:  XILINX®

References & Addition Reading

- ◆ J. Rose, R.J. Francis, D. Lewis and P. Chow, "Architecture of Field-Programmable Gate Arrays: The Effect of Logic Functionality on Area Efficiency", IEEE Journal of Solid-State Circuits, pp. 1217-1225, 1990.
- ◆ Altera Stratix III information:
 - <http://www.altera.com/literature/lit-stx3.jsp>
- ◆ Xilinx Virtex-4 information:
 - http://www.xilinx.com/products/silicon_solutions/fpgas/virtex/virtex4/index.htm
- ◆ Xilinx Virtex-5 information:-
 - http://www.xilinx.com/products/silicon_solutions/fpgas/virtex/virtex5/index.htm