

IMPERIAL COLLEGE OF SCIENCE TECHNOLOGY AND MEDICINE
UNIVERSITY OF LONDON

DEPARTMENT OF ELECTRICAL AND ELECTRONIC ENGINEERING
M.Eng. and A.C.G.I. EXAMINATIONS 2004

PART IV

INTRODUCTION TO DIGITAL IC DESIGN

<p><i>SOLUTIONS</i></p>



This is an open-book examination.

You may need red, green, blue, yellow and black coloured pens.

First Marker: *Peter Cheung*
Second Marker: *Thomas Clarke*

Solution to Question 1

  - a) This question tests student's ability to understand a full custom layout. This is a special cell for asynchronous systems, known as the Muller-C element with an extra inverter. Students do not need to know the circuit in order to answer this question.




T3 T5 T7


T2 T4 T6 T8

[12 marks]

 - b) This part of the question tests student's ability to relate the layout to the physical process and different layers on the chip.



[4]

 

poly

[4]

[8 marks]

metal1
oxide

poly

P+

P+

P+

P+

P-diff


Solution to Question 2 (corrected)

a)

Address	ROM Content
0	0000
1	1111
2	0101
3	1010


[6 marks]

b)

 

[8 marks]


c)

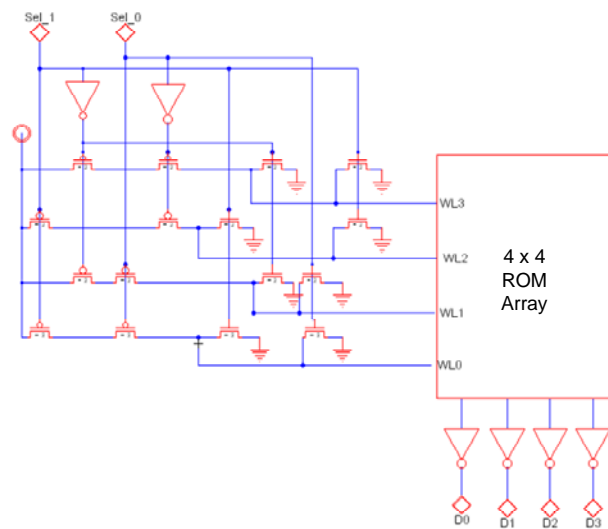

[6 marks]

Solution to Question 3


- (a) When clock CLK is low, the flip-flop is in the precharge phase. Node X is precharged to the level of the power supply, and node Q holds its previous value. On the rising edge of the clock, the flip-flop enters the *evaluation phase*. Here two periods are distinguished. In the first period when CLK is high, but Y is also high, it corresponds to an active clock pulse to the circuit and the circuit is in the *sampling* (or transparent) mode. The value of output Q is determined by the value of input D. Once the internal node X is discharged, due to its precharge nature, it will stay low until the next clock cycle. In the second period, the pulse is inactive. The sampling of D is disabled, so X and Q will retain the values they acquired during the sampling period. Notice that any subsequent change at D after the sampling period will have no effect on Q.

 **[10 marks]**

- (b) The shortcomings of this circuit are (any two of the three here will do):
1. Internal node X is a dynamic node and therefore this circuit will not work at low frequency.
 2. Output Q is in high impedance when the clock signal CLK is low.
 3. The timing of the sampling window T_{on} is critical: too short a T_{on} could lead to metastability or functional failure because the sampling window is too short to correctly evaluate the input. Too long a T_{on} may cause poor performance by imposing a long hold time.


[4 marks]

(c)

 **[6 marks]**

Solution to Question 4

a)

 

- (i) Out of the 4 paths shown in the figure, p1 is the critical one and determines the lower bound on the clock period. Using $T \geq t_{\text{reg}} + t_{\text{logic}} + t_{\text{setup}} - \delta$, we get **$T_{\text{min}} = 1 + 7 + 1 = 9$** . [4 marks]
- (ii) As the clock skew increases, the most significant path changes. Repeating the calculations in part (i) we get : $T_{\text{min}}(p1) = 9 - 4 = 5$, $T_{\text{min}}(p2) = 6$, $T_{\text{min}}(p3) = 7$, $T_{\text{min}}(p4) = 7 - 4 = 3$. (Note that the clock skew is 0 for paths p2 and p3). Therefore the minimum clock period is $T_{\text{min}} = 7$. [4 marks]
- b) (i) Gate width of minimum size inverter is $0.75 \mu\text{m}$. $t_d = 30\text{ns}$. Therefore, the Electrical Effort (and total effort F) for the two paths are:

$$F_{P1} = 900 / 0.75 = 1200; F_{P2} = 100 / 0.75 = 133;$$

$$\text{Delay estimates of the two paths are: } D_{P1} = 1200 * t_d = 36 \text{ ns}; D_{P2} = 133 * t_d = 4 \text{ ns}$$

$$\text{P1-P2 skew} = 1067 * t_d = 32 \text{ ns.}$$

(ii)

Total effort F for $P1 = 1200$, $P2 = 133$. Best number of stages (from notes) is given by:
$$N_{\text{best}} = \log(F) / \log(3.59). N_{P1} \approx 5.5, N_{P2} \approx 3.8. P1 \text{ should be buffered by 6 inverter stages, } P2 \text{ also by 4 stages. Therefore}$$

For P1, each stage should increase in size by $\sqrt[6]{1200} = 3.26$,
for P2, each stage should increase in size by $\sqrt[4]{133} = 3.4$.

Solution – increase sizes of p-trans and n-trans by these factors for each of the stages:

Stage	1	2	3	4	5	6
P1:	x 1	x 3	x 10	x 35	x 113	x 368
P2:	x 1	x 3	x 12	x 39		

$$P1 \text{ delay} \approx (3/1 + 10/3 + 35/10 + 113/35 + 368/113 + 1200/368) * t_d = 22.5 t_d$$

$$P2 \text{ delay} \approx (3/1 + 12/3 + 39/12 + 133/39) * t_d = 13.7 t_d$$

$$\text{Clock skew} \approx 8.8 * t_d$$

[7 marks]

Solution to Question 5 (corrected)

a)

a_j	b_j	c_{j+1}	d_{j+1}
0	0	c_i	d_i
0	1	c_i	c_i
1	0	d_i	d_i
1	1	c_i	d_i

[5 marks]

b) Design of the layout depends on student. Marks will be deducted if the layout is inefficient or contains excessive unnecessary crossovers.

[7 marks]

c)

$$c_j = (a_j > b_j), \text{ and } d_j = (a_j = b_j)$$

$C0 = '0'$, $D0 = '1'$ indicating that we assume $A=B$ to start.

$C4 = (A > B)$, $D4 = (A = B) + (A > B)$.

Therefore:

Case	C4	D4
$A > B$	1	1
$A = B$	0	1
$A < B$	0	0

[4 marks]

d) (i)

j	0	1	2	3	4
A	1	0	1	1	-
B	0	0	1	1	
C	0	1	1	1	1
D	1	1	1	1	1

(ii)

j	0	1	2	3	4
A	0	1	1	1	-
B	1	0	1	1	
C	0	0	0	0	0
D	1	0	0	0	0

(iii)

j	0	1	2	3	4
A	1	0	0	1	-
B	1	0	0	1	
C	0	0	0	0	0
D	1	1	1	1	1

[4 marks]

Solution to Question 6

a)

$$Y = \text{NOT } (A * B + C * D)$$

[4 marks]

b) $\lambda = 0.25\mu$ Then all lengths are 1λ . In order to ensure worst case rise and fall time to be roughly the same, all n-trans use 4λ width, and all p-trans 8λ width.

[4 marks]

c) Use Boolean difference method:

$$\begin{aligned} Y(B=0) &= Y(A, 0, C, D) = \text{NOT}(C * D) \\ Y(B=1) &= Y(A, 1, C, D) = \text{NOT}(A + C * D) \end{aligned}$$

Therefore Boolean difference is:

$$\begin{aligned} dY/dB &= Y(B=0) \text{ XOR } Y(B=1) \\ &= \text{NOT}(C * D) \text{ XOR } \text{NOT}(A + C * D) \\ &= A * \text{NOT}(C) + A * \text{NOT}(D) \end{aligned}$$

To test for stuck-at-0 fault at B,

test input	= B*(dY/dB),
	= A*B*NOT(C) + A*B*NOT(D) = 1

Therefore the test vector for B stuck-at-0 = 110x and 11x0, i.e. (1100, 1101, 1110)

To test for stuck-at-1 fault at B,

test input	= NOT(B)*(dY/dB),
	= A*NOT(B)*NOT(C) + A* NOT(B)*NOT(D) = 1

Therefore the test vector for B stuck-at-1 = 100x and 10x0, i.e. (1000, 1001, 1010)

[5 marks]

d) If $B = \text{NOT}(C)$, then we can use the cell as a MUX between A and D inputs.

[7 marks]

