

Lecture 11 Pass Transistor Logic

Peter Cheung
Department of Electrical & Electronic Engineering
Imperial College London

Reading: "Top-Down Pass-Transistor Logic Design", K. Yano etc., IEEE J. of Solid-State Circuits, Vol 31, No. 6, June 1996.

URL: www.ee.ic.ac.uk/pcheung/
E-mail: p.cheung@ic.ac.uk


Recent development in PTL

- New development by designers at Hitachi Japan in the last 6 years.
- Three circuit styles proposed:
 - Complementary Pass-transistor Logic (CPL), 1990
 - Double Pass-transistor Logic (DPL), 1993
 - Lean Integration with Pass-transistors (LEAP), 1996
- All exploit pass-transistors to implement general logic functions

Complementary Pass-transistor Logic (CPL)

- ◆ "A 3.8 ns CMOS 16 x 16b Multiplier Using Complementary Pass-Transistor Logic" by K. Yano etc., IEEE J. of Solid-state Circuits, Vol 15, No 2, April 1990.
- Logic network employs input signals at both gate and drain terminals.
- Inputs and Outputs are always complementary.
- Outputs from network provide strong '0's but weak '1's. Inverters and PMOS pull-ups provide amplification and buffering as necessary.

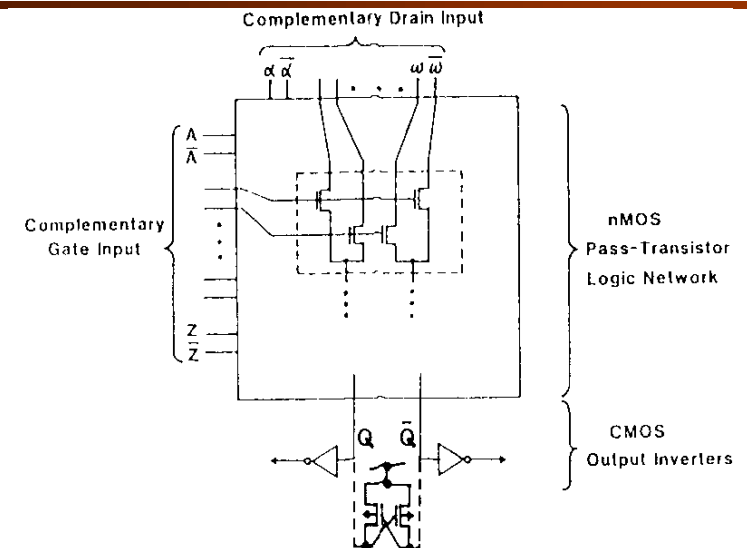Complementary Pass-transistor Logic (CPL)



Basic gates designed in CPL

Circuit				
Logic Function				


3-input gates designed in CPL

Circuit			
Logic Function			

CPL based 1-bit full adder

	CMOS	CPL
Full Adder Circuit		
Transistor Count	40	28
Area	4730μm ²	4218 μm ²
Delay (4V)	0.63ns	0.26ns
Power (100MHz)	1.2mW	0.86mW

Advantages of CPL

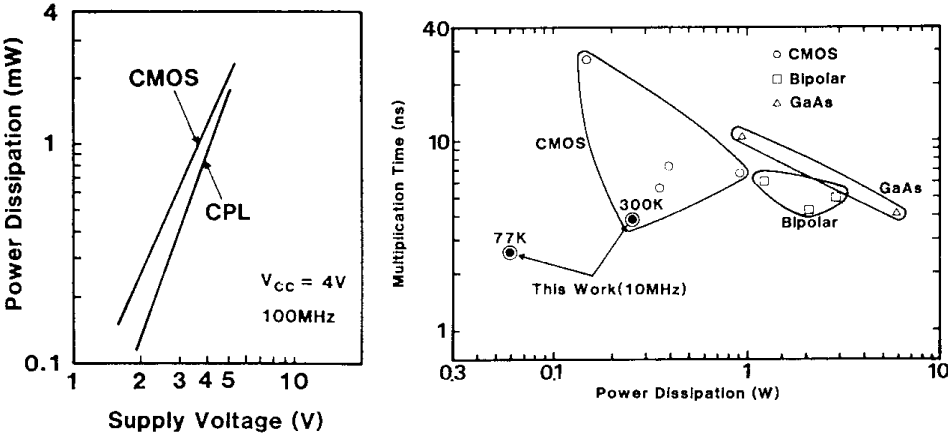


Double Pass-transistor Logic (DPL)

- ♦ "A 1.5-ns 32-b CMOS ALU in Double Pass-Transistor Logic", M. Suzuki etc., IEEE J. of Solid-State Circuits, Vol 28, No 11, Nov., 1993

	CPL	CMOS	DPL																																																												
Circuit																																																															
Truth Table & Operation	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>XOR</th><th>Pass</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>B</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>B</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>\bar{B}</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>\bar{B}</td></tr> </tbody> </table>	A	B	XOR	Pass	0	0	0	B	0	1	1	B	1	0	1	\bar{B}	1	1	0	\bar{B}	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>XOR</th><th>Pass</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>B</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>B</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>\bar{B}</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>\bar{B}</td></tr> </tbody> </table>	A	B	XOR	Pass	0	0	0	B	0	1	1	B	1	0	1	\bar{B}	1	1	0	\bar{B}	<table border="1"> <thead> <tr> <th>A</th><th>B</th><th>XOR</th><th>Pass</th></tr> </thead> <tbody> <tr><td>0</td><td>0</td><td>0</td><td>$\frac{B+\bar{B}}{2}$</td></tr> <tr><td>0</td><td>1</td><td>1</td><td>$\frac{B+\bar{B}}{2}$</td></tr> <tr><td>1</td><td>0</td><td>1</td><td>$\frac{B+\bar{B}}{2}$</td></tr> <tr><td>1</td><td>1</td><td>0</td><td>$\frac{B+\bar{B}}{2}$</td></tr> </tbody> </table>	A	B	XOR	Pass	0	0	0	$\frac{B+\bar{B}}{2}$	0	1	1	$\frac{B+\bar{B}}{2}$	1	0	1	$\frac{B+\bar{B}}{2}$	1	1	0	$\frac{B+\bar{B}}{2}$
A	B	XOR	Pass																																																												
0	0	0	B																																																												
0	1	1	B																																																												
1	0	1	\bar{B}																																																												
1	1	0	\bar{B}																																																												
A	B	XOR	Pass																																																												
0	0	0	B																																																												
0	1	1	B																																																												
1	0	1	\bar{B}																																																												
1	1	0	\bar{B}																																																												
A	B	XOR	Pass																																																												
0	0	0	$\frac{B+\bar{B}}{2}$																																																												
0	1	1	$\frac{B+\bar{B}}{2}$																																																												
1	0	1	$\frac{B+\bar{B}}{2}$																																																												
1	1	0	$\frac{B+\bar{B}}{2}$																																																												
Swing	$0 \leftrightarrow (V_{cc} - V_{th})$	$0 \leftrightarrow V_{cc}$	$0 \leftrightarrow V_{cc}$																																																												

Basic gates in DPL

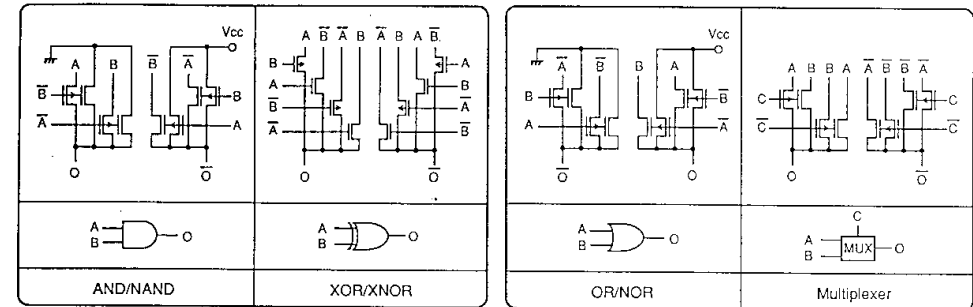


Why is DPL faster?


	CPL	CMOS	DPL
Current Path			
Equiv. Circuit			
Equiv. Resistance	$\frac{4}{3}R$	$\frac{3}{2}R$	R

Sum circuit in DPL

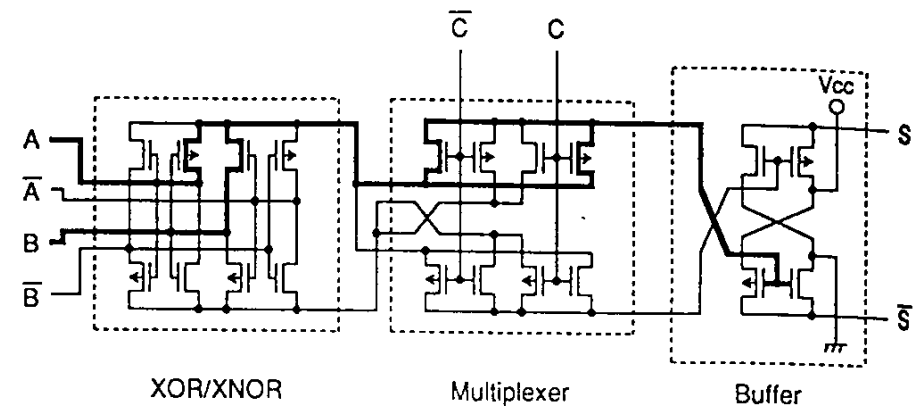- ♦ This adder circuit is extremely elegant. We have shown that for 0.6 micron technology, it offers up to 20% faster operating speed when compare with normal CMOS with only marginal increase in area.



Carry circuit in DPL

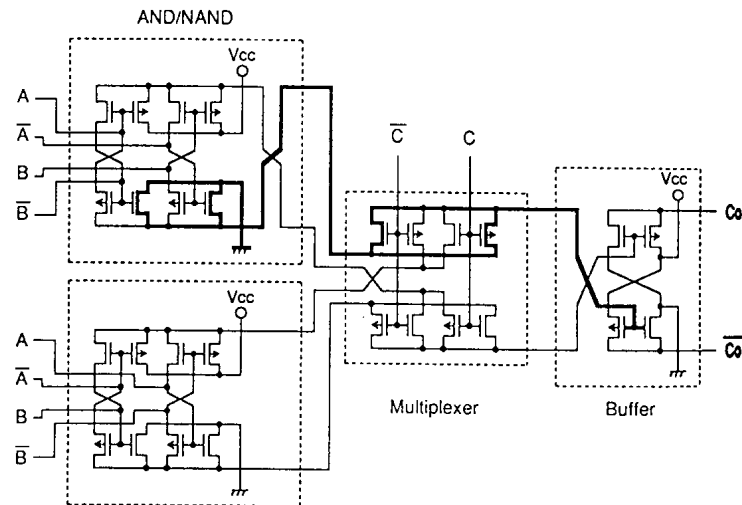


22-Feb-02

E4.20 Digital IC Design

Lecture 11 - 13

Power & Speed of DPL

 


22-Feb-02

E4.20 Digital IC Design

Lecture 11 - 14

Overall add time of DPL

 


22-Feb-02

E4.20 Digital IC Design

Lecture 11 - 15

Lean Integration with Pass-Transistor (LEAP)

 - ◆ "Top-Down Pass-Transistor Logic Design", K. Yano etc., IEEE J. of Solid-State Circuits, Vol 31, No. 6, June 1996.
- It eliminated the need for keeping a large cell library by replacing a library of 61 basic cells with a new set of THREE library cells called Y1, Y2 and Y3, and 4 inverters of different drive strength.



The gate width of nMOS are 6μm.


22-Feb-02

E4.20 Digital IC Design

Lecture 11 - 16

Inverters used in LEAP

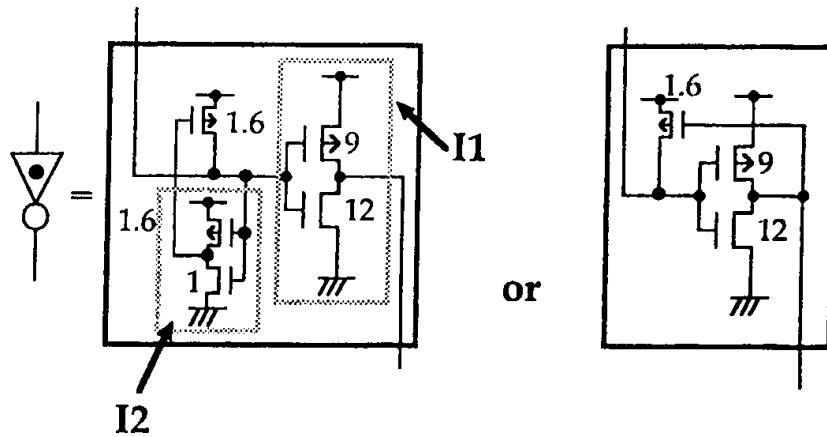- Note that the inverter on the left is used for driving very large output load and the right inverter for normal load capacitance.




Y2 can be configured for different logic

- Arbitrary logic circuits can be implemented at almost transistor level, not gate level.

Input configuration				
Boolean Expression	$F = ABC$	$F = ABC$	$F = AB\bar{C}D$	$F = BD\bar{B}E$

Speed of LEAP

 

CMOS vs LEAP

	Reported Circuits [18, 19]	Circuit Inventor (This Work)
Circuit Diagram		
Tr. Count	28 (1)	24 (0.86)
Area	1810 μm^2 (1)	1161 μm^2 (0.64)
Delay	0.73 ns (1)	0.32 ns (0.44)
Power	3.65 $\mu\text{W}/\text{MHz}$ (1)	2.35 $\mu\text{W}/\text{MHz}$ (0.64)
FOM*	1	6.5