

Topic 8

Sequential Circuits¹

Peter Cheung
Department of Electrical & Electronic Engineering
Imperial College London


Rabaey Chapter 7

URL: www.ee.ic.ac.uk/pcheung/
E-mail: p.cheung@ic.ac.uk

¹ Based on slides from Prentice-Hall


Mux-Based Latches

Negative latch
(transparent when CLK= 0)

 


$$Q = \overline{Clk} \cdot Q + Clk \cdot In$$

Positive latch
(transparent when CLK= 1)


 


$$Q = Clk \cdot Q + \overline{Clk} \cdot In$$

Mux-Based Latch

 


Mux-Based Latch

  

NMOS only

Non-overlapping clocks


Master-Slave (Edge-Triggered) Register

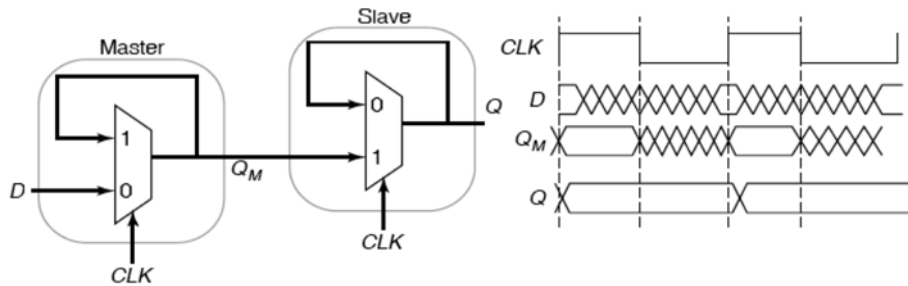


Two opposite latches trigger on edge
Also called master-slave latch pair

Master-Slave Register

Multiplexer-based latch pair

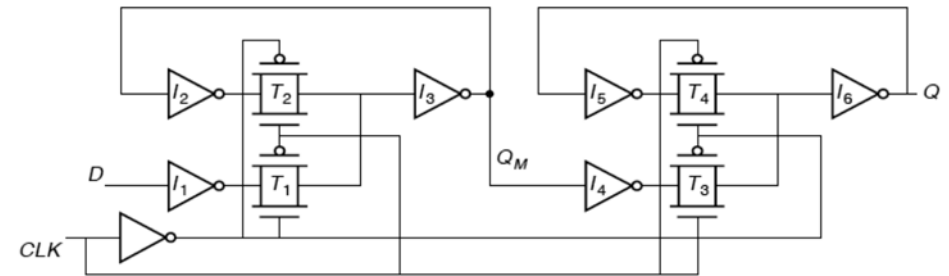


Reduced Clock Load Master-Slave Register

 



Overpowering the Feedback Loop — Cross-Coupled Pairs

NOR-based set-reset

 


Cross-Coupled NAND

Cross-coupled NANDs

  


This is not used in datapaths any more, but is a basic building block for memory cell

Sizing Issues

 

 
Output voltage dependence on transistor width




Transient response

Storage Mechanisms


Static

 



Dynamic (charge-based)

 

Making a Dynamic Latch Pseudo-Static


 


Master-Slave Static Flip-flop

 
 


- ◆ Overlapping Clocks Can Cause
 - Race Conditions
 - Undefined Signals



Two-phase dynamic flip-flop

  


Use 2-phase non-overlapping clocks

  

Latch + Logic

  


Other Latches/Registers: C²MOS

 

“Keepers” can be added to make circuit pseudo-static


Insensitive to Clock-Overlap

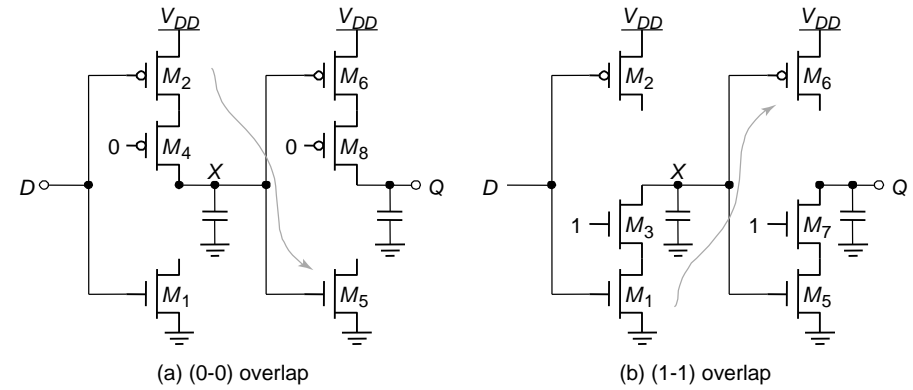

(a) (0-0) overlap

(b) (1-1) overlap

Pipelining

 


Reference

Clock Period	Adder	Absolute Value	Logarithm
1	$a_1 + b_1$		
2	$a_2 + b_2$	$ a_1 + b_1 $	
3	$a_3 + b_3$	$ a_2 + b_2 $	$\log(a_1 + b_1)$
4	$a_4 + b_4$	$ a_3 + b_3 $	$\log(a_2 + b_2)$
5	$a_5 + b_5$	$ a_4 + b_4 $	$\log(a_3 + b_3)$

Pipelined


Other Latches/Registers: TSPC

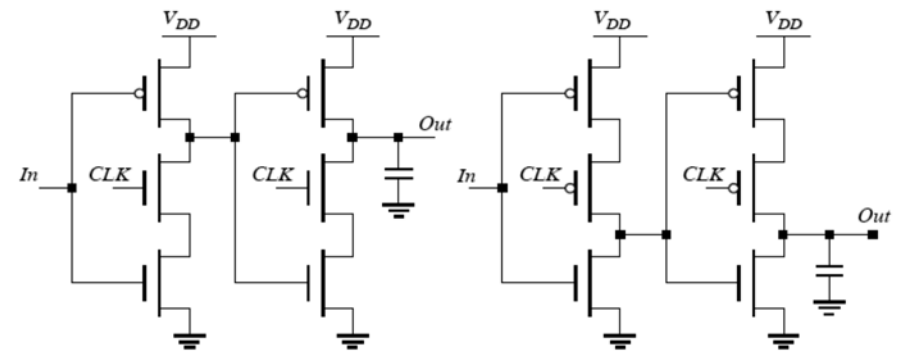


Positive latch
(transparent when CLK= 1)

Negative latch
(transparent when CLK= 0)

Including Logic in TSPC

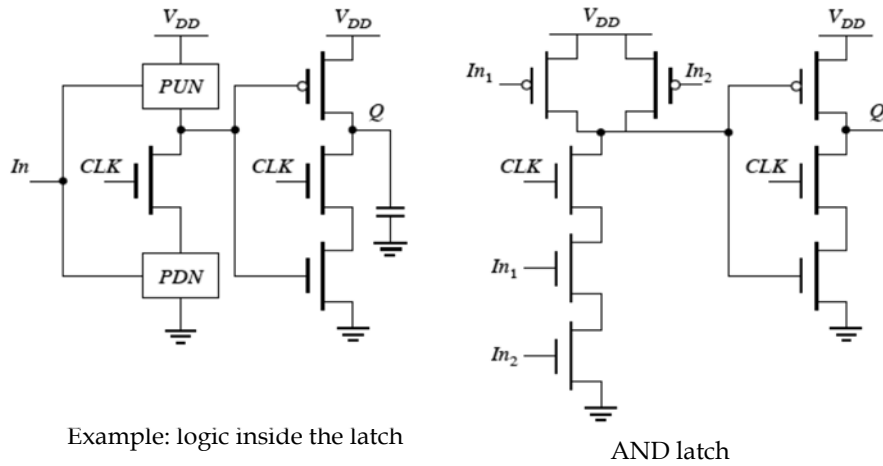


TSPC Register

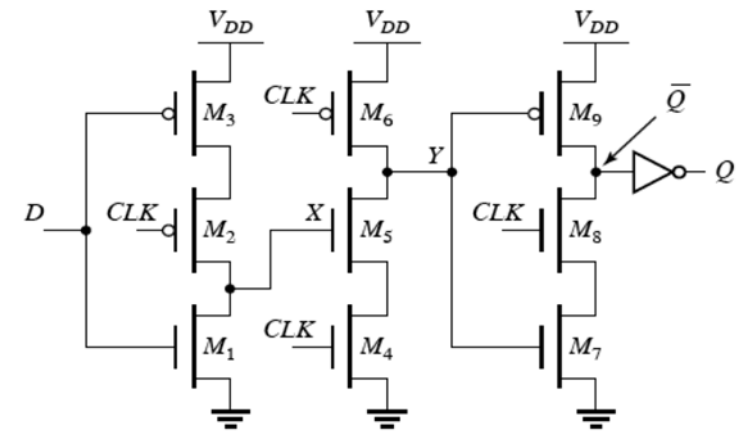


μ - π latches: Poor man's TSPC Latch


- What is wrong with this TSPC Latch?

 

- Second attempt:

 


μ - π latches Final solution

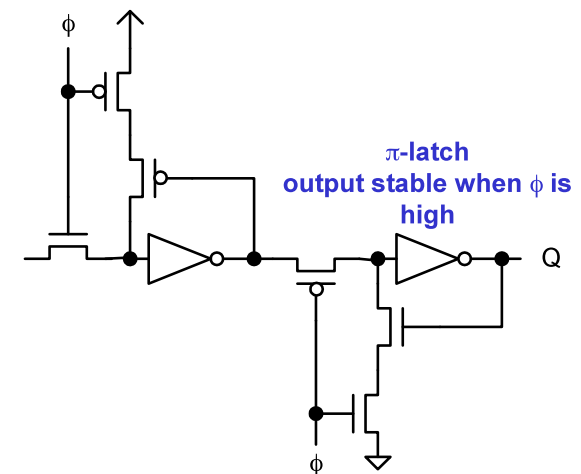


Pulse-Triggered Latches An Alternative Approach

Ways to design an edge-triggered sequential cell:


Master-Slave Latches

 

Pulse-Triggered Latch

 


Pulsed Latches

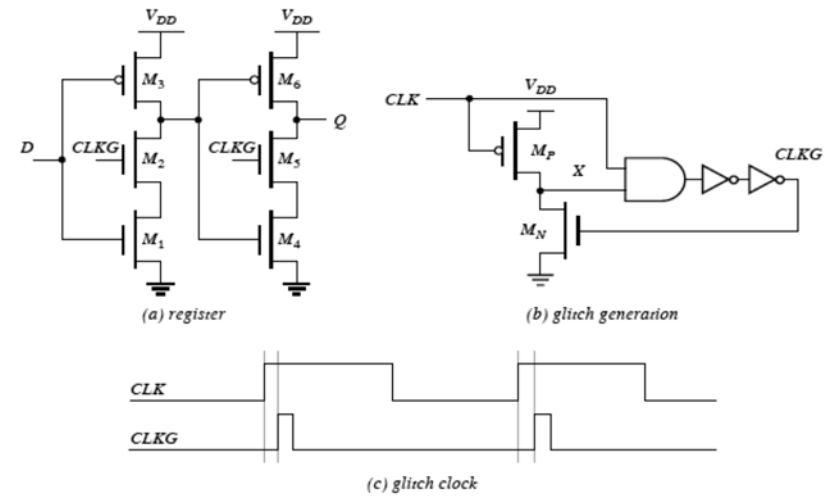


Pulsed Latches

 
Hybrid Latch - Flip-flop (HLFF), AMD K-6 and K-7 :




Hybrid Latch-FF Timing

 


Latch-Based Pipeline

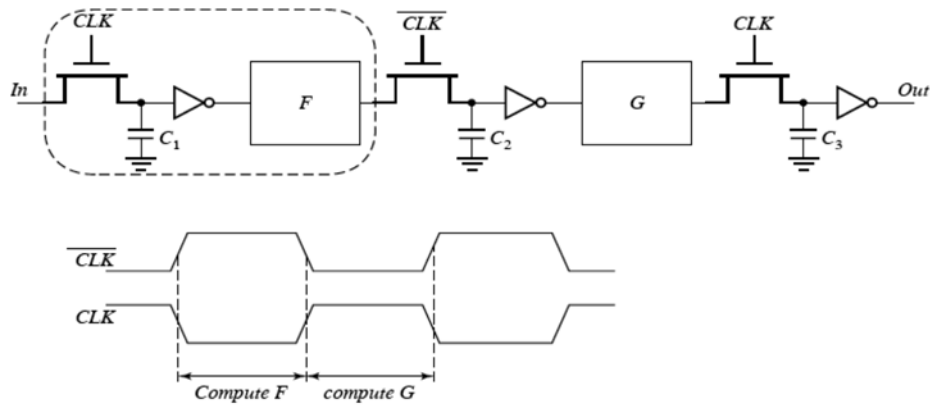

 
Non-Bistable Sequential Circuits— Schmitt Trigger



 
- VTC with hysteresis
- Restores signal slopes




Noise Suppression using Schmitt Trigger

 


CMOS Schmitt Trigger

 

Schmitt Trigger Simulated VTC

 


 Voltage-transfer characteristics with hysteresis.




The effect of varying the ratio of the PMOS device M_4 . The width is $k \cdot 0.5 \mu\text{m}$.

CMOS Schmitt Trigger (2)

 

Multivibrator Circuits

 


Bistable Multivibrator
flip-flop, Schmitt Trigger


Monostable Multivibrator
one-shot

Astable Multivibrator
oscillator


Transition-Triggered Monostable

 

Monostable Trigger (RC-based)

 


(a) Trigger circuit.

 



(b) Waveforms.

Relaxation Oscillator

 



$$T = 2 (\log 3) RC$$

Astable Multivibrators (Oscillators)

  


simulated response of 5-stage oscillator

Voltage Controller Oscillator (VCO)

  


propagation delay as a function of control voltage


Differential Delay Element and VCO

 

delay cell

 

two stage VCO

 

simulated waveforms of 2-stage VCO