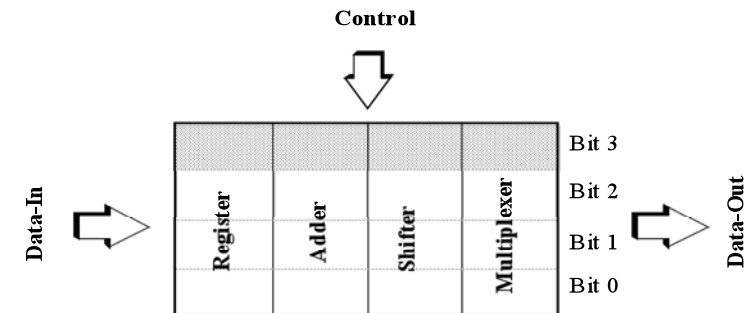


Topic 9 Arithmetic Circuits & Datapaths

Peter Cheung
Department of Electrical & Electronic Engineering
Imperial College London


URL: www.ee.ic.ac.uk/pcheung/
E-mail: p.cheung@ic.ac.uk

Bit-Sliced Design




Tile identical processing elements

Full-Adder

 

| A | B | C_i | S | C_o | Carry status |
|-----|-----|-------|-----|-------|--------------|
| 0 | 0 | 0 | 0 | 0 | delete |
| 0 | 0 | 1 | 1 | 0 | delete |
| 0 | 1 | 0 | 1 | 0 | propagate |
| 0 | 1 | 1 | 0 | 1 | propagate |
| 1 | 0 | 0 | 1 | 0 | propagate |
| 1 | 0 | 1 | 0 | 1 | propagate |
| 1 | 1 | 0 | 0 | 1 | generate |
| 1 | 1 | 1 | 1 | 1 | generate |

The Binary Adder

 

$$\begin{aligned}
 S &= A \oplus B \oplus C_i \\
 &= \overline{A}\overline{B}C_i + \overline{A}B\overline{C}_i + A\overline{B}\overline{C}_i + ABC_i \\
 C_o &= AB + BC_i + AC_i
 \end{aligned}$$

Express Sum and Carry as a function of P, G, D

Define 3 new variable which ONLY depend on A, B

Generate (G) = AB

Propagate (P) = A ⊕ B


Delete = A B

$$C_o(G, P) = G + PC_i$$

$$S(G, P) = P \oplus C_i$$

Can also derive expressions for S and C_o based on D and P

The Ripple-Carry Adder

 


Worst case delay linear with the number of bits

$$t_d = O(N)$$

$$t_{\text{adder}} \approx (N-1)t_{\text{carry}} + t_{\text{sum}}$$


Goal: Make the fastest possible carry path circuit

Complimentary Static CMOS Full Adder

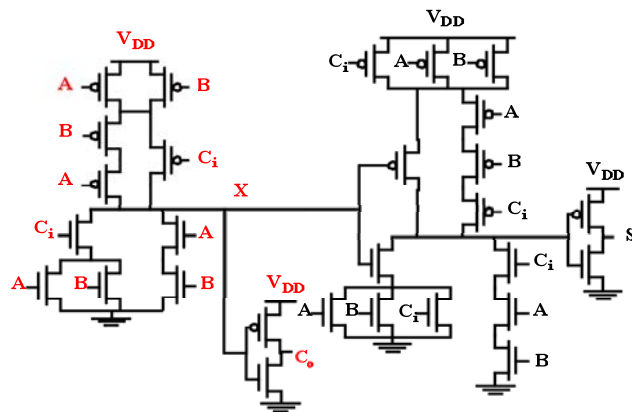

28 Transistors


Inversion Property

 

$$\bar{S}(A, B, C_i) = S(\bar{A}, \bar{B}, \bar{C}_i)$$

$$\bar{C}_o(A, B, C_i) = C_o(\bar{A}, \bar{B}, \bar{C}_i)$$

 Minimize Critical Path by Reducing Inverting Stages



Exploit Inversion Property


Note: need 2 different types of cells

The better structure: the Mirror Adder

Generate $(G) = AB$

Propagate $(P) = A \oplus B$

Delete = $\overline{A} B$

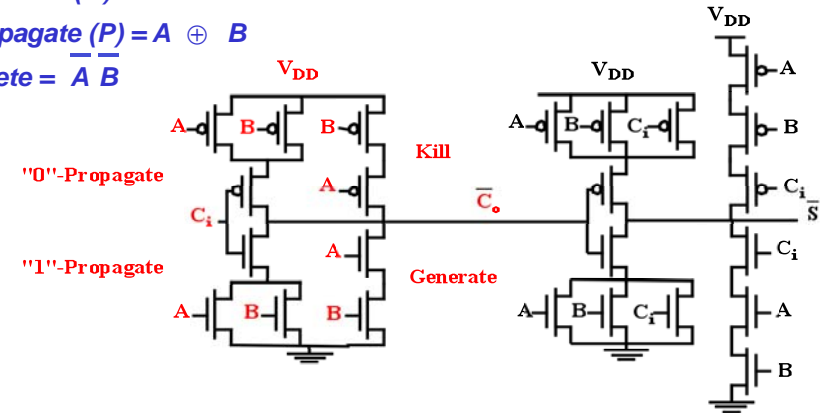


24 transistors

The Mirror Adder

- The NMOS and PMOS chains are **completely symmetrical**. This guarantees identical rising and falling transitions if the NMOS and PMOS devices are properly sized. A maximum of two series transistors can be observed in the carry-generation circuitry.
- When laying out the cell, the most critical issue is the minimization of the capacitance at node C_o . The reduction of the diffusion capacitances is particularly important.
- The capacitance at node C_o is composed of four diffusion capacitances, two internal gate capacitances, and six gate capacitances in the connecting adder cell.
- The transistors connected to C_i are placed closest to the output.
- Only the transistors in the carry stage have to be optimized for optimal speed. All transistors in the sum stage can be minimal size.

Quasi-Clocked Adder

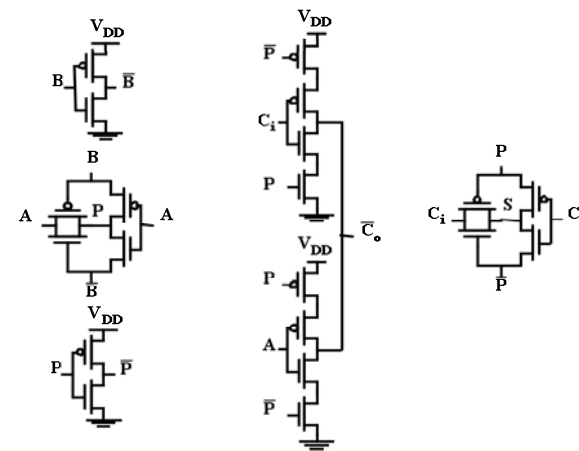


Signal Setup


Carry Generation

Sum Generation



Manchester Carry Chain

 

Sizing Manchester Carry Chain

 

  
$$t_p = 0.69 \sum_{i=1}^N C_i \left(\sum_{j=1}^i R_j \right)$$



Speed (normalized by $0.69RC$)


Area (in minimum size devices)

Carry-Bypass Adder

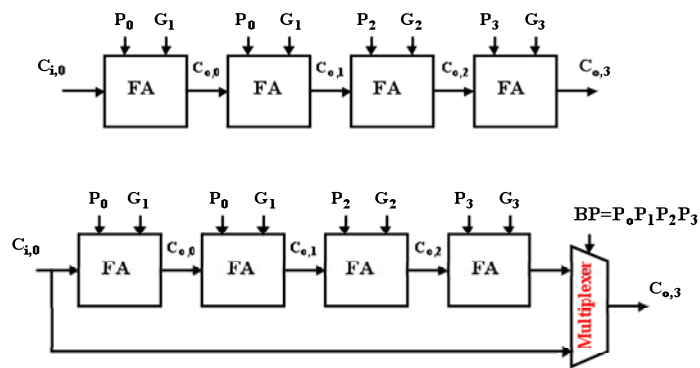


Idea: If $(P_0 \text{ and } P_1 \text{ and } P_2 \text{ and } P_3 = 1)$ then $C_{o3} = C_0$, else "kill" or "generate".


Manchester-Carry Implementation

 


Carry-Bypass Adder (cont.)

 


Carry Ripple versus Carry Bypass

 


Carry-Select Adder

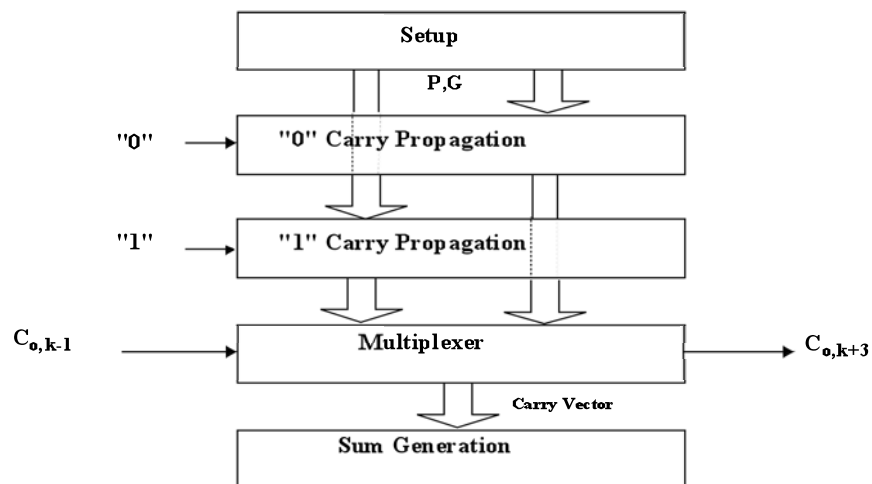

Carry Select Adder: Critical Path

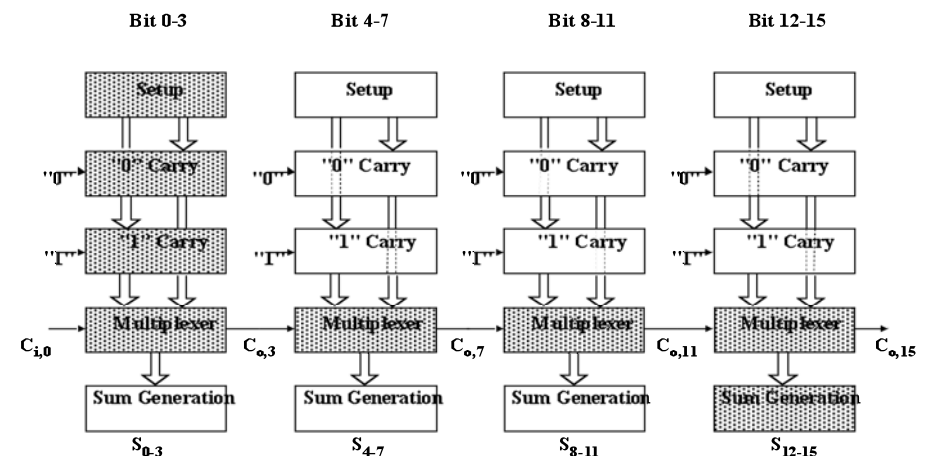


Linear Carry Select

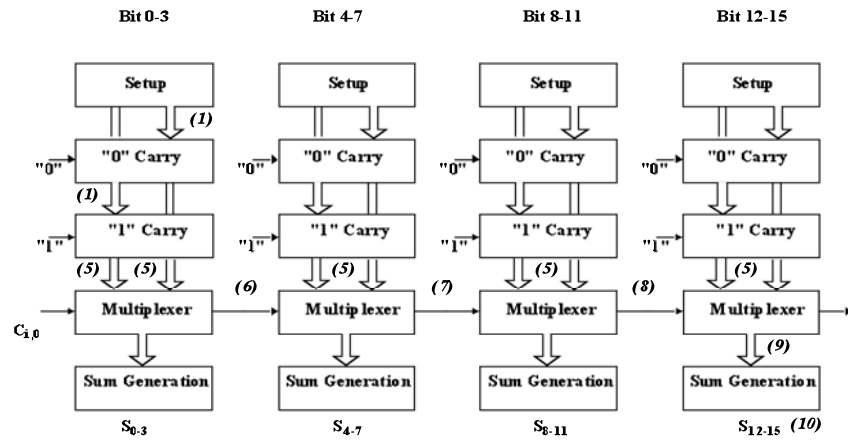


$$t_{add} = t_{setup} + \left(\frac{N}{M}\right)t_{carry} + Mt_{mux} + t_{sum}$$

Square Root Carry Select

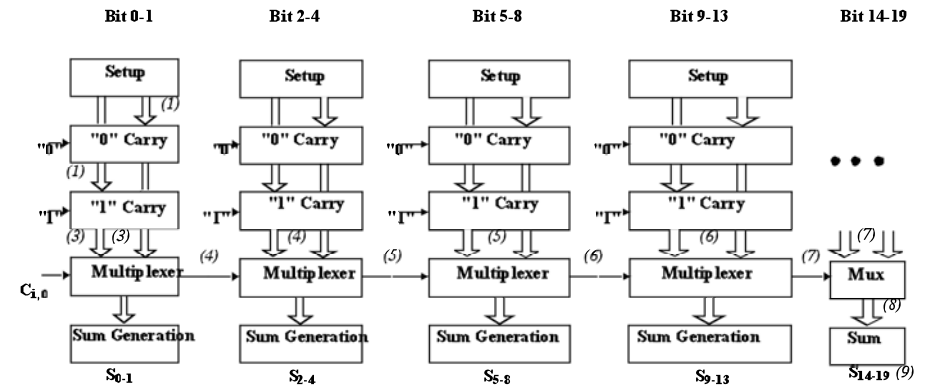


$$t_{add} = t_{setup} + P \cdot t_{carry} + (\sqrt{2N})t_{mux} + t_{sum}$$


Adder Delays - Comparison

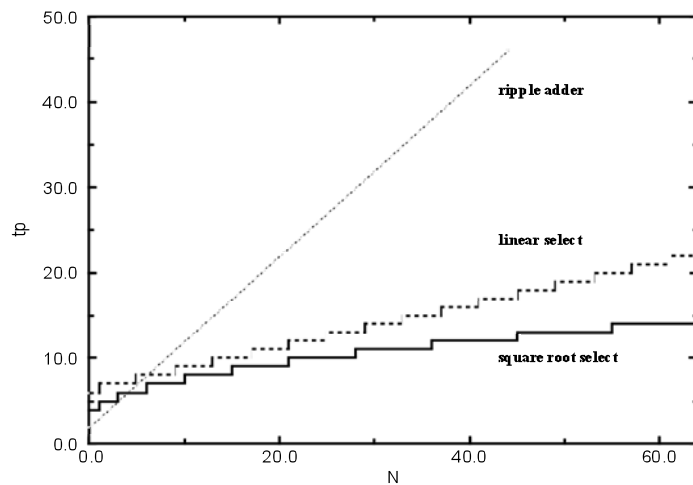


LookAhead - Basic Idea

 


Look-Ahead: Topology

 

The Array Multiplier

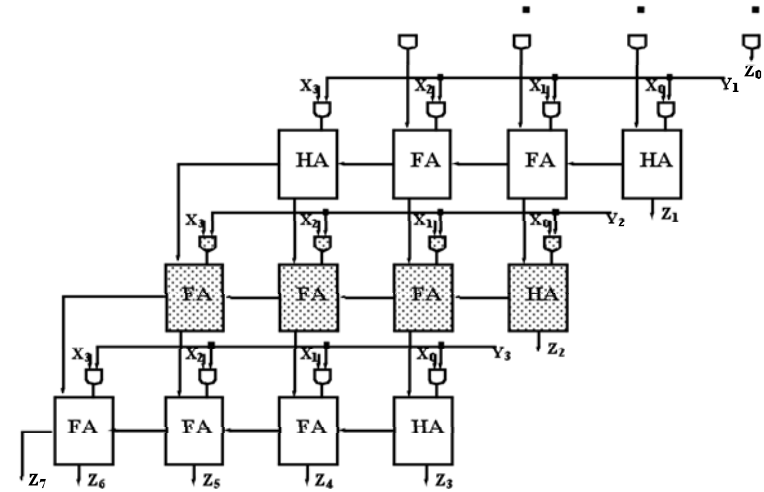


The MxN Array Multiplier — Critical Path

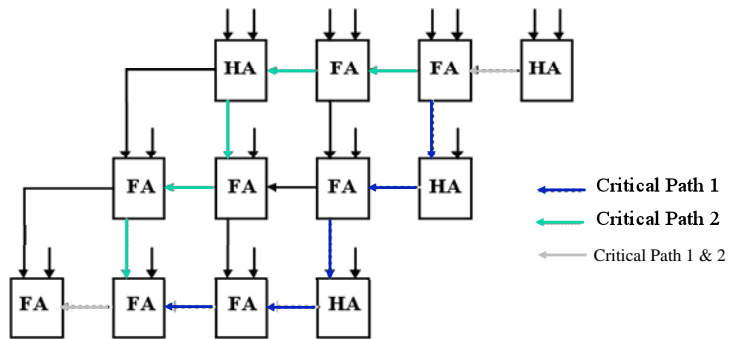

$$t_{mult} = [(M-1) + (N-2)]t_{carry} + (N-1)t_{sum} + (N-1)t_{and}$$


Carry-Save Multiplier

 

Vector Merging Adder


$$t_{mult} = (N-1)t_{carry} + (N-1)t_{and} + t_{merge}$$

Adder Cells in Array Multiplier

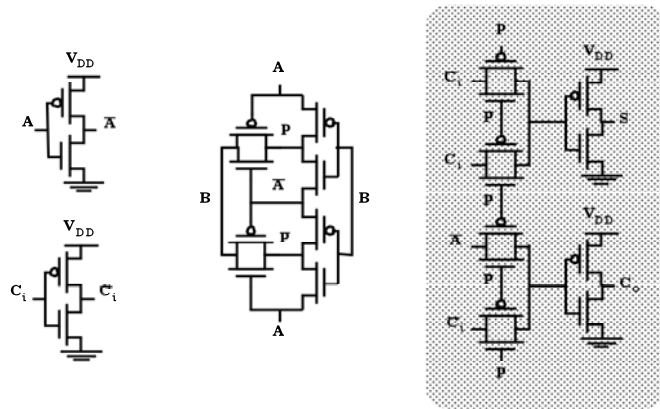

Identical Delays for Carry and Sum

Multiplier Floorplan

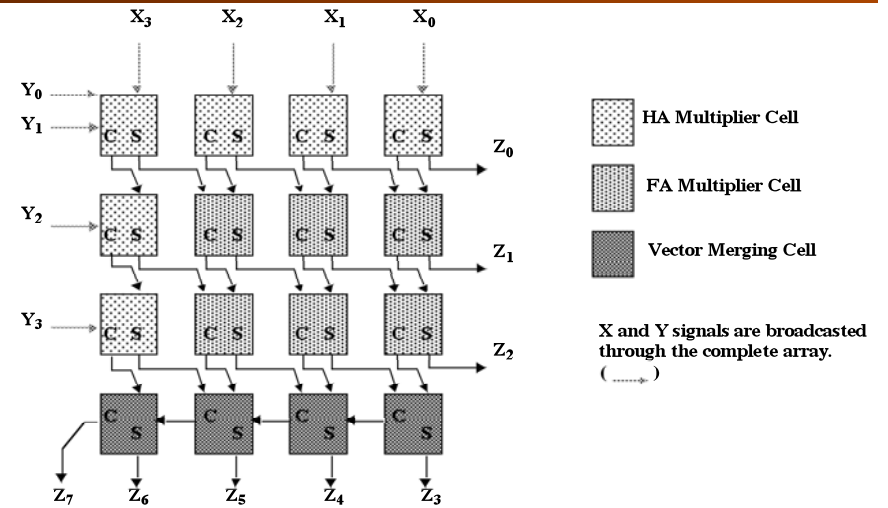


Multipliers —Summary


- Optimization Goals Different Vs Binary Adder
- Once Again: Identify Critical Path
- Other possible techniques
 - Logarithmic versus Linear (Wallace Tree Mult)
 - Data encoding (Booth)
 - Pipelining

FIRST GLIMPSE AT SYSTEM LEVEL OPTIMIZATION

The Binary Shifter

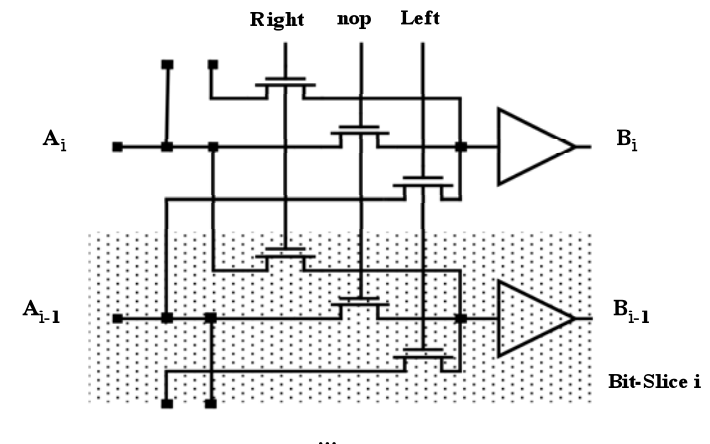


The Barrel Shifter

 


Area Dominated by Wiring

4x4 barrel shifter

 


$$\text{Width}_{\text{barrel}} \sim 2 p_m M$$

Logarithmic Shifter

 


0-7 bit Logarithmic Shifter

 


$$\text{width}_{\text{log}} \sim p_m (2K + (1 + 2 + \dots + 2^{K-1})) = p_m (2^K + 2K - 1)$$


Design as a Trade-Off

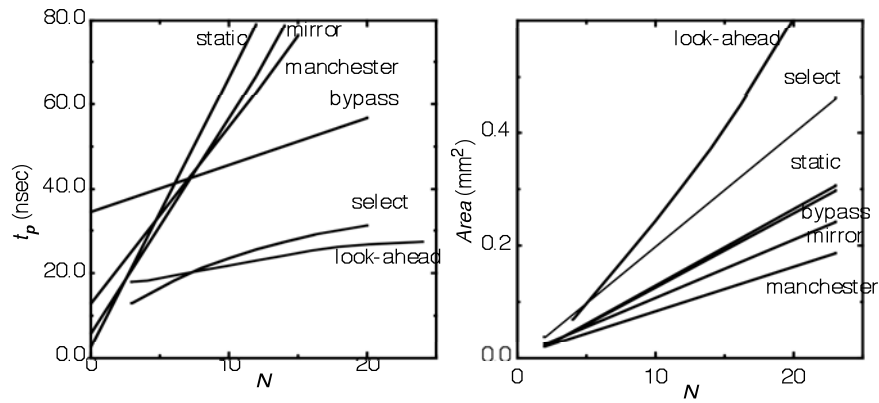

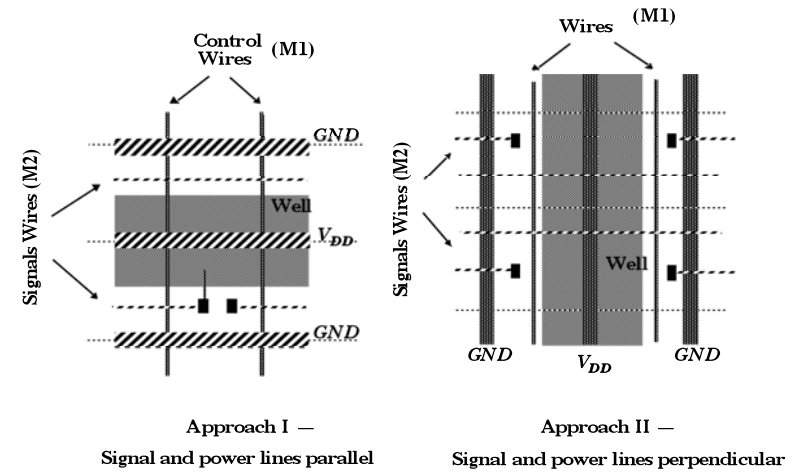Layout Strategies for Bit-Sliced Datapaths



Layout of Bit-sliced Datapaths

 

Layout of Bit-sliced Datapaths

- (a) Datapath without feedthroughs and without pitch matching (area = 4.2 mm^2).
- (b) Adding feedthroughs (area = 3.2 mm^2).
- (c) Equalizing the cell height reduces the area to 2.2 mm^2 .

