


Topic 5

Layout Design

Peter Cheung
 Department of Electrical & Electronic Engineering
 Imperial College London

URL: www.ee.ic.ac.uk/pcheung/
 E-mail: p.cheung@ic.ac.uk

Layout and Cross-section of an inverter

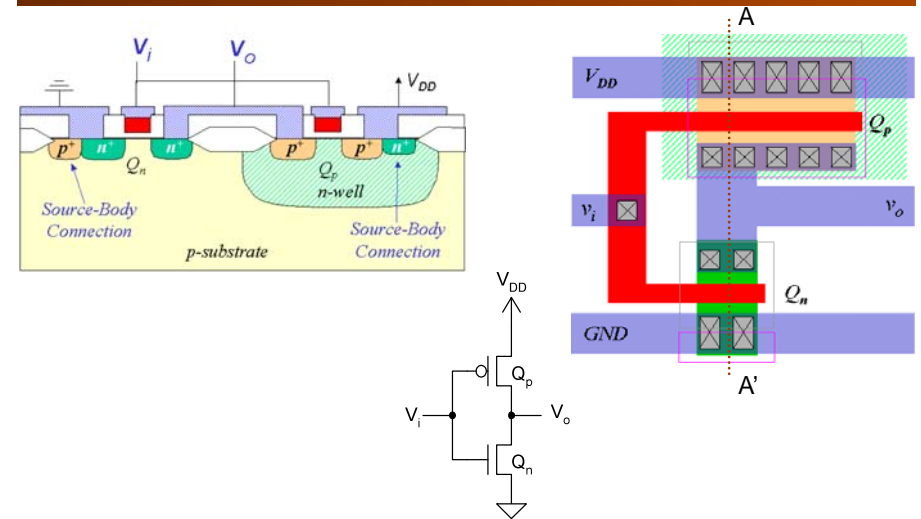


Layout & Fabrication

- ◆ Fabrication uses a set of layers that are usually not exactly the same as the layout layers that the designer use because:
 - It is easy to combine some layers together - for example, all "active" layers are diffusion layers (n+ and p+ diffusion) merged together.
 - Other layers used for fabrication can be deduced from other layers. For example, the n-well region can be deduced from the p-type diffusion.
 - Therefore most layout CAD tools use mask layers that are more intuitive to the layout designer, and map to the real mask later.
- ◆ CAD tools are used to generate the real mask layers for fabrication
 - Generating the manufacturing mask data is called '**tapeout**'
 - Some geometrical layout rules are created to make sure that this tapeout process is possible.
- ◆ We will be using Steve Rubin's Electric (version 8.05) as the main layout editing tools. Install and run Electric, and bring out the User's Manual. Read Chapter 2: Basic Editing. Complete Labs 1 & 2 (from course webpage).


Electric Handles Objects

 - ◆ Most CAD layout systems treat the IC layout as geometric layouts overlapping. For example, polysilicon layer overlapping n-diffusion gives you a n-transistor.
- ◆ Electric treat transistors and contacts as objects (called nodes). Read Chapter 1.6 of Electric User's Manual for the fundamental concepts.




Electric Connectivity

 
- ◆ Nodes are connected together using wires (called arcs).
- ◆ You must explicitly CONNECT wires to OBJECTS. Simply having overlaps of colour layers does not imply that they are electrically connected.



 Transistor **not** connected to diffusion wire




 Transistor **connected** to diffusion wire (highlighted)





Electric Handles Objects

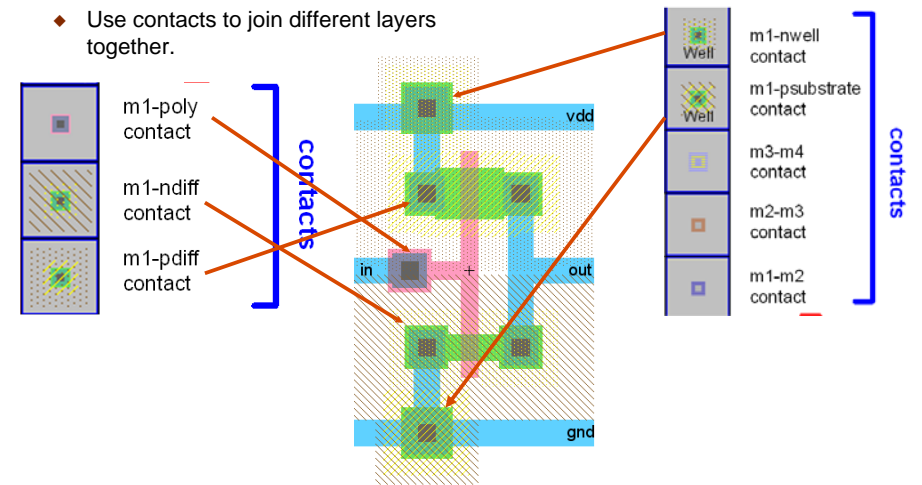- ◆ Use contacts to join different layers together.




What is this circuit?

  

Layout Design Rules

- ◆ Design Rules specifies the constraints on layout. Two types of layout constraints are important for this course:
 - Resolution constraints
 - Alignment/overlap constraints
- ◆ Resolution constraints specify:
 - Smallest width feature that can be used (e.g. channel length, wire width)
 - Smallest spacing that will guarantee no shorts
 - Governed by lithography and processing steps for technology used
 - Resolution often depends on the smoothness of the surface & how planar the process is.
- ◆ Alignment/overlap constraints specify:
 - Alignment between layers
 - Minimum overlaps or overhangs:

 

Scalable Design Rules and λ

- ◆ Design rules can be expressed in absolute physical units, e.g.
 - poly width $0.3\mu\text{m}$
 - poly spacing $0.45\mu\text{m}$
 - metal width $0.45\mu\text{m}$
 - metal spacing $0.45\mu\text{m}$
- ◆ Typically not multiples of one another in order to get the densest layout
- ◆ Difficult to remember
- ◆ Difficult to port from one process to another
- ◆ Scalable design rules express dimension in normalised units called **lambda (λ)**
- ◆ Normalise everything so the minimum gate length (i.e. width of poly gate) is $2*\lambda$
- ◆ All other design rules are expressed in integer multiples of λ
- ◆ For example:
 - poly width 2λ , space 3λ
 - metal width & space 3λ
- ◆ Usually requires rounding up
- ◆ These are subsequently scaled to generate masks for a variety of processes

Scalable Design Rules +

- ◆ MOSIS SCMOS design rules uses **lambda (λ)** based rules
 - Easily ported to many fabrication lines
 - Can scale to use smaller geometry in future
 - λ was initially 1.5μ , now it can be smaller than 0.15μ
- ◆ Conservative and less efficient in area because:
 - Use only Manhattan Layouts - i. e. everything are rectilinear and use only 90 degree angles
- ◆ Disadvantages (on area) is out-weighted by advantages
- ◆ Course web page gives all design rules for MOSIS Scalable process
- ◆ We target to 0.18μ technology

Some Important Geometric Rules (in λ)

Resolution rules:

LAYER	WIDTH	SPACE
poly	2	3
diff	3	3
metal1	3	3
metal2	3	4
nwell	12	6
cut	2	2
via	2	3

Alignment rules:

cut/via surround	1
poly overlap diff	2
poly space to diff	1

Notes:

Cut plus surround is 4
causes layout to fall on an 8λ grid


Some Important Geometric Rules (in λ)

Resolution rules:

LAYER	WIDTH	SPACE
poly	2	3
diff	3	3
metal1	3	3
metal2	3	4
nwell	12	6
cut	2	2
via	2	3


Alignment rules:

cut/via surround	1
poly overlap diff	2
poly space to diff	1

 


Well Spacing

 - ◆ N-trans and p-trans separate by 12λ with room for one wire in between.
- ◆ Metal1 pitch is 6λ and Metal2 pitch is 8λ .
- ◆ Contact size (including diffusion) is at least 4λ .




Estimate area

 - ◆ Estimate area by counting wiring tracks
 - Multiply by around 8 to express in λ . (Assuming you use metal 1 and 2 pitch of 8.)



Stick Diagram

- ◆ A stick diagram is a symbolic layout:
 - Contains the basic topology of the circuit
 - The relative positions of the objects are roughly correct, e.g. transistor 1 is to the right of transistor 2, and under transistor
- ◆ Each wire is assigned a layer, and crossing wires must be on different layers
 - Wires are drawn as stick figures with no width
- ◆ The size of the objects is not to scale
 - Add features such as wire easily in between other wires
- ◆ It is always much faster to design layout on paper using stick diagram first before using the layout CAD tool

 

Layout issues

- ◆ In CMOS there are two types of diffusion
 - ndiff (green) – Poly crossing ndiff makes nMOS transistors
 - pdiff (also green in Electric) – Poly crossing pdiff makes pMOS transistors
- ◆ Be careful, ndiff and pdiff are different
- ◆ You can't directly connect ndiff to pdiff
 - Must connect ndiff to metal and then metal to pdiff
- ◆ Can't get ndiff too close to pdiff because of wells
- ◆ Large spacing rule between ndiff and pdiff
- ◆ Need to group nMOS devices together and pMOS devices together because of large spacing rule between ndiff and pdiff


Planning a layout design

Here are a few simple guidelines to CMOS layouts

- ◆ You need to route power and ground (in metal), no automatic connection
- ◆ Try to keep nMOS devices near nMOS devices and pMOS devices near pMOS devices.
 - nMOS usually are placed near Gnd, and pMOS near Vdd
- ◆ Run poly vertically and diffusion horizontally, with metal1 horizontal (or the reverse, just keep them orthogonal)
 - Good default layout plan
- ◆ Keep diffusion wires as short as possible (just connect to transistor)
- ◆ All long wires (wire that go outside a cell, for example) should be in either m1 or m2.
- ◆ Try to design/layout as regular as possible

 
Example: O3AI

- ◆ OR 3-inputs, AND, then Inverter $Y = \overline{(A+B+C)} \cdot D$




Standard Cells

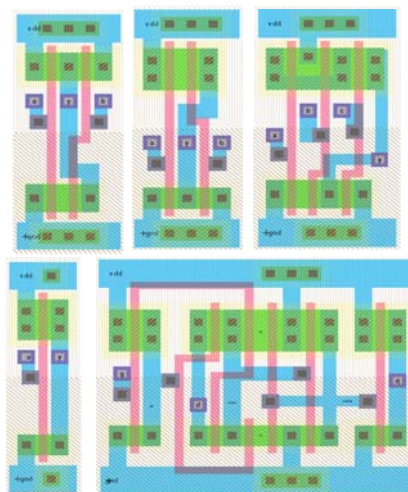- ◆ Uniform cell height
- ◆ Uniform well height
- ◆ M1 Vdd and Gnd rails
- ◆ M2 access to I/Os
- ◆ Well/substrate taps
- ◆ Exploits regularity



Synthesized circuit using standard cell

 - ◆ Synthesize Hardware Description Language into gate-level netlist
- ◆ Place-and-Route using standard cell library



Pitch Matching

- ◆ Design snap-together cells for datapaths and arrays (such as RAM & ROM)

- Plan wires into cells
- Connect by abutment like putting lego block together.
- No extra wire area needed

A	A	A	A	B
A	A	A	A	B
A	A	A	A	B
A	A	A	A	B
C		C		D

MIPS Processor Datapath

- ◆ 8-bit datapath built from 8 bitslices (regular)
- ◆ Control circuit at the top of the datapath

